



دانشگاه صنعتی امیر کبیر
(پلی تکنیک تهران)

Electrical and Electronic Circuits

chapter 13. Operational Amplifier

Afarghadan@aut.ac.ir

عظیم فرقدان 



مهر ۱۴۰۳

Objectives of the Lecture


- Introduction to Operational Amplifiers
 - Precise Model of Operational Amplifiers
 - Ideal Model
 - Applications of Operational Amplifiers
 - Inverting Amplifier
 - Non-Inverting Amplifier
 - Voltage Follower (Buffer)
 - Multi-Stage Amplifier
 - Ideal Voltage and Current Sources
- Comparator Circuit
- Several Examples

Operational Amplifier (Op-Amp)

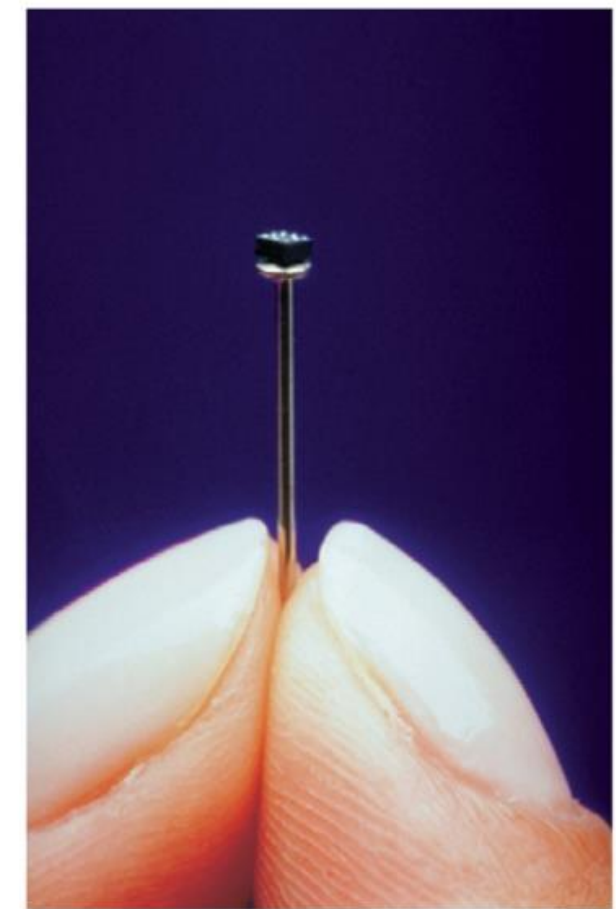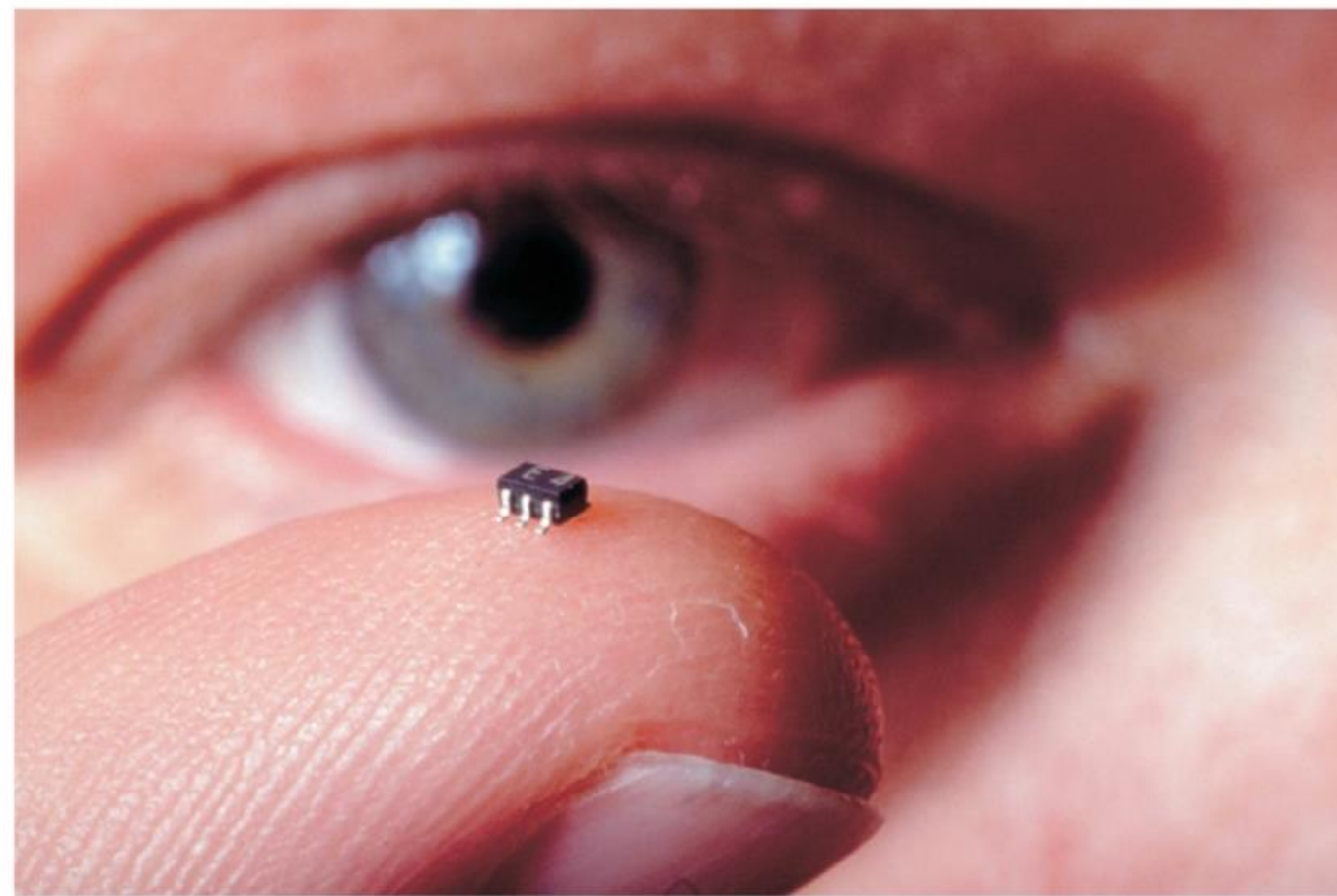
- The **Operational Amplifier (Op-Amp)** is an integrated circuit (IC) widely utilized as an amplifier in various applications.
- Its origins date back to the 1940s when it was employed in analog computational circuits for constructing adders, sub tractors, and analog multipliers.



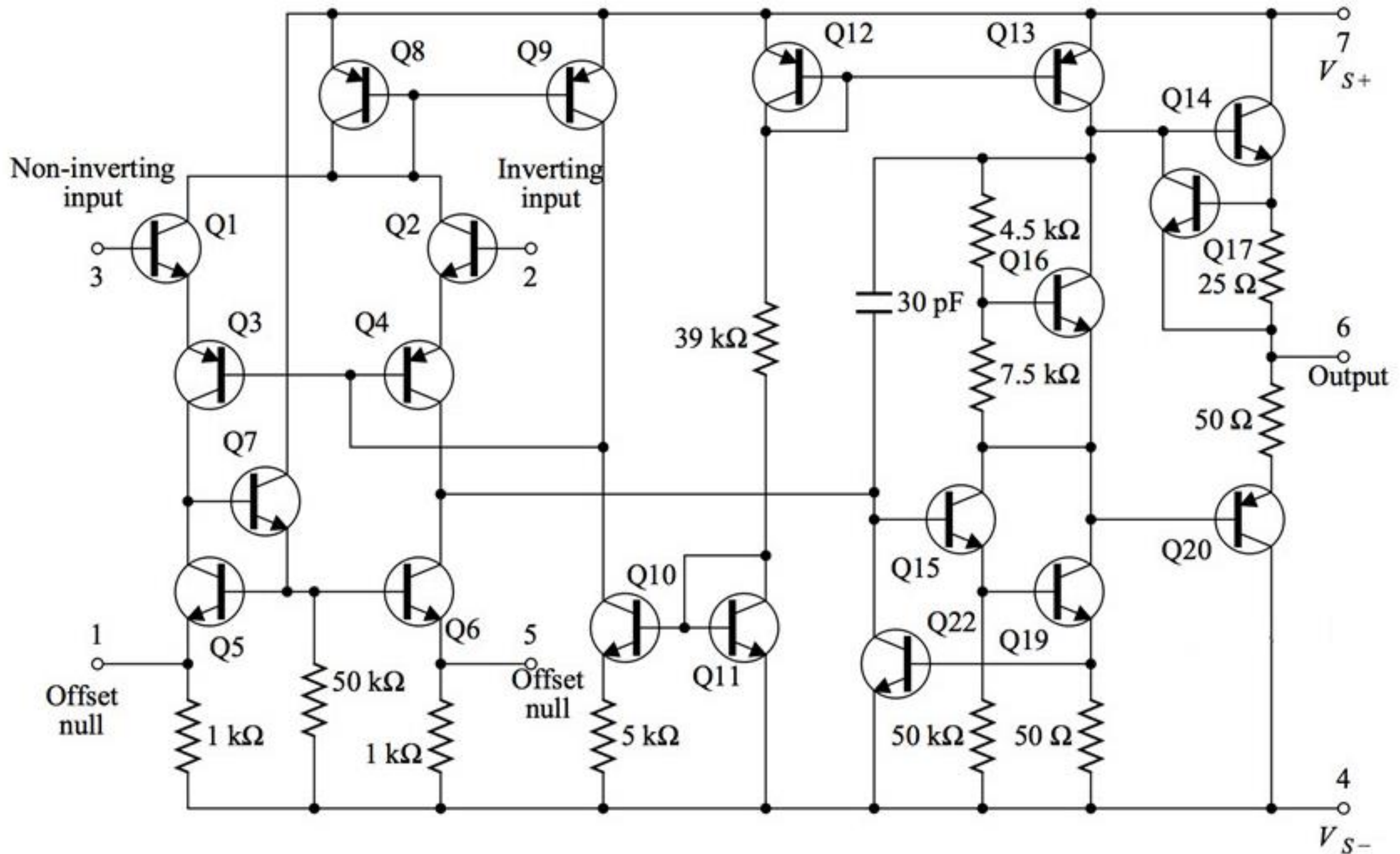The Internal Circuit of a Typical Operational Amplifier




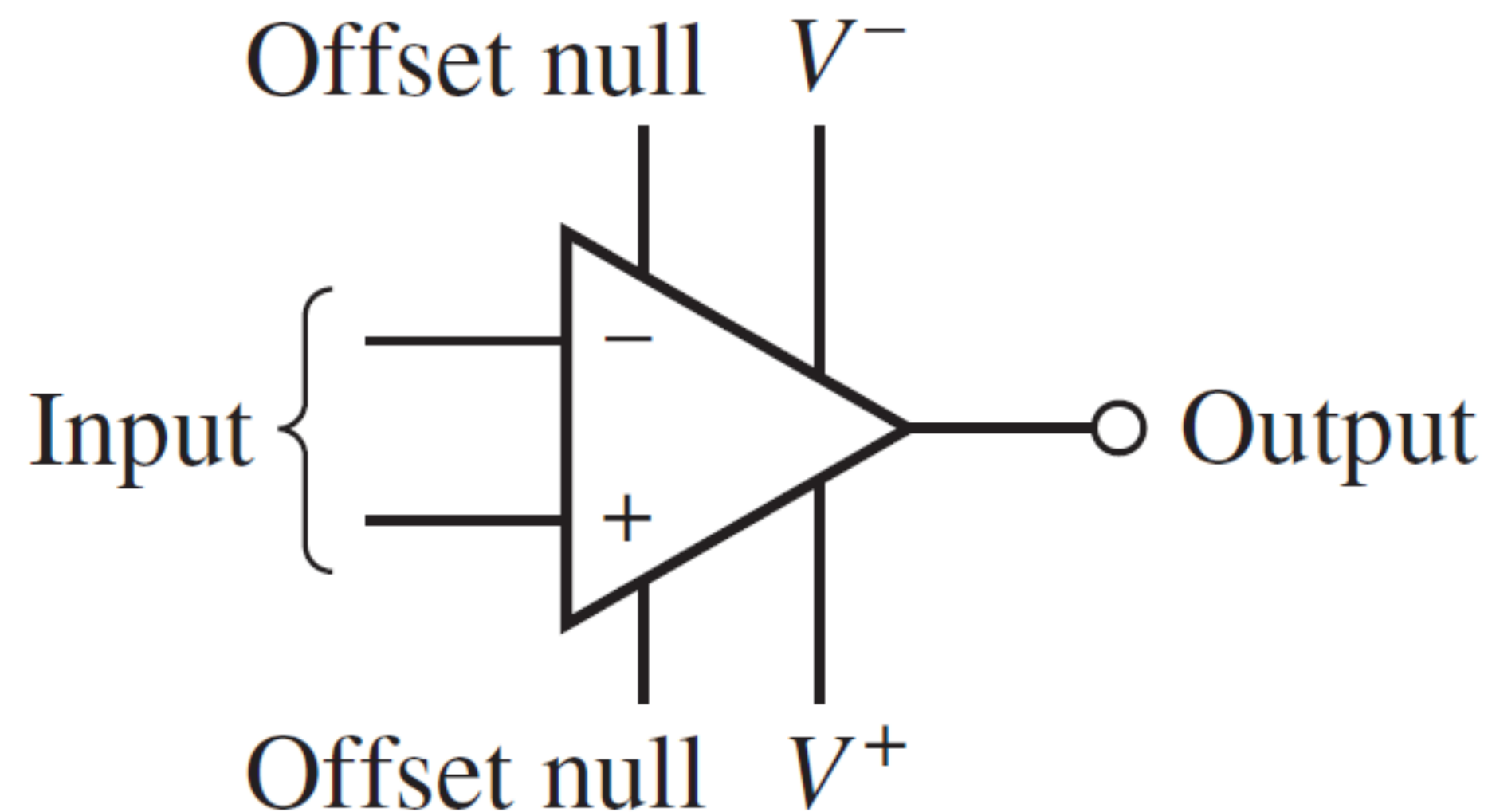- An operational amplifier (Op-Amp) is generally represented by the following symbol and includes the following pins:
- **Input Pins:** *Input*
- **Output Pin:** *Output*
- **Power Supply Pins:** V^+ , V^-
- **Offset Adjustment Pins:** *Offset*




Op-Amp Symbol

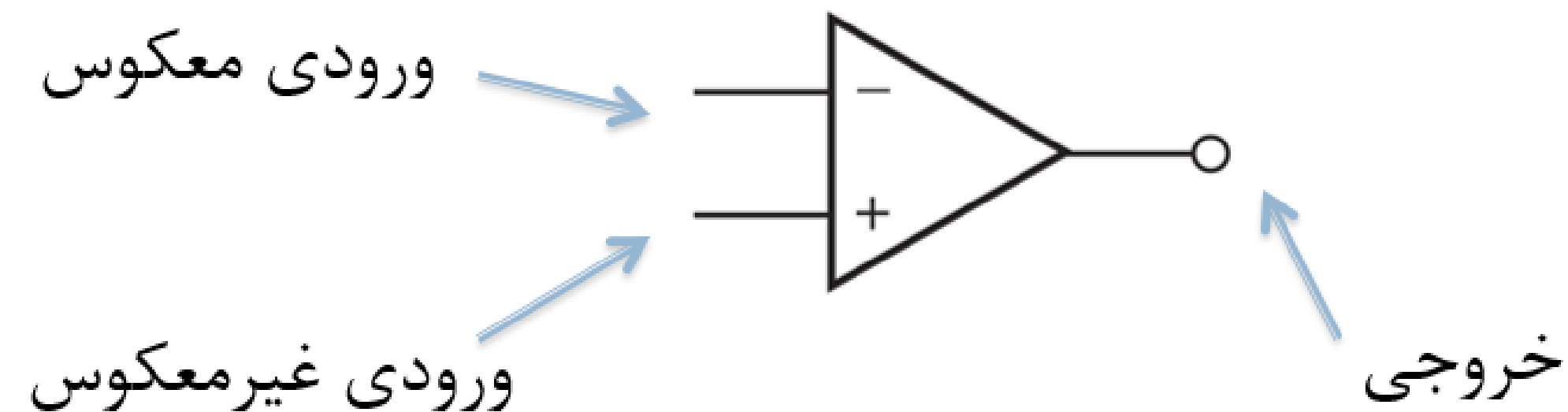- ✓ Let us focus on the **input** and **output pins**, assuming the other pins are connected to appropriate voltage levels.
- ✓ An operational amplifier functions as a **differential amplifier**, meaning it amplifies the difference between its input signals.



Precise Model of an Op-Amp

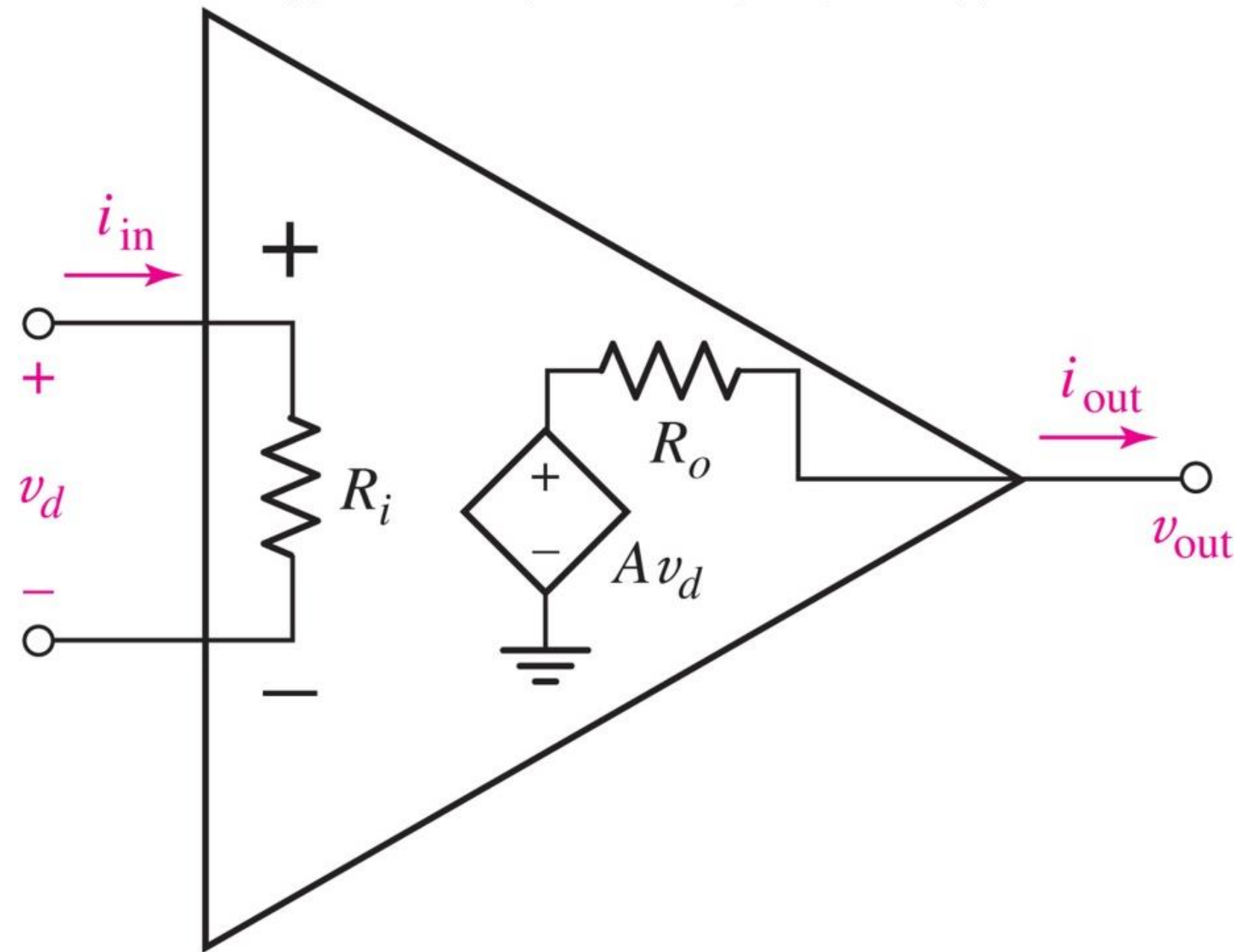
- A circuit that operates as a voltage amplifier can be modelled using the following equivalent circuit.
- This model includes:
 - **Input Resistance (R_i)**
 - **Output Resistance (R_o)**
 - **Open-Loop Gain (A)**



✓ In the circuit below, what is the gain of the amplifier?

➤ $KCL_1: \frac{-v_d - v_{in}}{R_1} + \frac{-v_d - v_{out}}{R_f} + \frac{-v_d}{R_i} = 0$

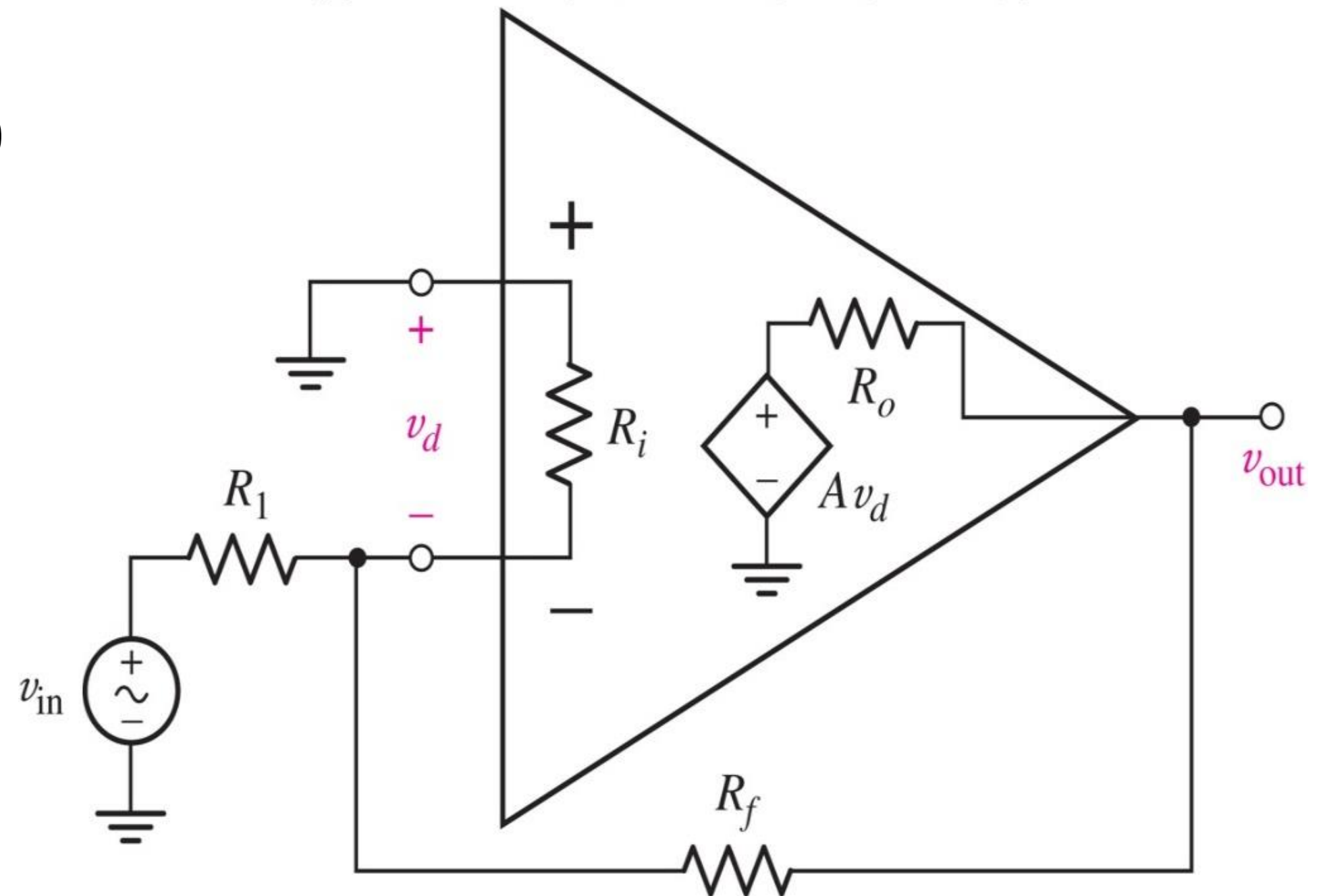➤ $KCL_2: \frac{v_{out} + v_d}{R_f} + \frac{v_{out} - Av_d}{R_o} = 0$



✓ By solving the system of equations and eliminating v_d , we obtain:

$$\blacktriangleright A_v = \frac{v_{out}}{v_{in}} = \left[\frac{R_o + R_f}{R_o - A R_f} \left(1 + \frac{R_1}{R_f} + \frac{R_1}{R_i} \right) - \frac{R_1}{R_f} \right]^{-1}$$

➤ Example Solution for the Inverting Amplifier Using LM741 Specifications


➤ $A = 200000$

➤ $R_i = 2M\Omega$

➤ $R_o = 75\Omega$

➤ If $R_f = 47$ and $R_1 = 4.7$

➤ Then: $A_v = -9.999$

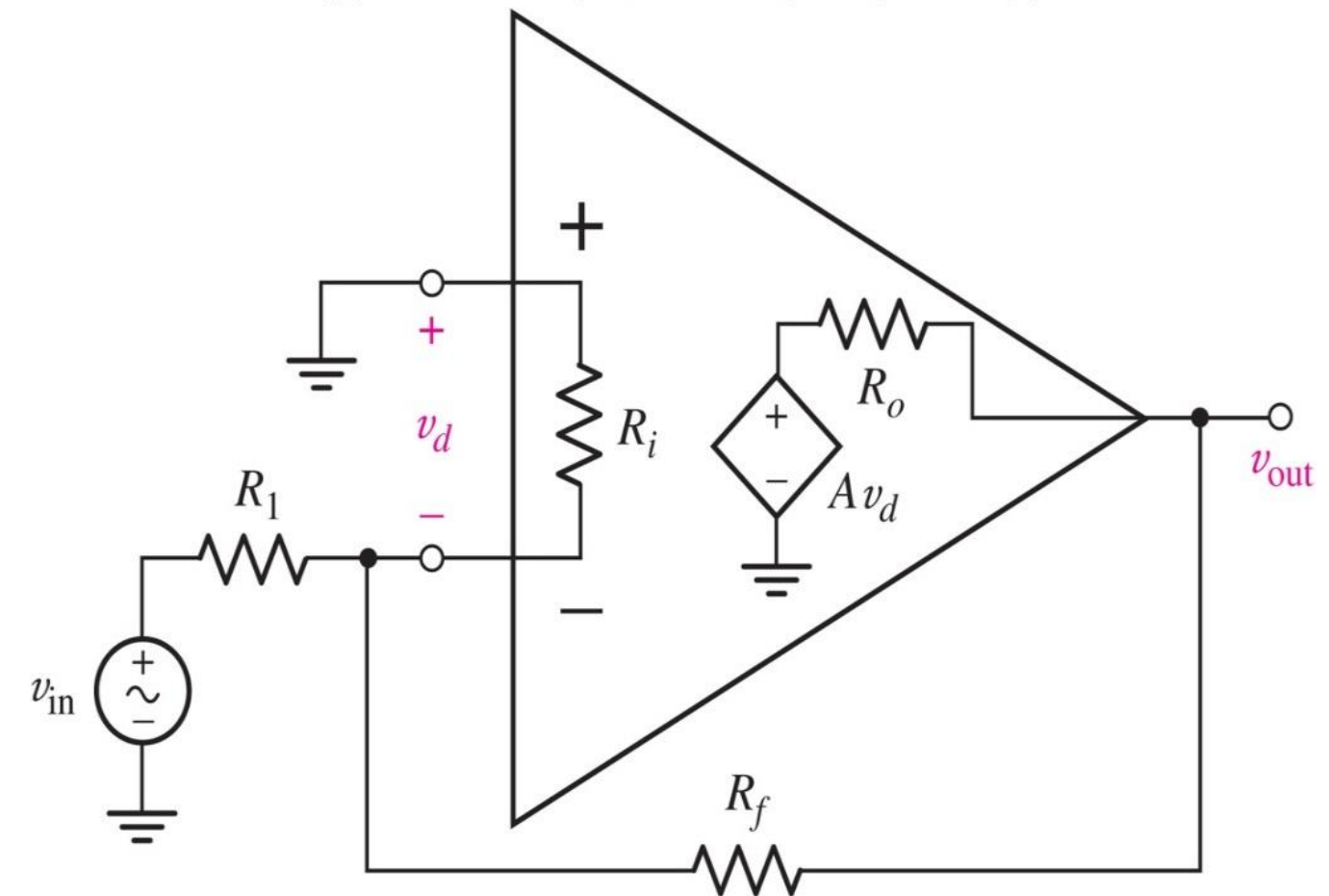

- ✓ **High Input Resistance:**(in the range of mega-ohms to tera-ohms)
 - To ensure that the maximum voltage of the source is applied across its input.
- ✓ **Low Output Resistance:**(in the range of a few ohms to a few tens of ohms)
 - to ensure that the entire output voltage of the amplifier is delivered to the load.
- ✓ **Adjustable Gain:**(achieved by applying feedback resistance):
 - As observed in the circuit shown, provided that A is sufficiently large, the gain of the amplifier can be approximated with high accuracy as $A_v \approx -\frac{R_f}{R_1}$.


Ideal Model

➤ In the ideal case, when $A = \infty$, $R_i = \infty$, and $R_o = 0$, the behaviour of the operational amplifier can be described as follows:

➤ Since v_{out} has a finite value (it cannot exceed the supply voltage),


$$v_d = \frac{v_{out}}{A} \approx 0.$$

➤ As a result, $i_{in} \approx 0$.

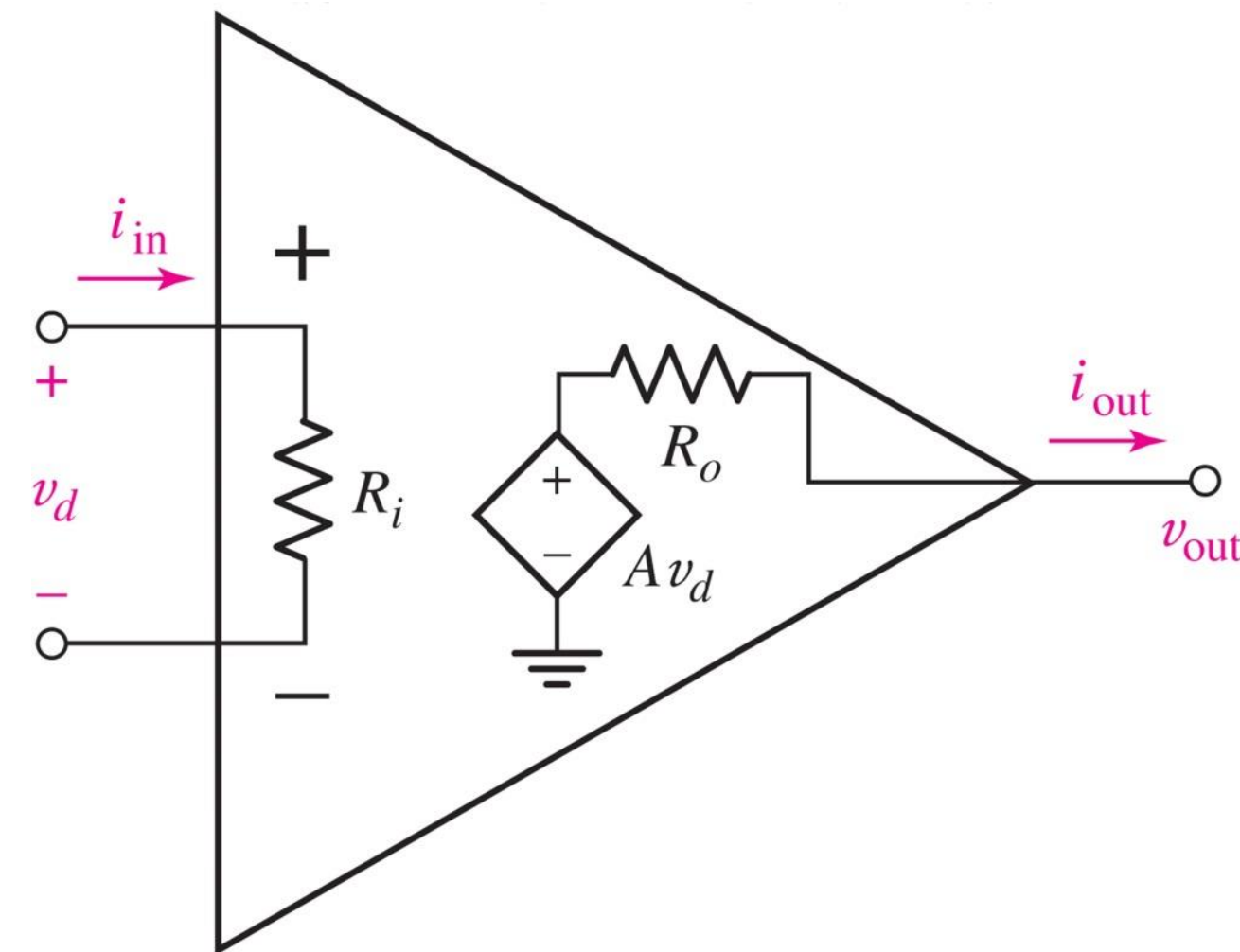


Rules of the Ideal Model:

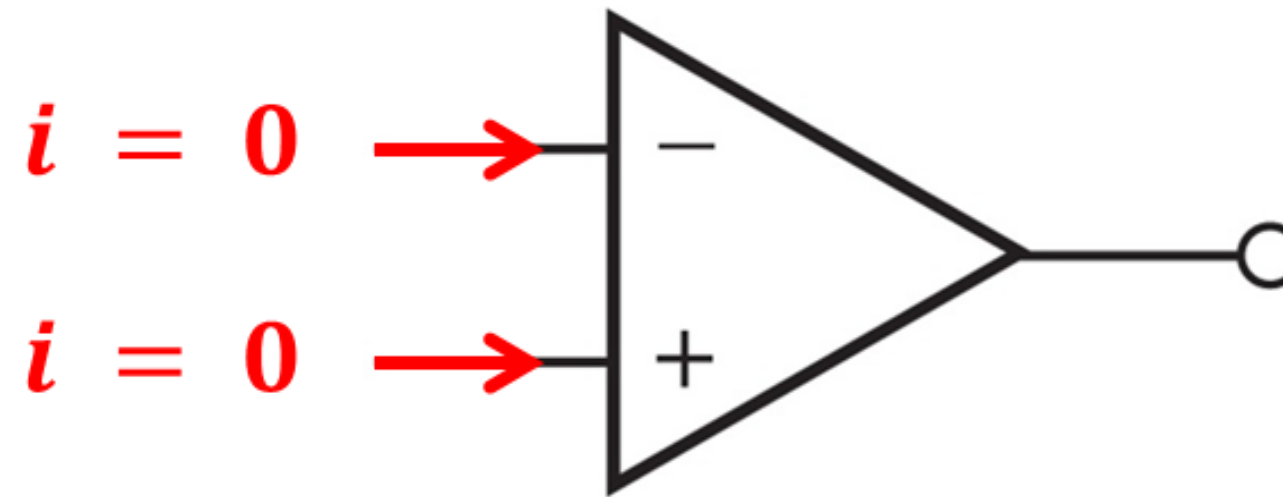1.No current flows through the input terminals.




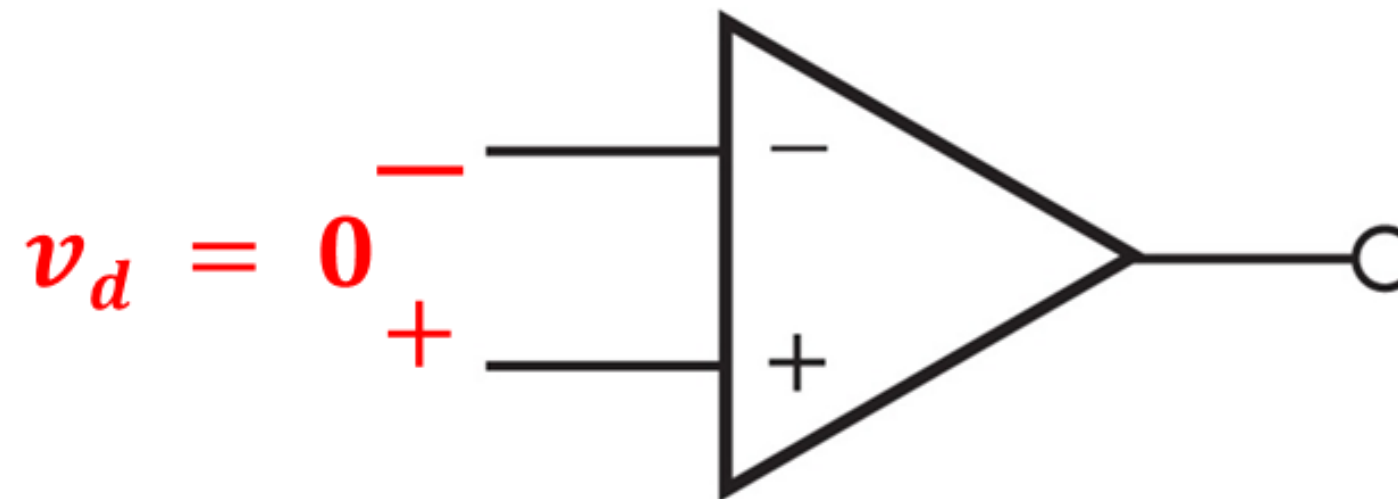2.The voltage difference between the two input terminals is zero.



Inverting Amplifier

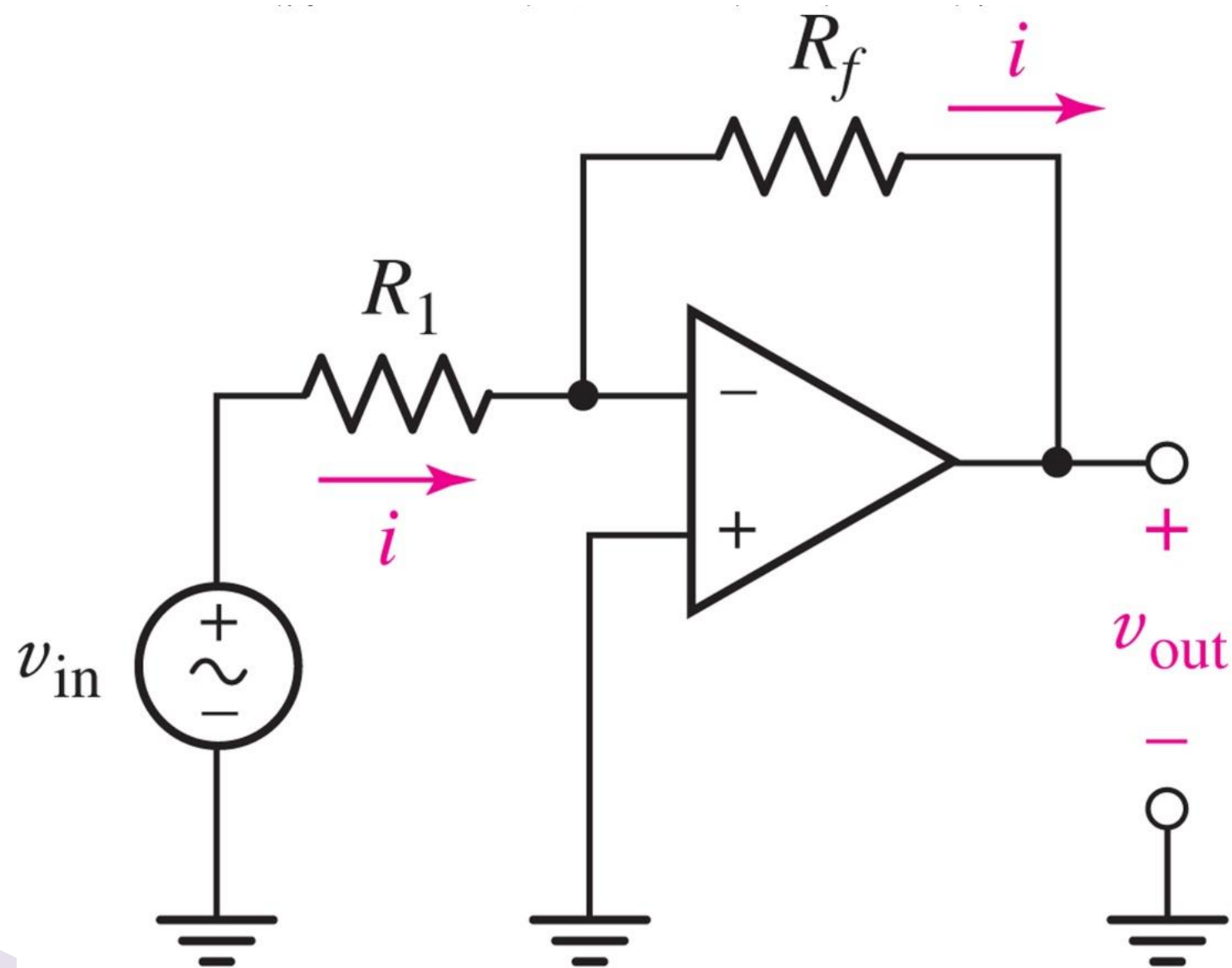- ✓ By applying KVL and using the rules of the ideal operational amplifier, we have:





$$v_{out} = -\frac{R_f}{R_1} v_{in}$$


Example

- $v_{in}(t) = 5\sin 3t \text{ mV}$, $R_f = 47\text{K}\Omega$, $R_1 = 4.7\text{K}\Omega$

$$v_{out}(t) = -50 \sin 3t \text{ mV}$$

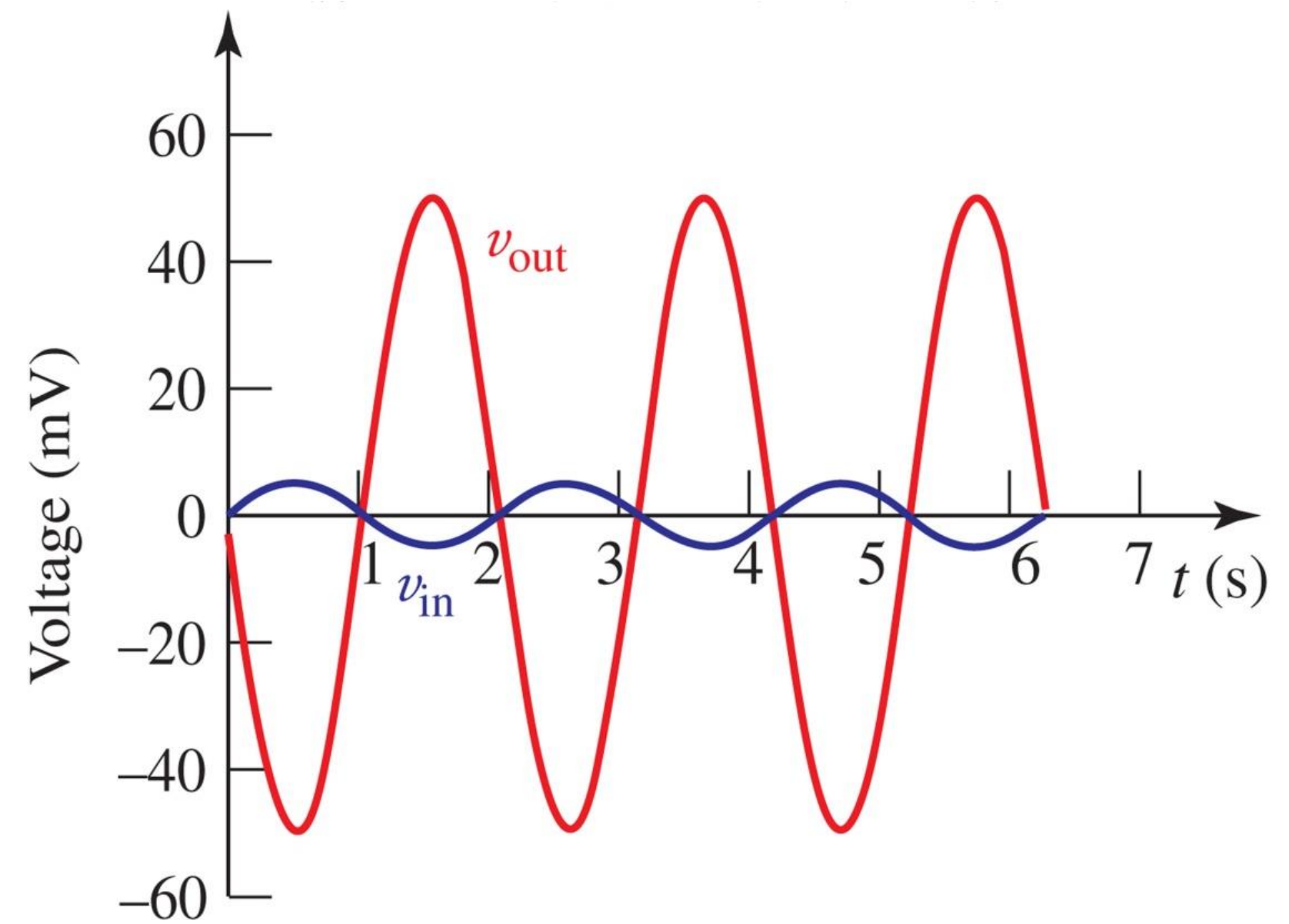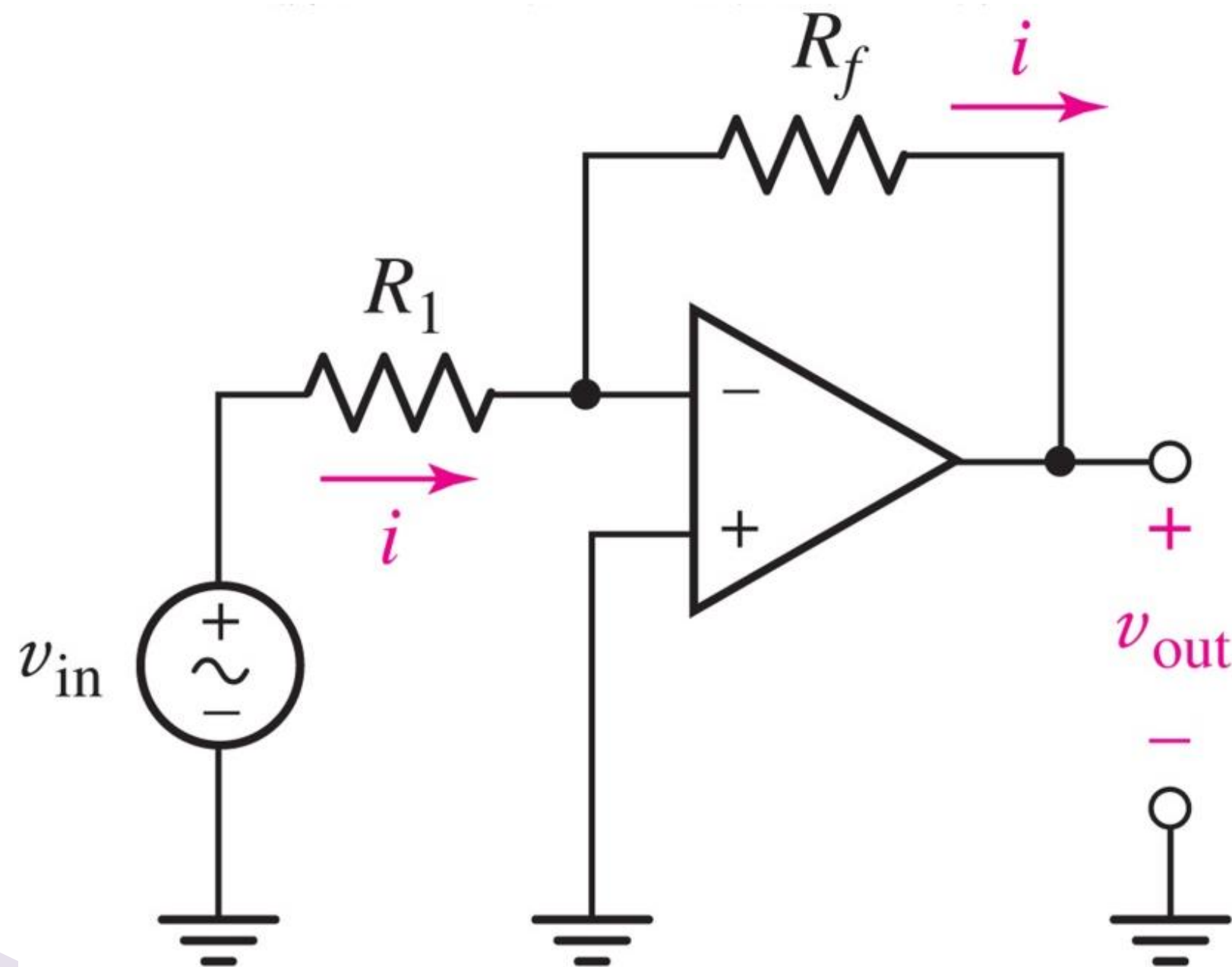


Non-Inverting Amplifier

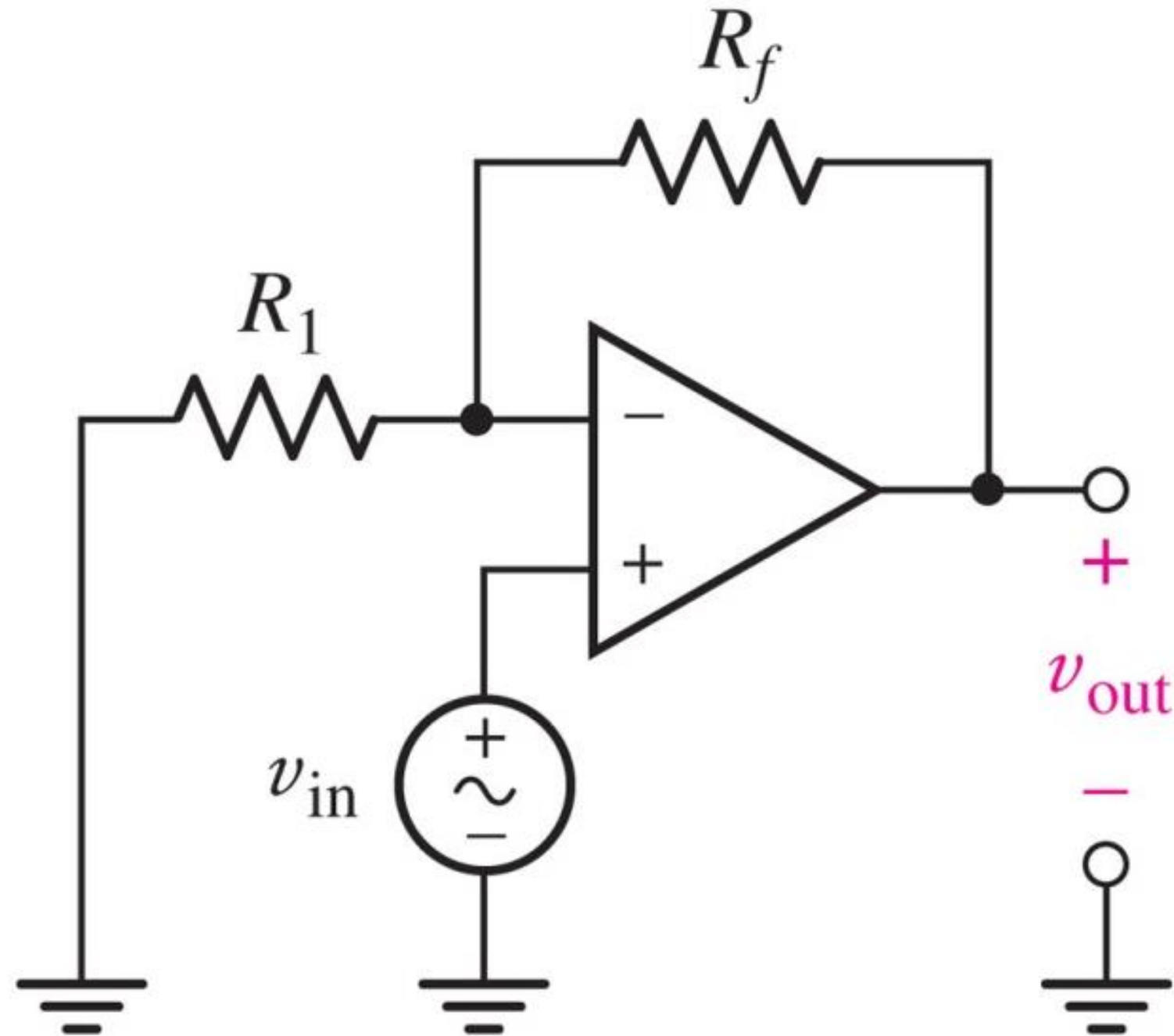

$$v_{out} = \left(1 + \frac{R_f}{R_1} \right) v_{in}$$


Voltage Follower (Buffer)

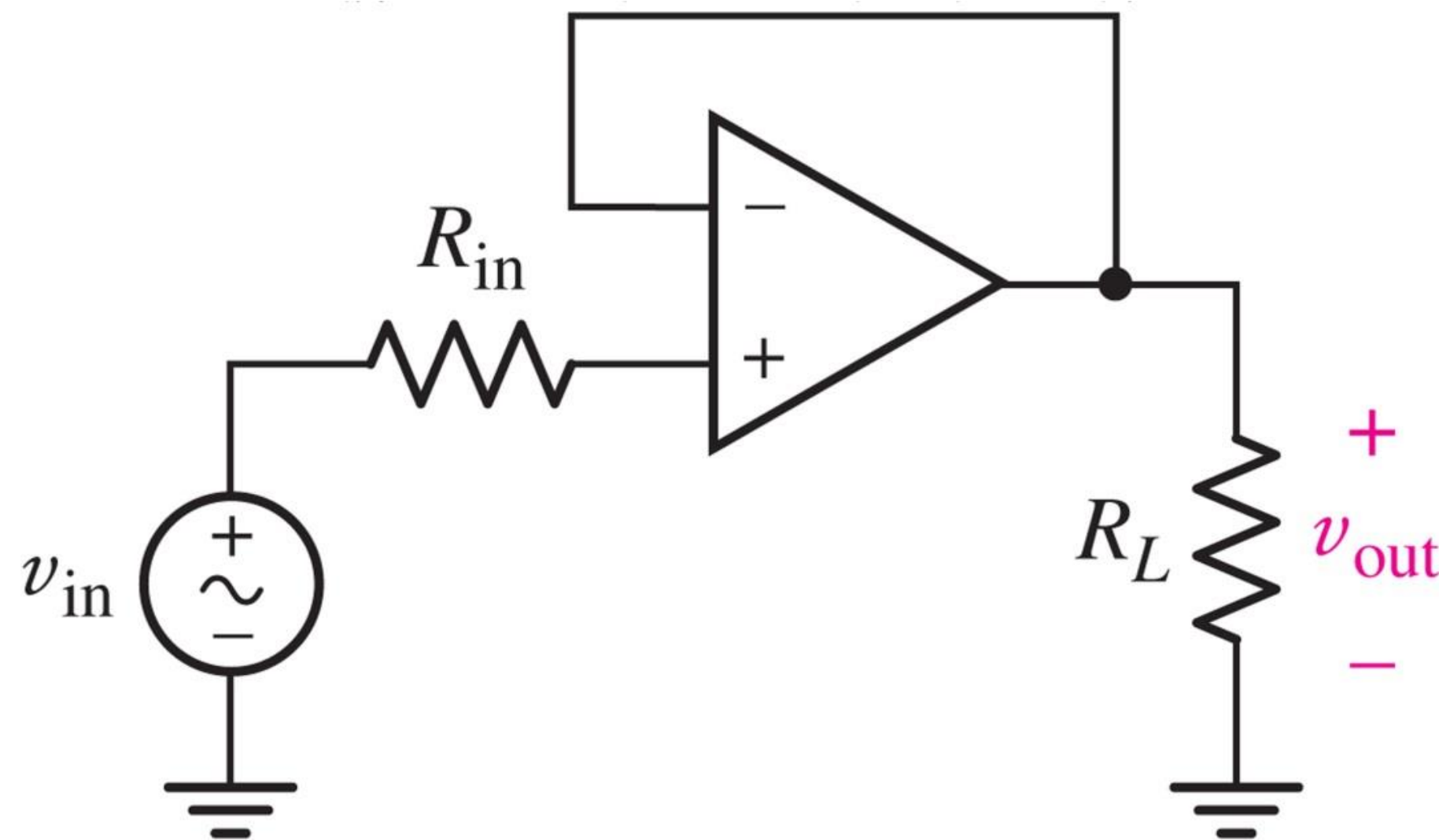

$$v_{out}(t) = v_{in}(t)$$

1. The output voltage of the buffer is independent of the load resistance (R_L). The buffer can **supply the required current** to maintain a constant output voltage, even if R_L changes.
2. This circuit eliminates the effect of the source's input resistance by presenting a very high input resistance to the source and a very low output resistance to the load.


Analog Summing Circuit

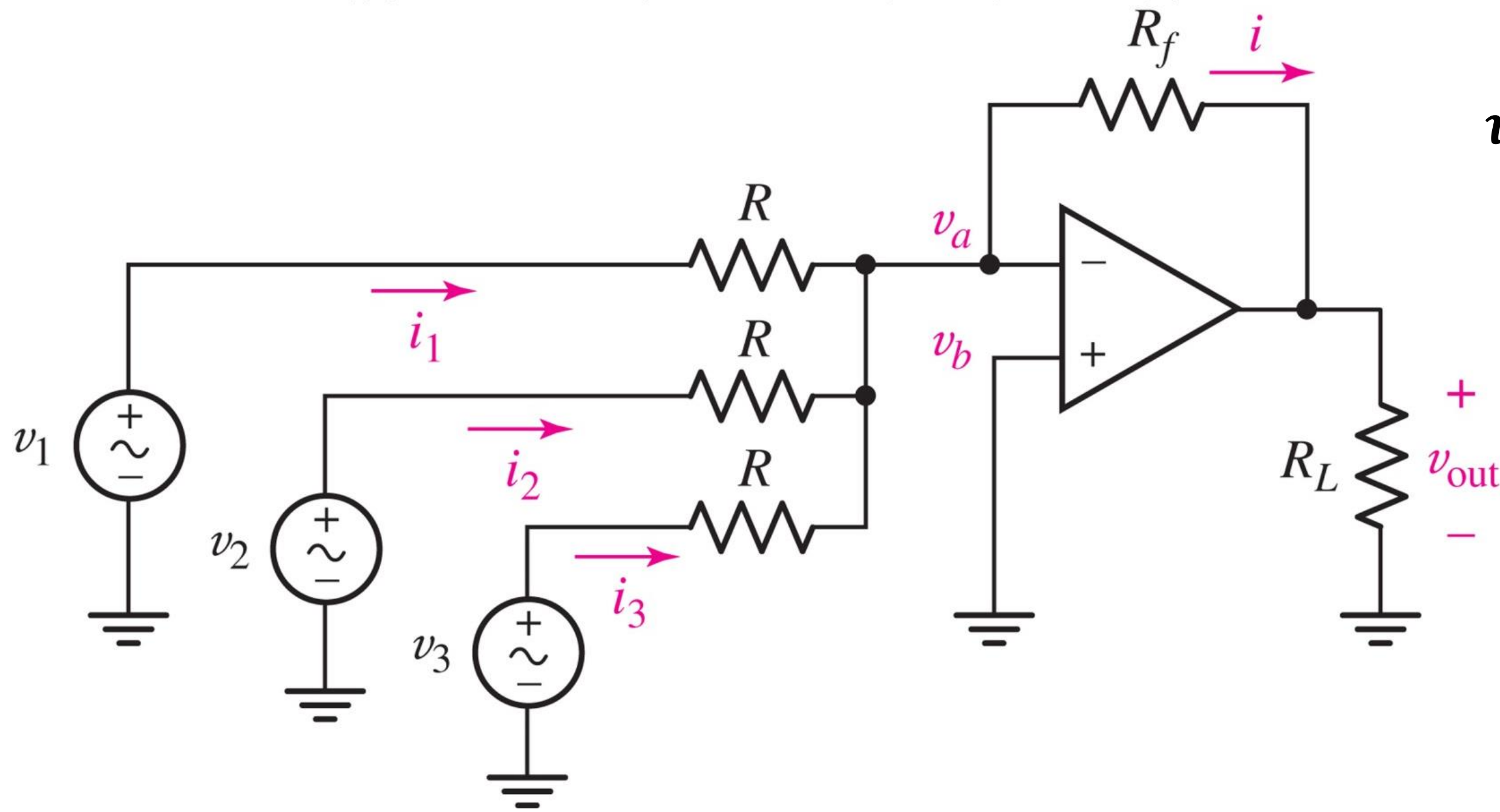

$$v_{out} = -\frac{R_f}{R} (v_1 + v_2 + v_3)$$

- ✓ This circuit performs the addition of input signals and amplifies the result by a factor of $-\frac{R_f}{R}$.

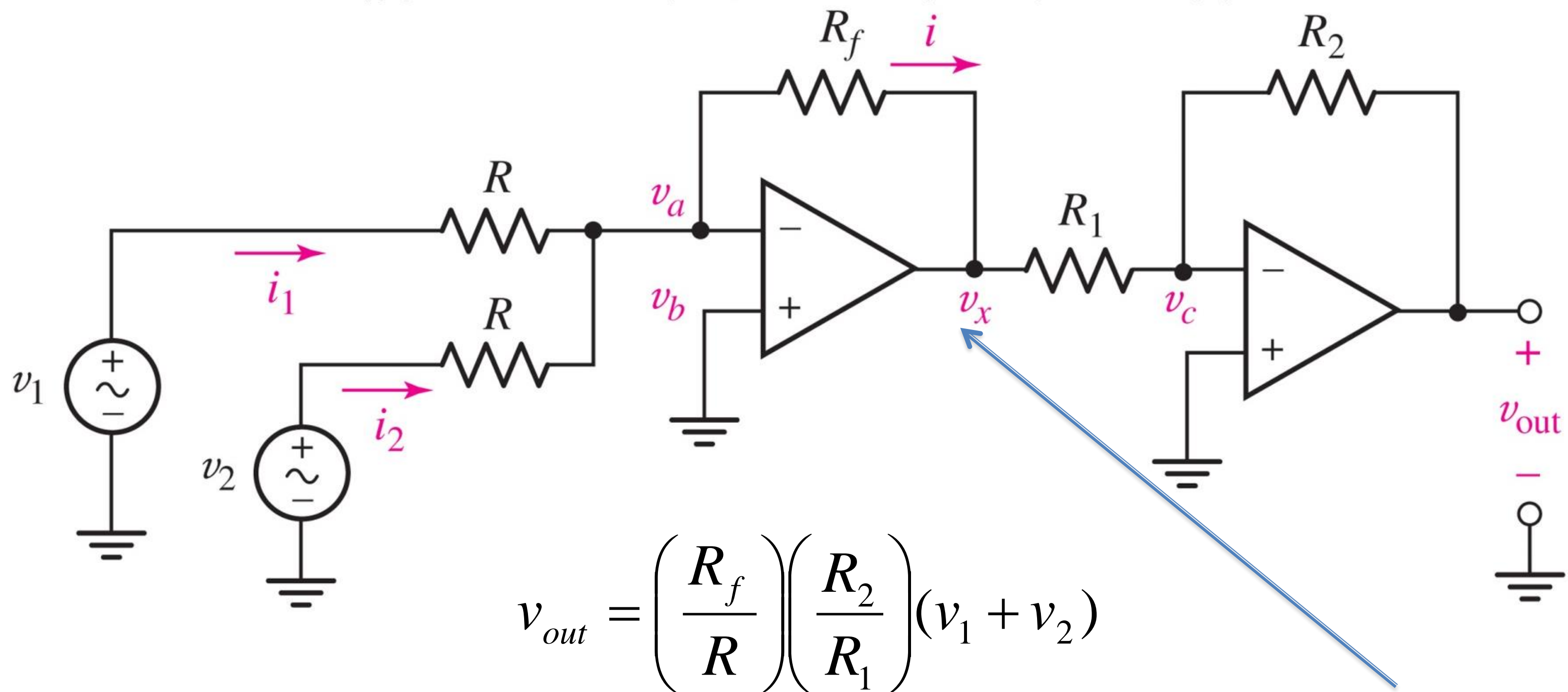
Cascading Multiple Operational Amplifiers



- ✓ The output voltage of each stage is independent of the subsequent stage. (**Why?**)
- ✓ As a result, **Op-Amp** can be cascaded without any alteration in their individual gains.


Op-Amp as an Ideal Voltage Source
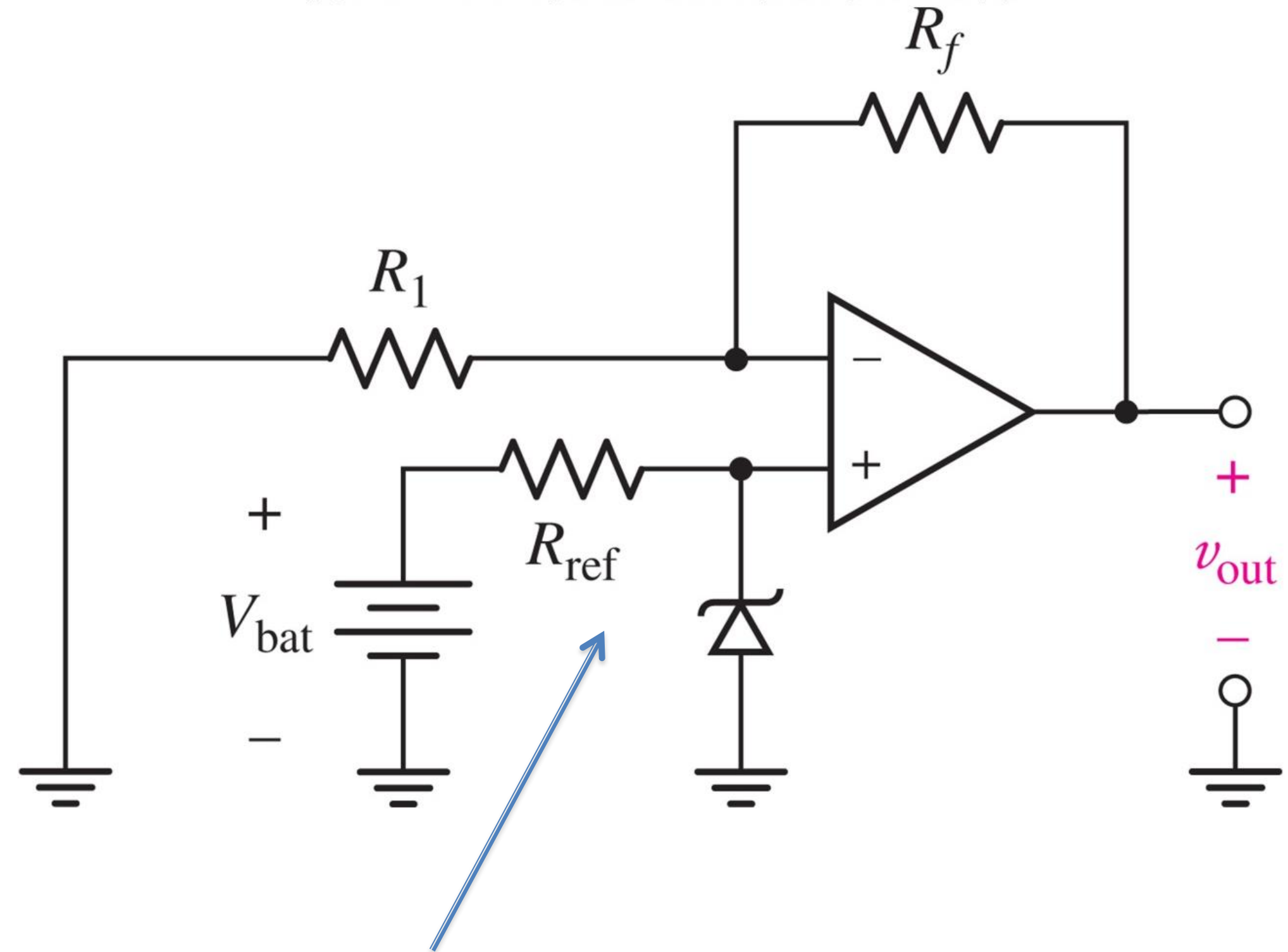
$$v_{out} = \left(1 + \frac{R_f}{R_1}\right) V_Z$$



This circuit resembles the voltage regulator using a Zener diode, which we have encountered before.

Op-Amp as an Ideal Current Source

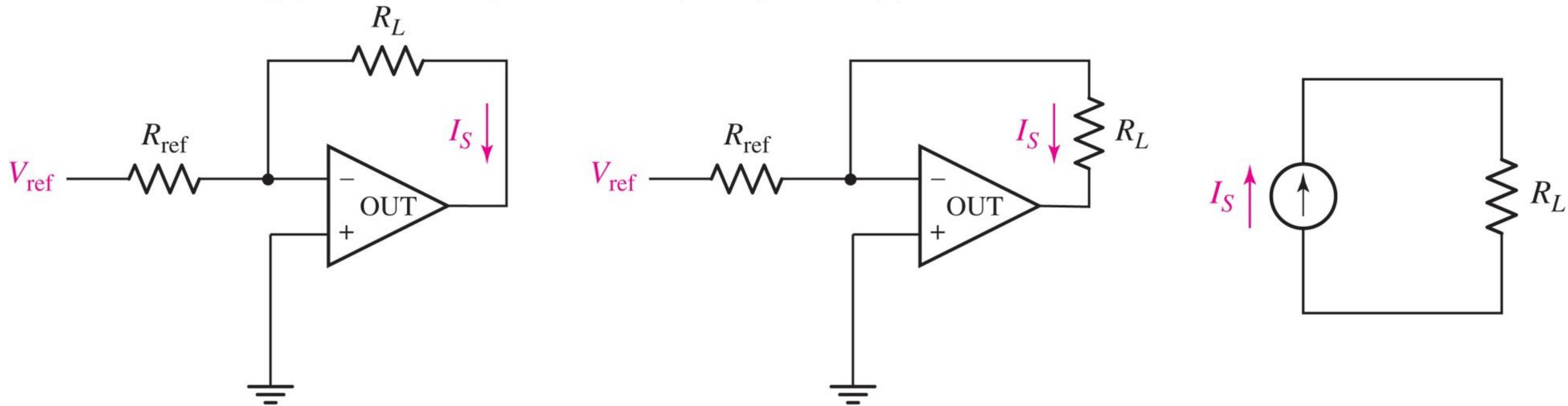


- Using a reference voltage V_{ref} and a resistor R_{ref} , an ideal current source can be constructed with a current:

$$I_S = \frac{V_{ref}}{R_{ref}}$$

- This current is independent of the load resistance R_L ,


Power Supplies for Op-Amp

- An operational amplifier requires power to function and perform amplification. Therefore, it must be connected to a power supply.
- Typically, equal and opposite voltage values are applied to the V^+ and V^- terminals. These voltage levels usually range between $\pm 5V$ and $\pm 24V$.
- The ground of the power supplies must be connected to the input and output ground reference of the circuit to ensure proper operation and signal integrity.

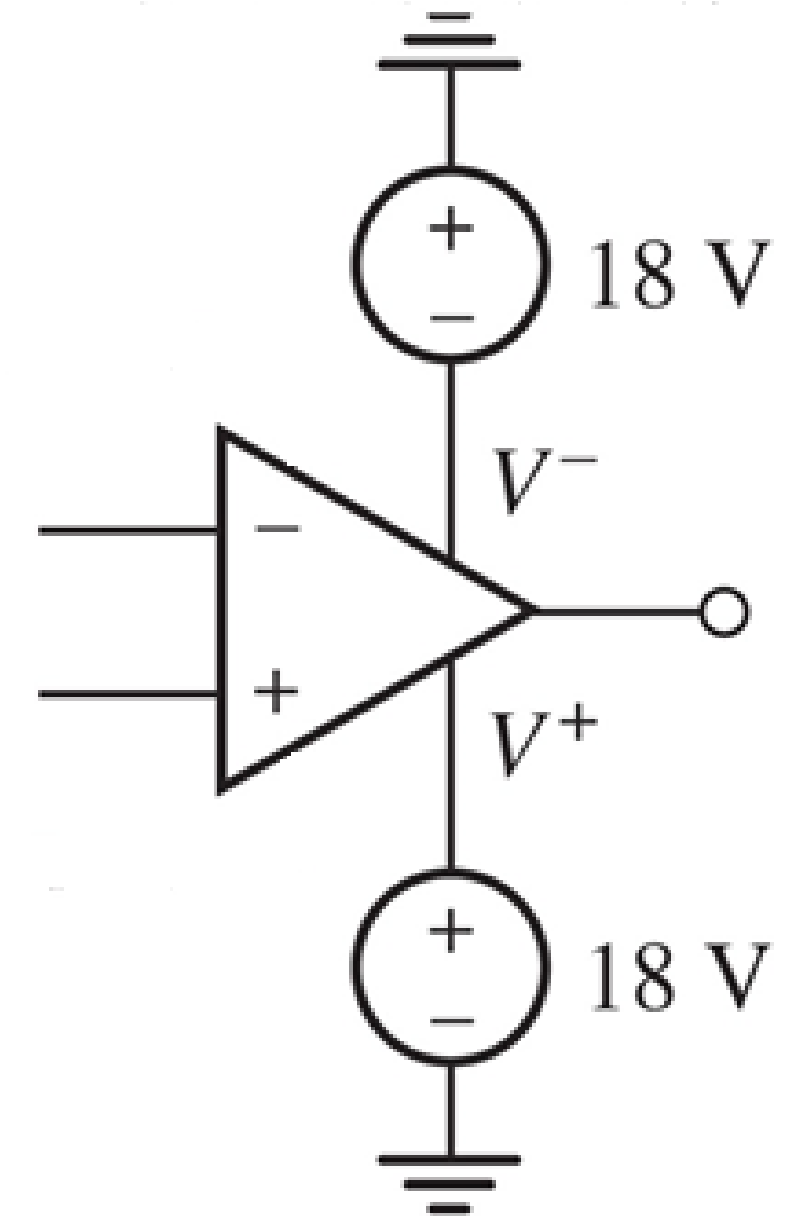

Output Saturation

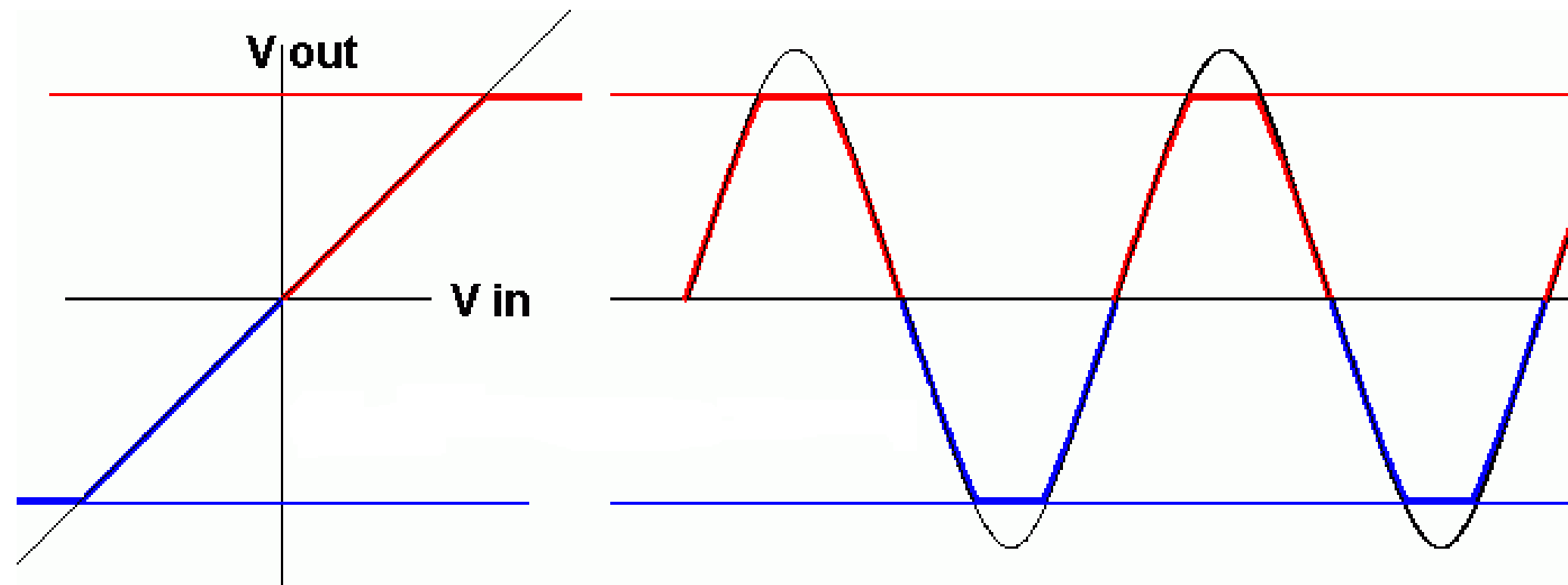- ✓ If the input signal is such that the amplified output exceeds V^+ or falls below V^- , the output will saturate.
- ✓ In this state, the output voltage remains clamped at V^+ or V^- , depending on the direction of the input signal.



The output signal enters saturation and becomes clipped


Role of Negative Feedback

- The role of negative feedback is to transform a large and undefined gain into a fixed, controlled gain.

- Why Don't We Apply Feedback to the Positive Terminal?

$$v_+ \uparrow \rightarrow v_d \uparrow \xrightarrow{v_{out} = Av_d} v_{out} \uparrow \rightarrow v_- \uparrow \rightarrow v_d \downarrow \dots$$


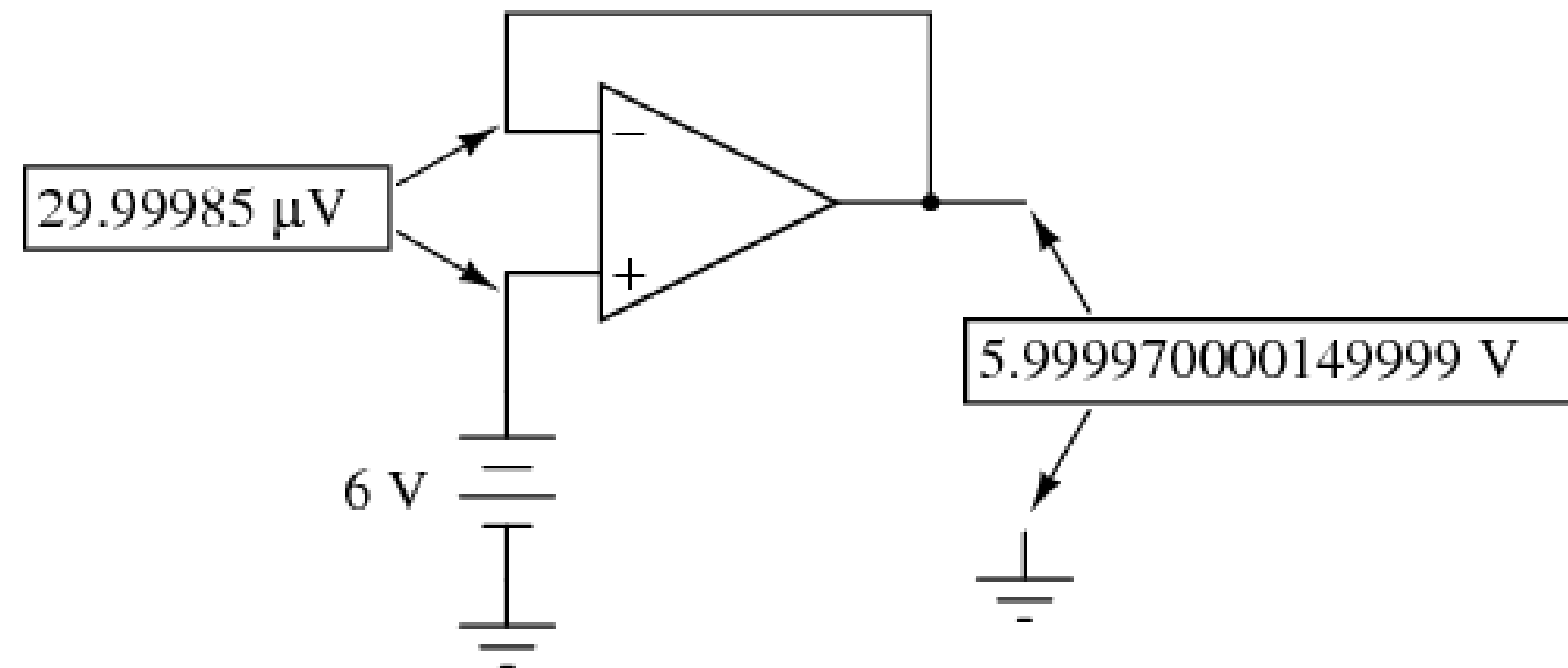
- Thus, the negative feedback stabilizes the operation by keeping v_d close to zero



Voltage Comparator


- An operational amplifier can be used as a voltage comparator when operated in open-loop configuration (without feedback).
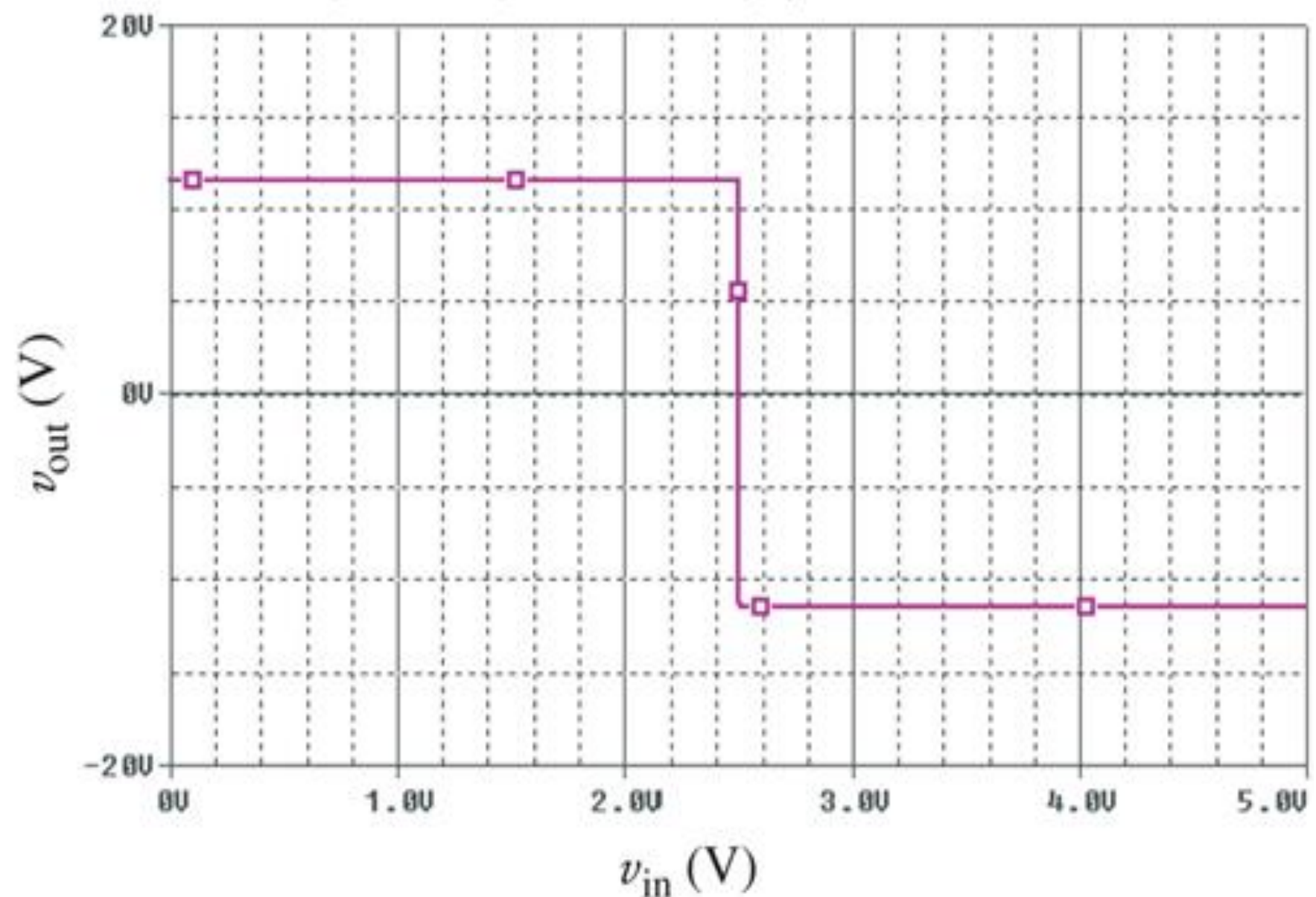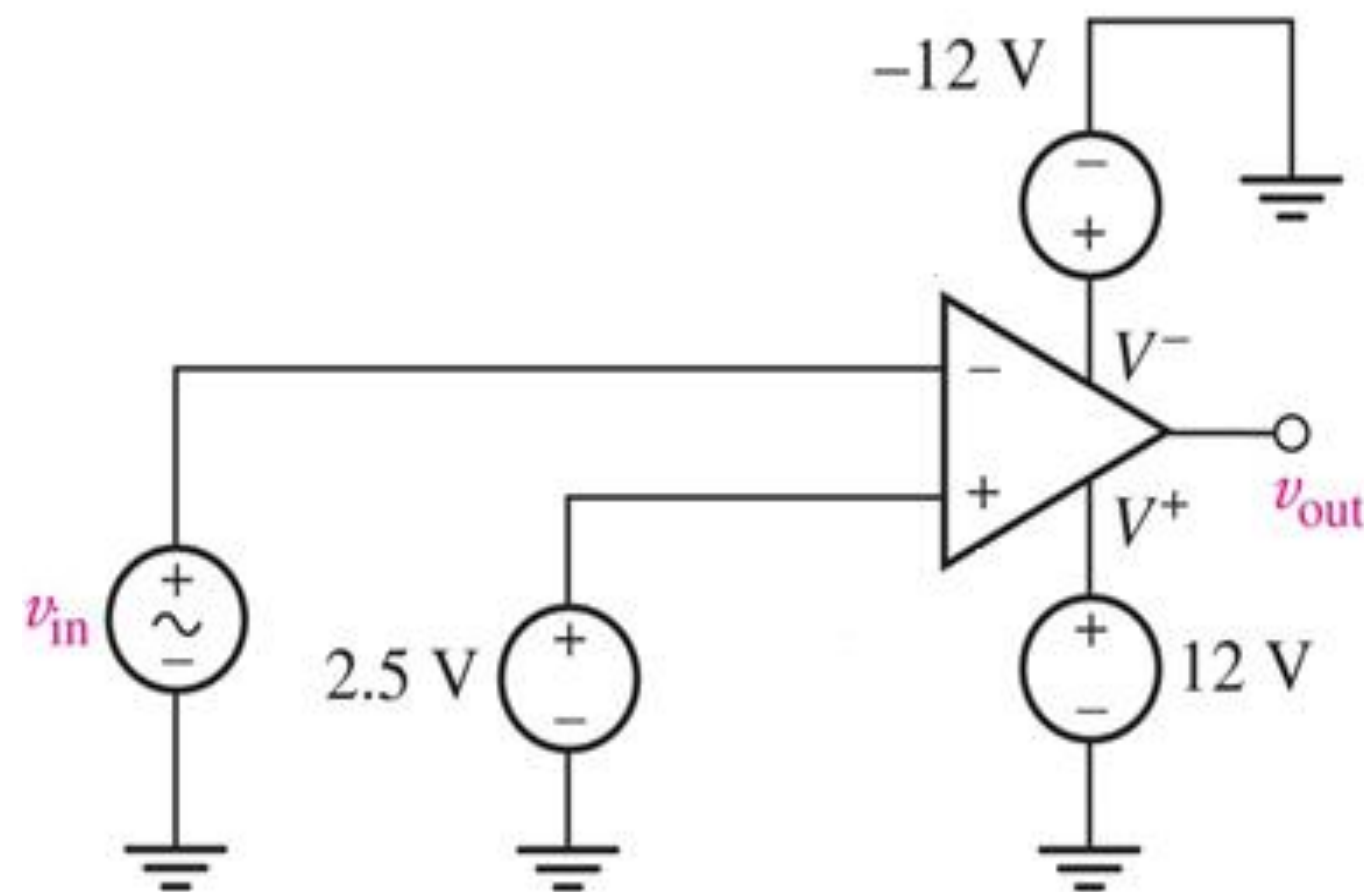
$$v_{out} = \begin{cases} 12 & v_{in} < 2.5 \\ -12 & v_{in} > 2.5 \end{cases}$$





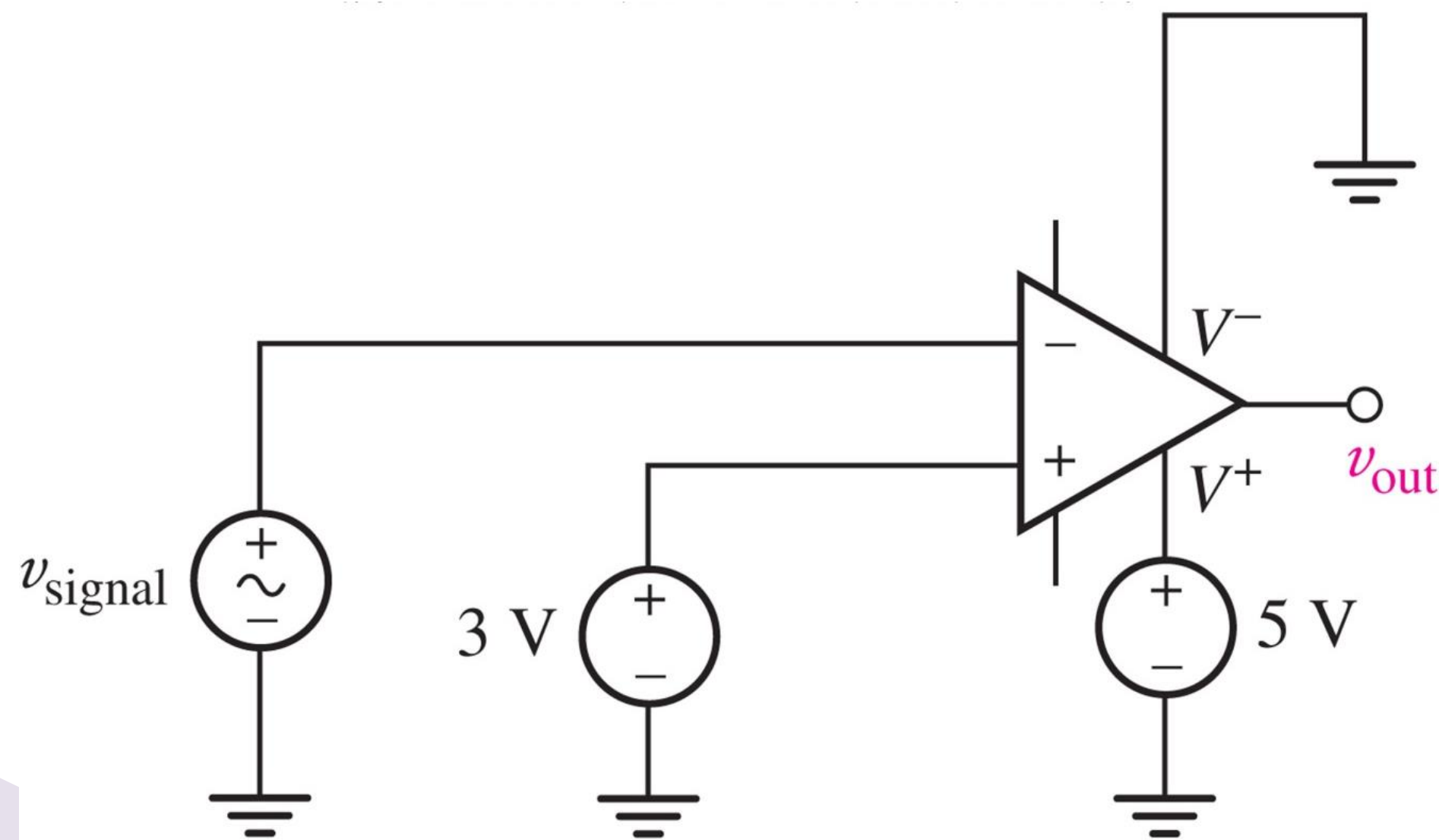Example



Assume we have a temperature sensor that generates a voltage ranging from 0 to 5 volts for temperatures between 0 and 100 degrees Celsius. Design a circuit that provides a logical output of 1 when the temperature is below 60 degrees.



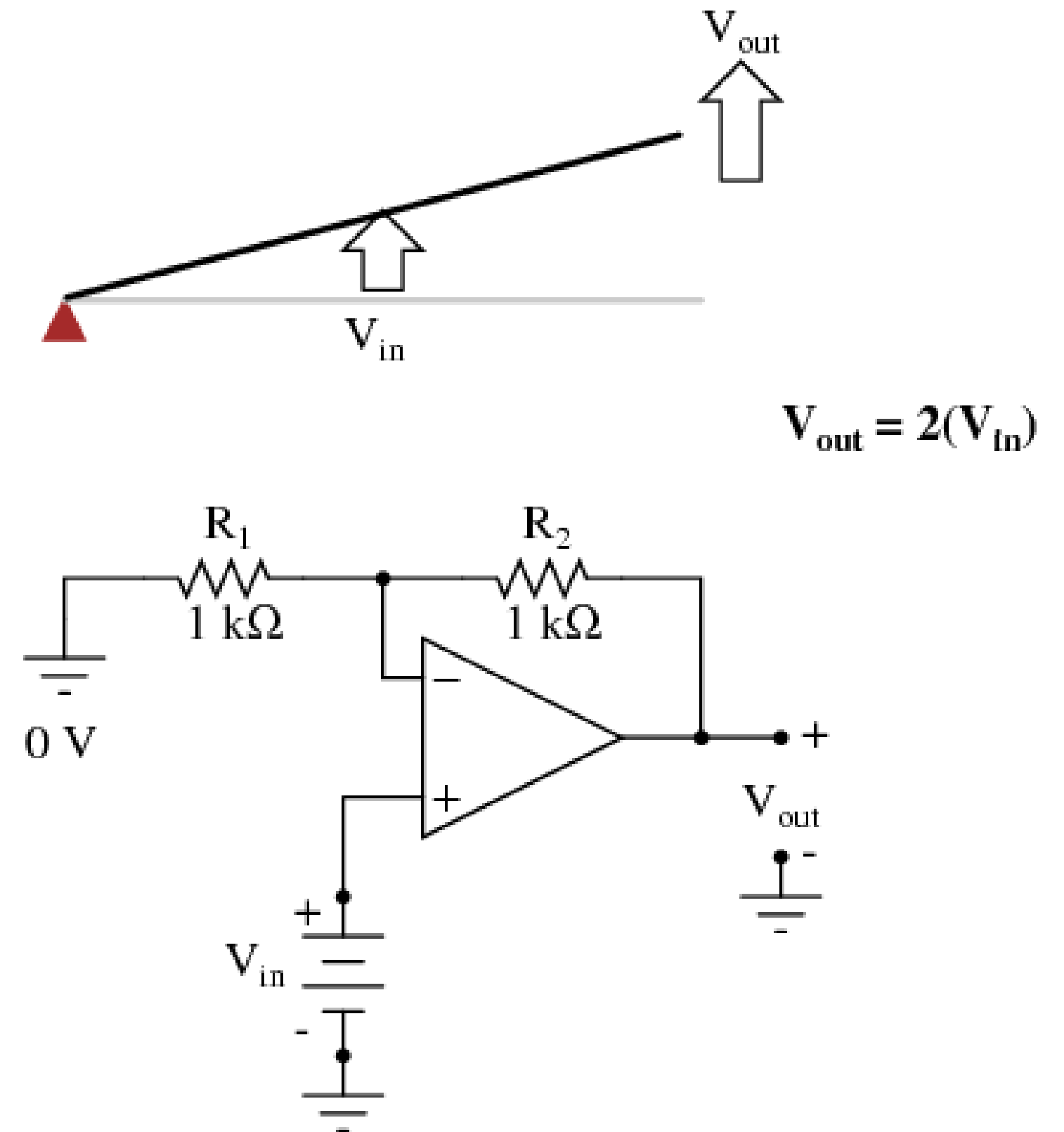
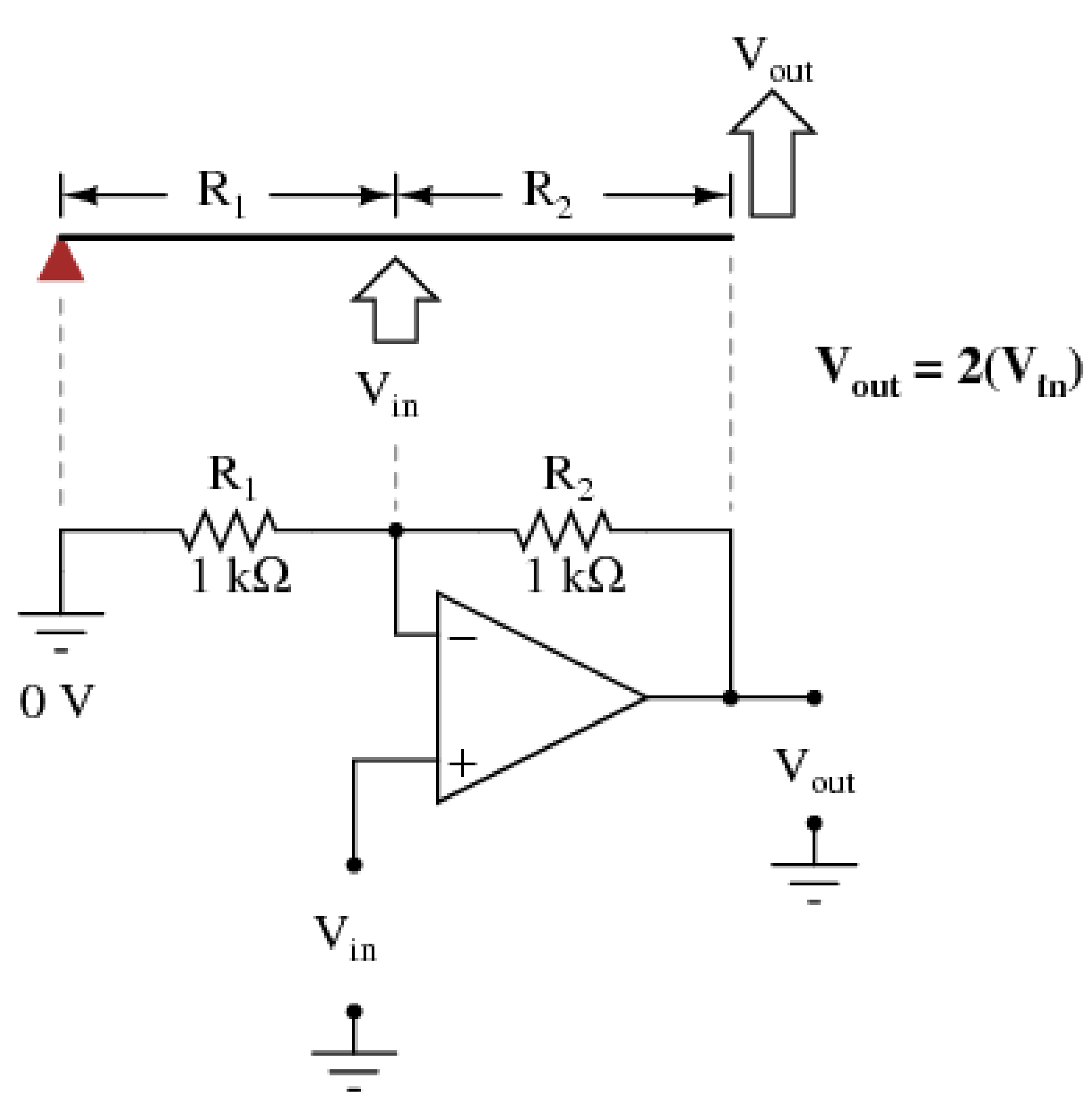
Similarity of Non-Inverting Amplifier to a Lever



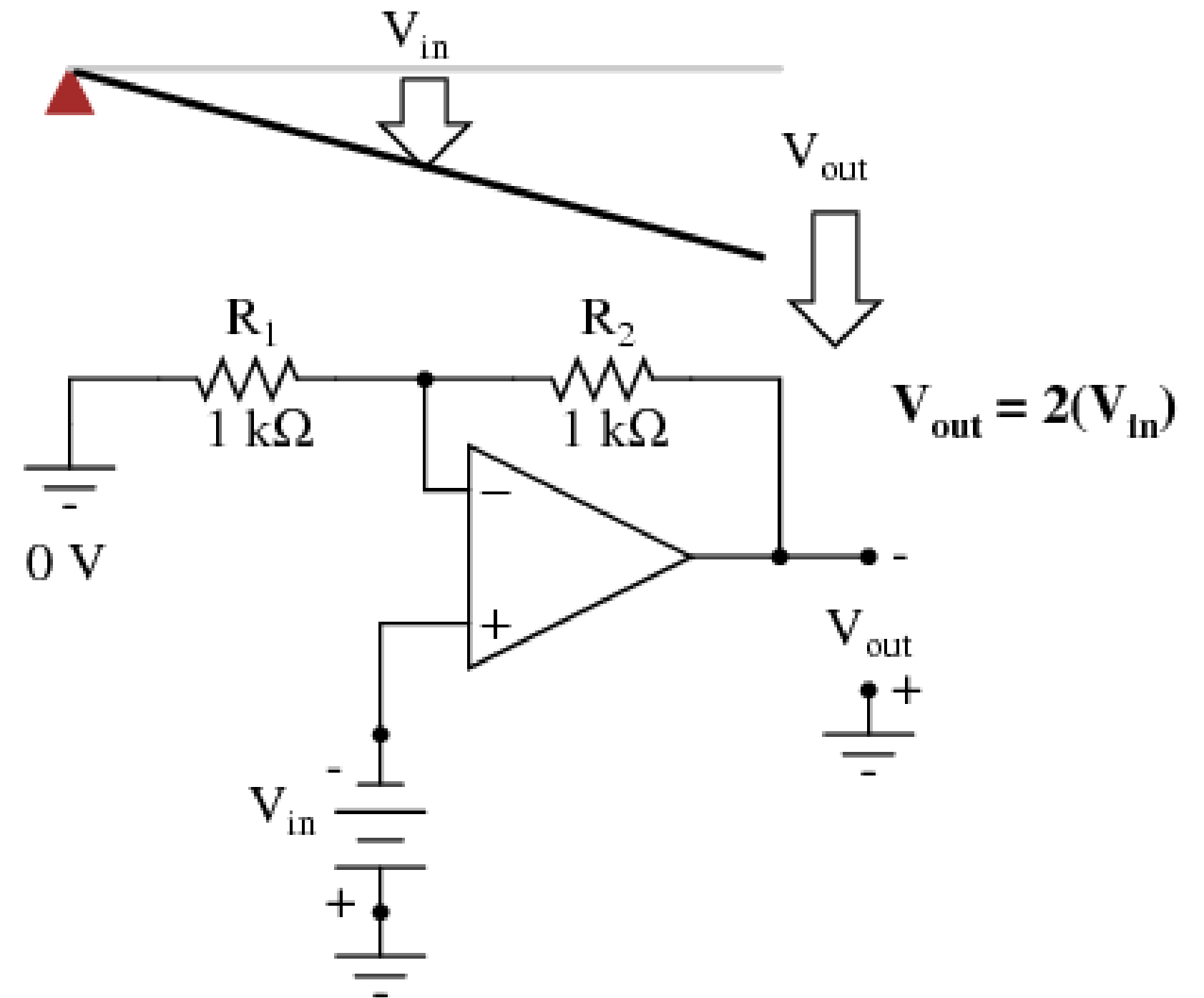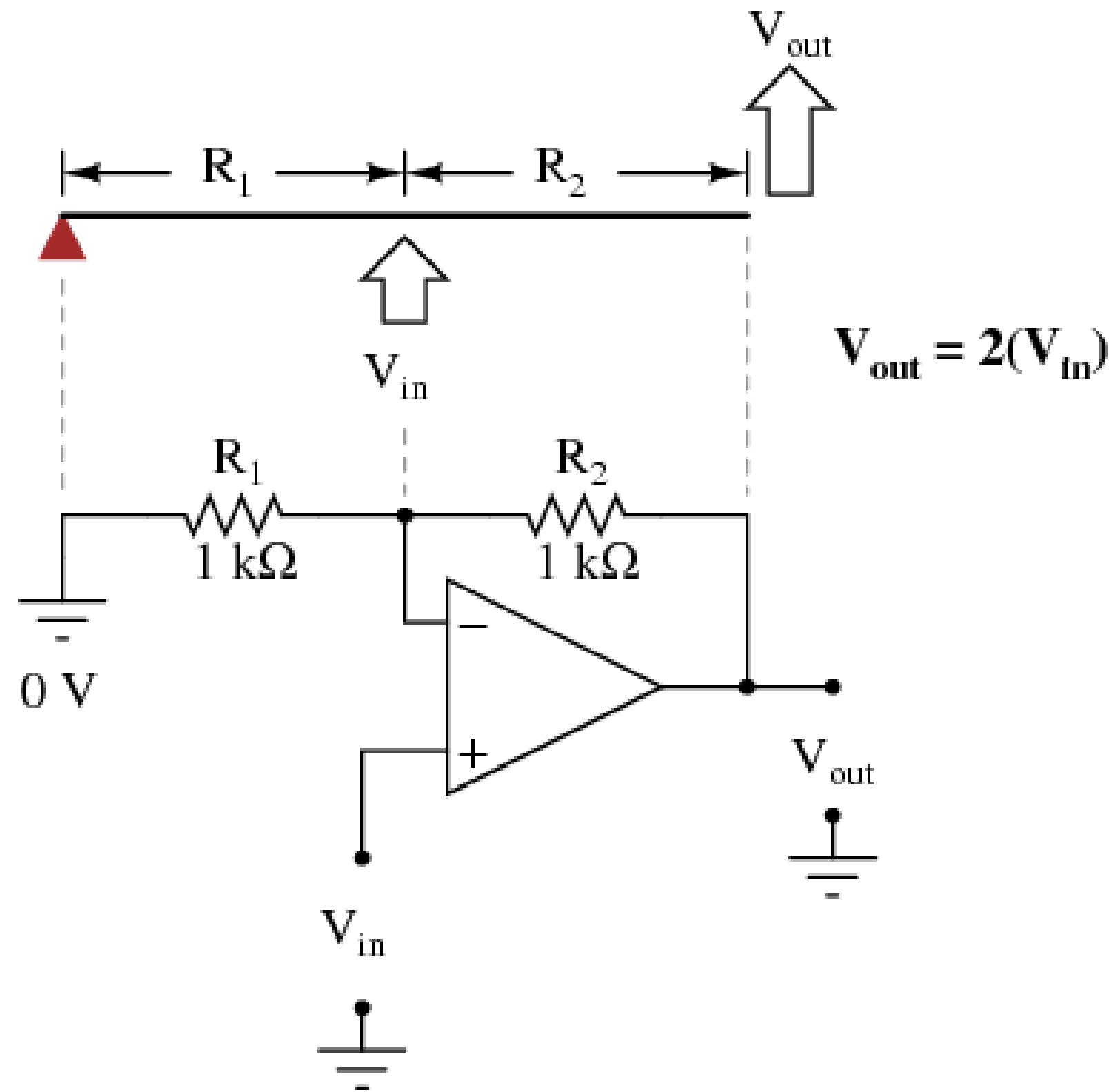Similarity of Non-Inverting Amplifier to a Lever




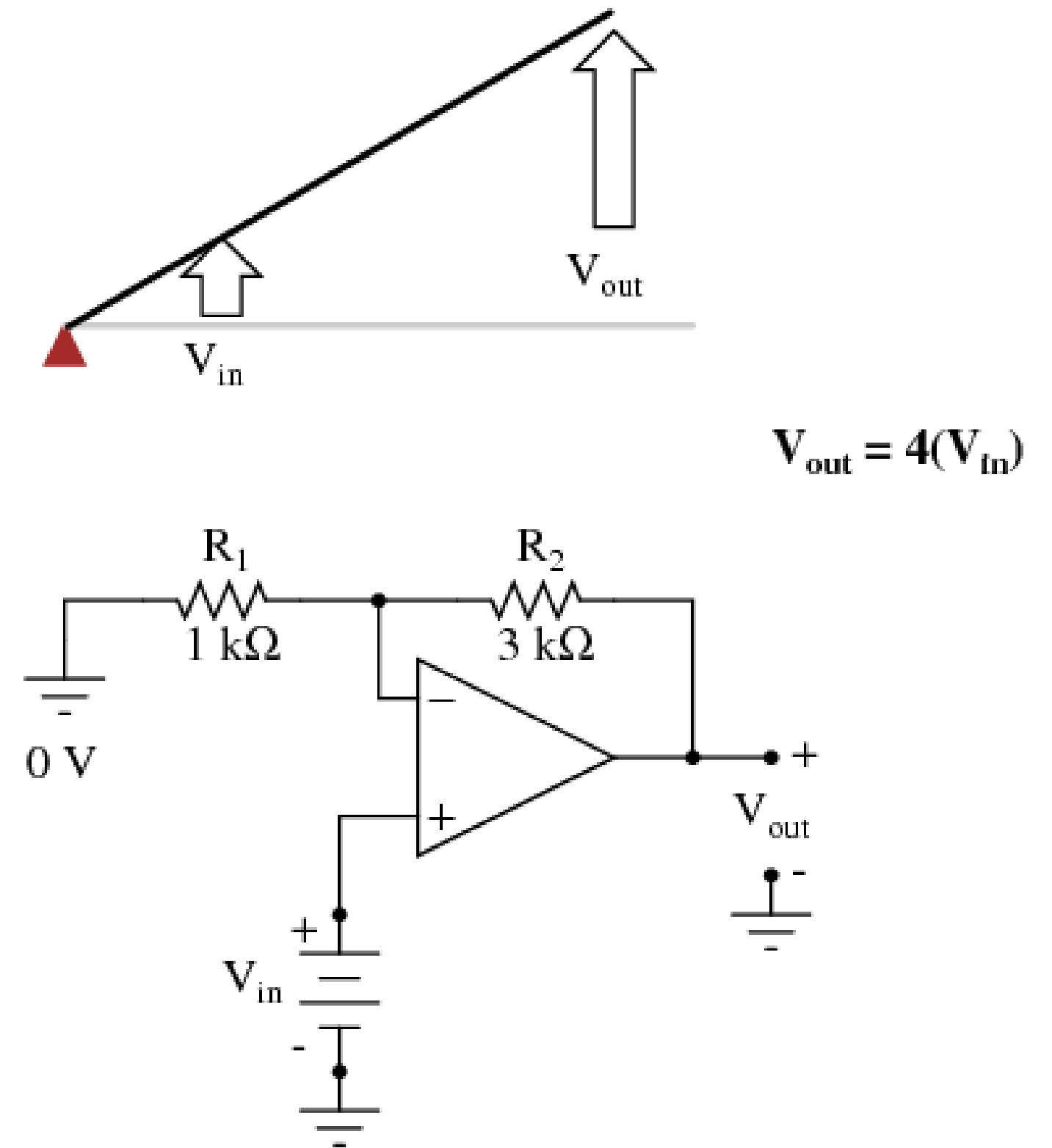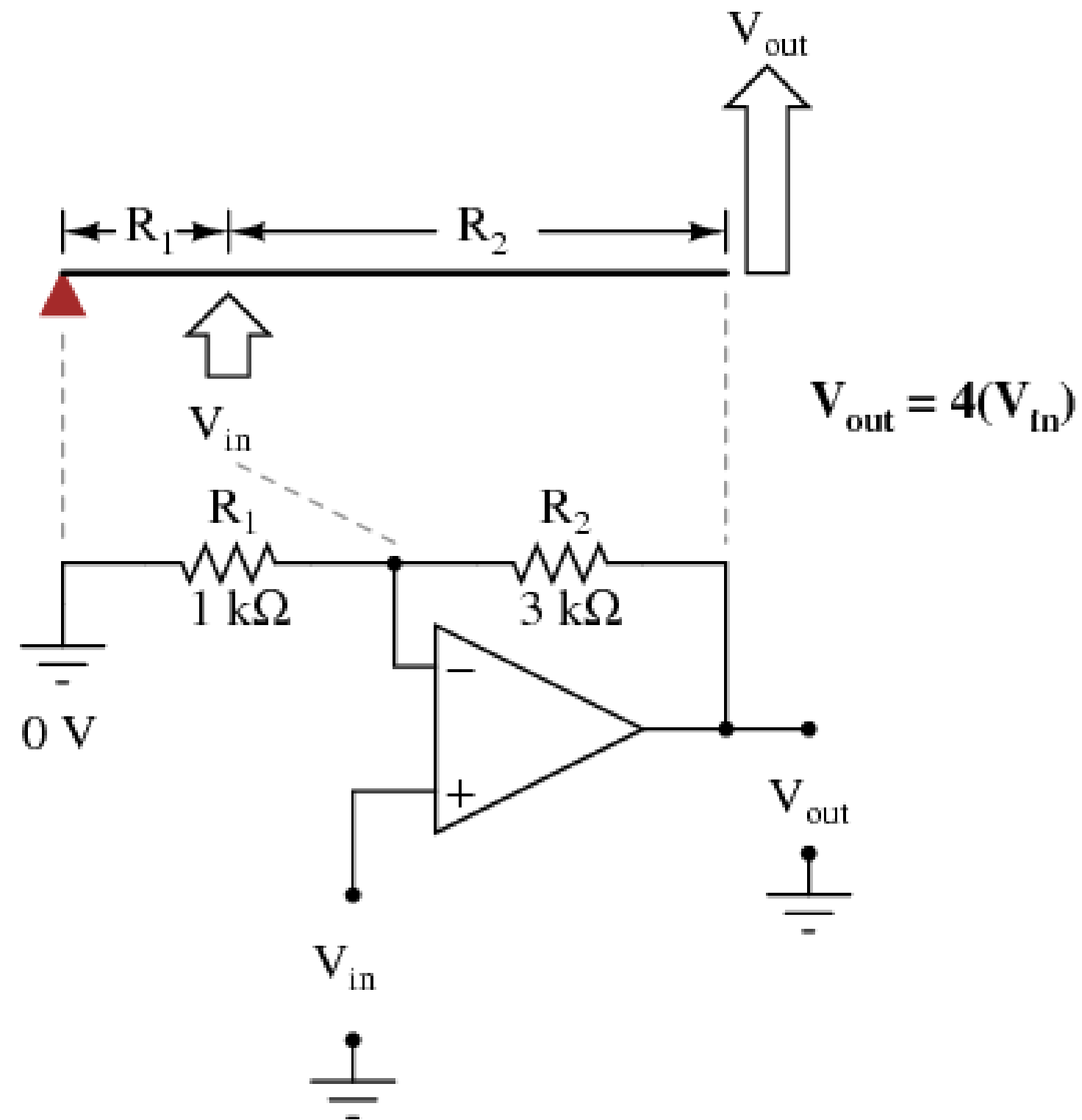
Similarity of Non-Inverting Amplifier to a Lever



Class Exercise 1

$$V_1 = ?$$

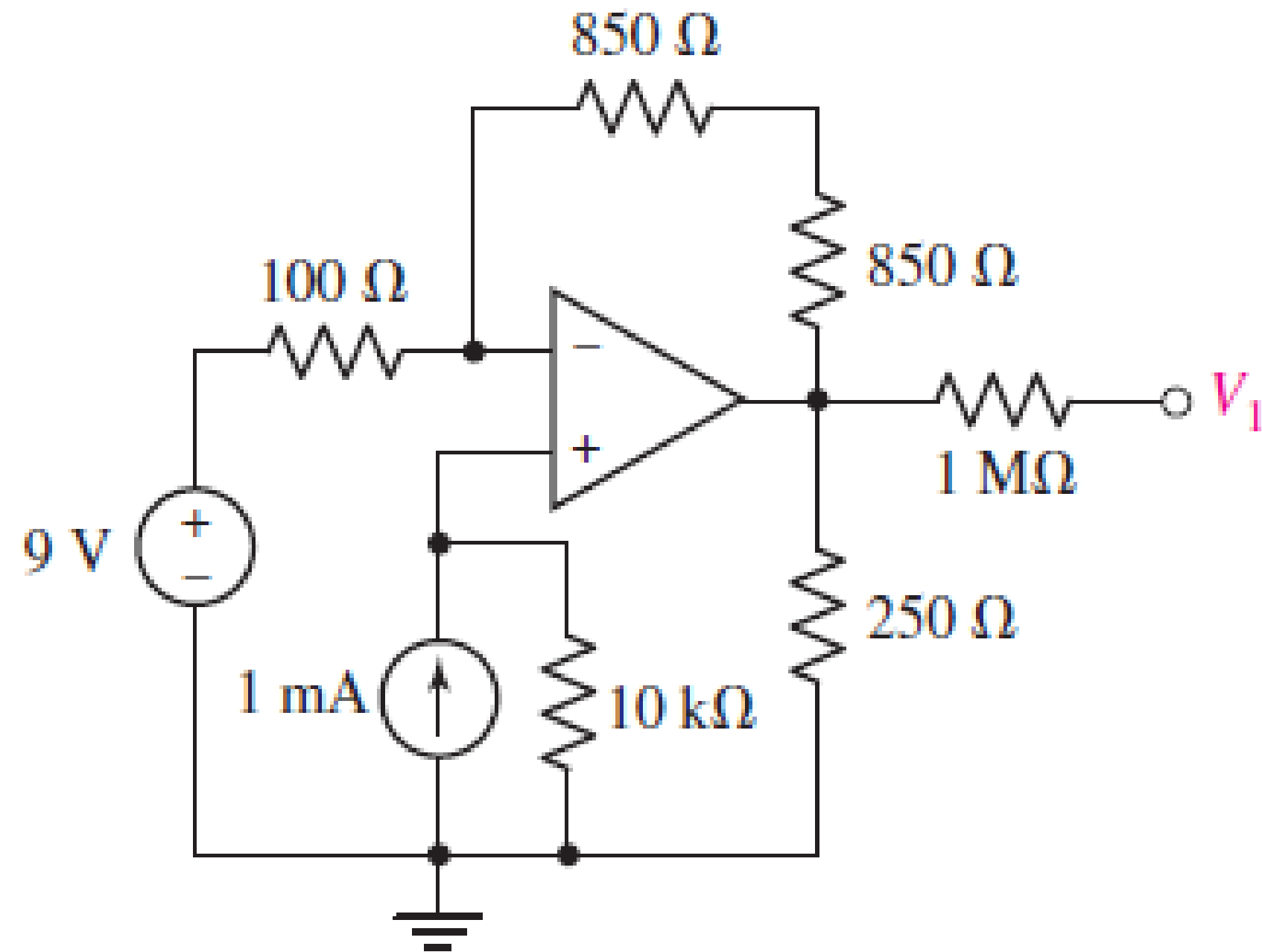

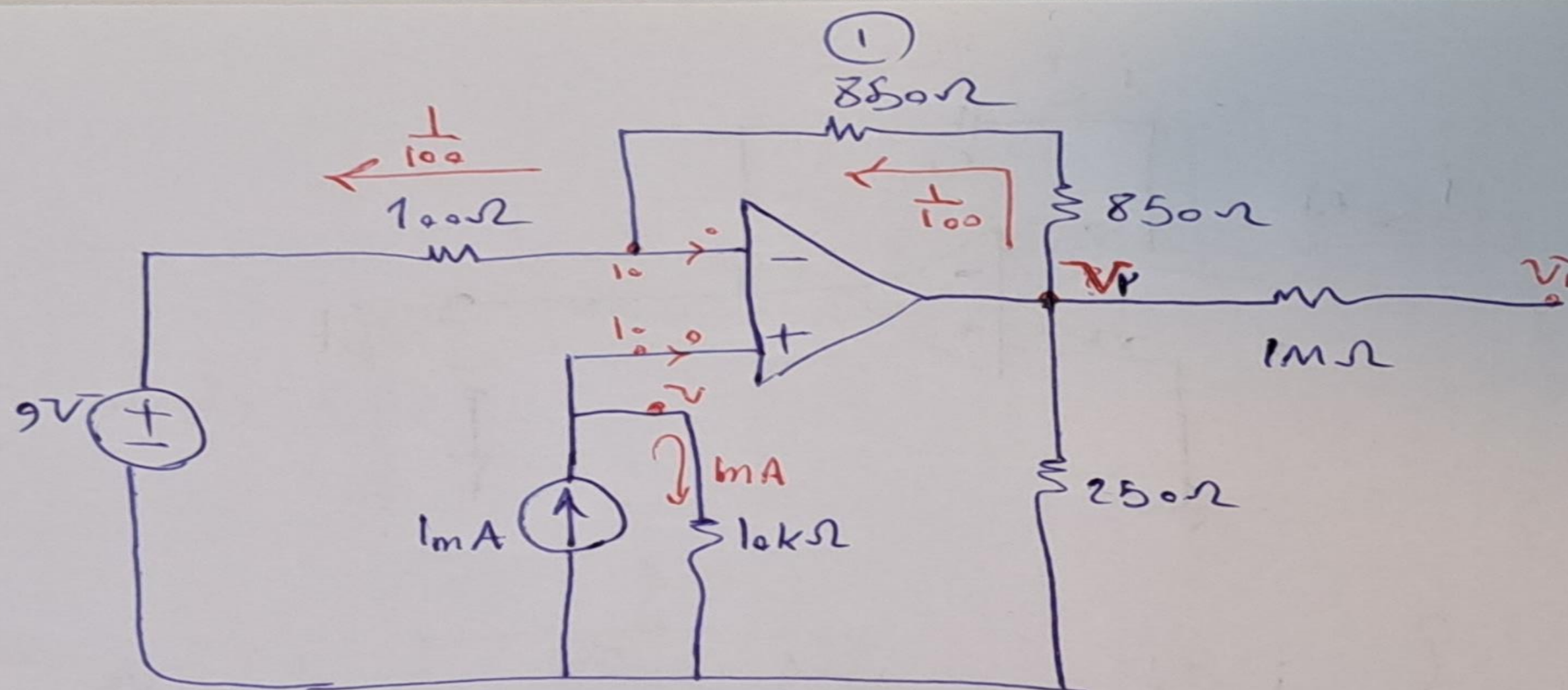


$$V = 10k \times 1m = 10V$$

$$\frac{V_2 - 10}{1700} = \frac{1}{100} \Rightarrow V_2 - 10 = 17 \Rightarrow V_2 = 27V$$


چونکه V_1 روی حسواسه و هیچ بریانه از آن عبور نمی کنه $V_1 = V_2$ و برابر $27V$ افتاده.

Class Exercise 2

$V_{out} = ?$

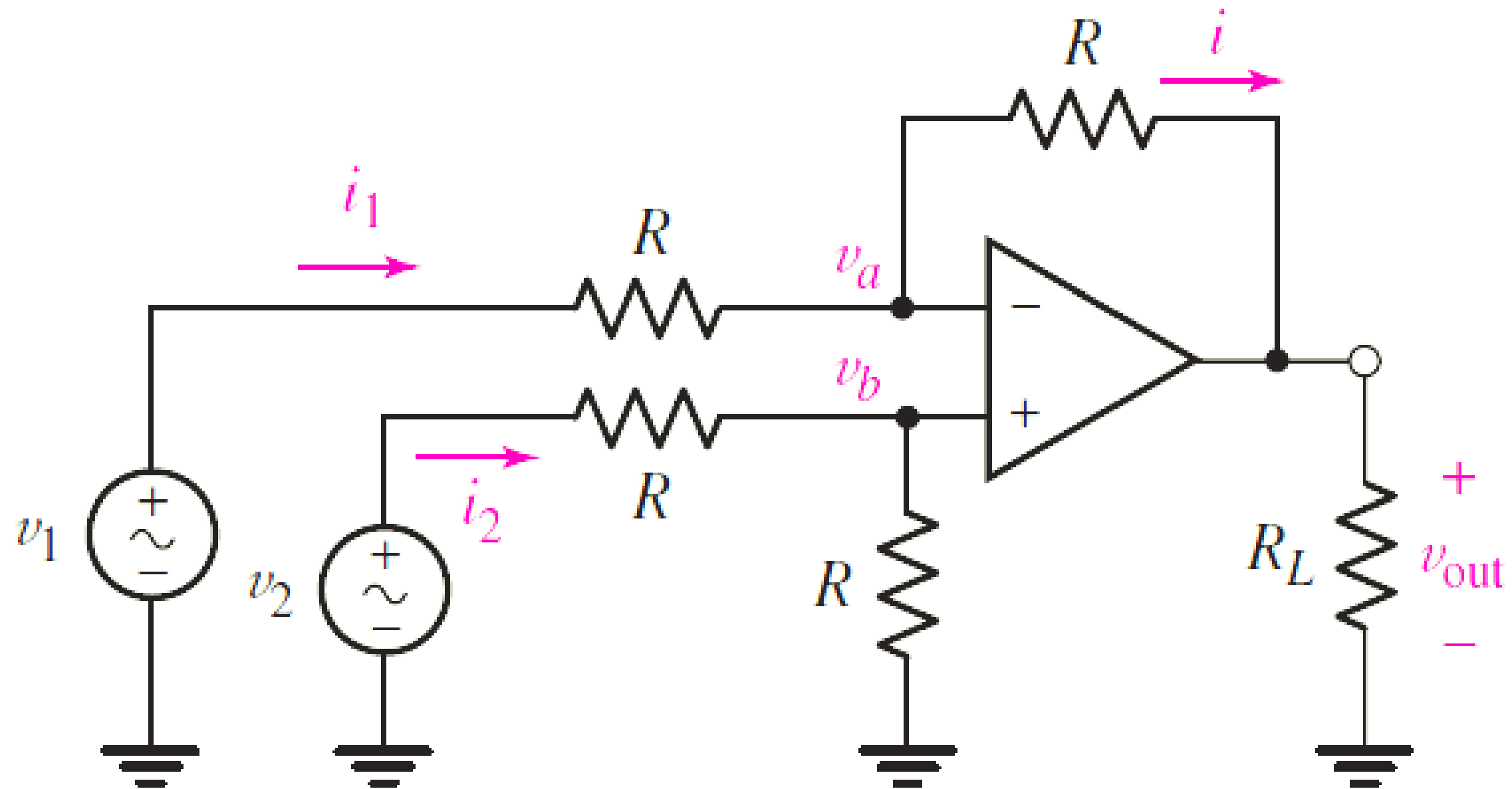

۷

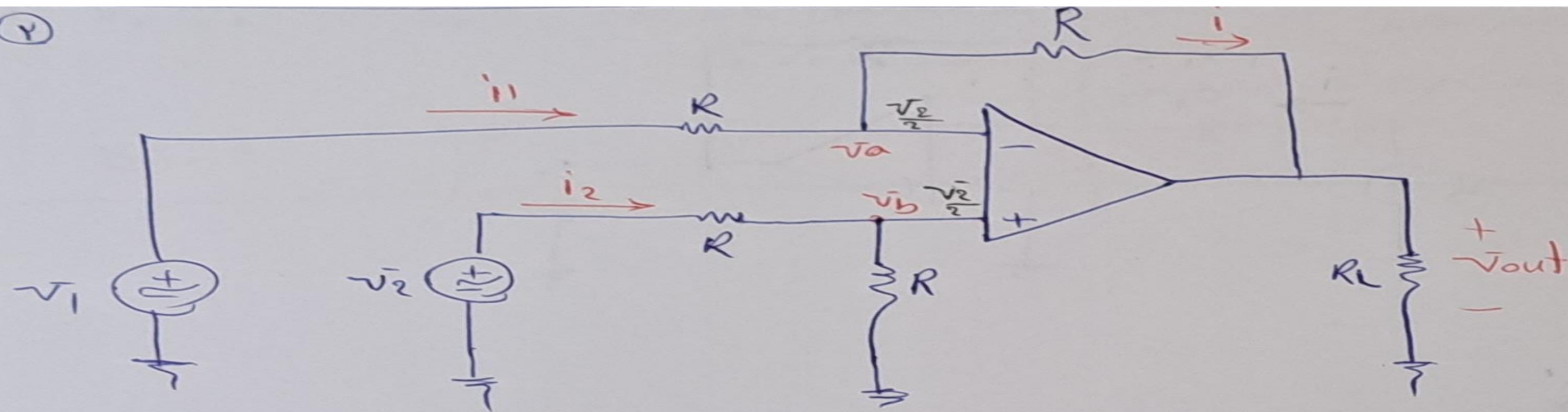

تقسیم ولتاژ بین دو تا R

$$V_b = \frac{V_2}{2}$$

$$i_1 = \frac{V_1 - \frac{V_2}{2}}{R}$$

$$i_1 = i = \frac{\frac{V_2}{2} - V_{out}}{R}$$


$$\frac{V_1 - \frac{V_2}{2}}{R} = \frac{\frac{V_2}{2} - V_{out}}{R}$$

$$V_{out} = V_1 - V_2$$

۱

Class Exercise 3


$V_{out} = ?$

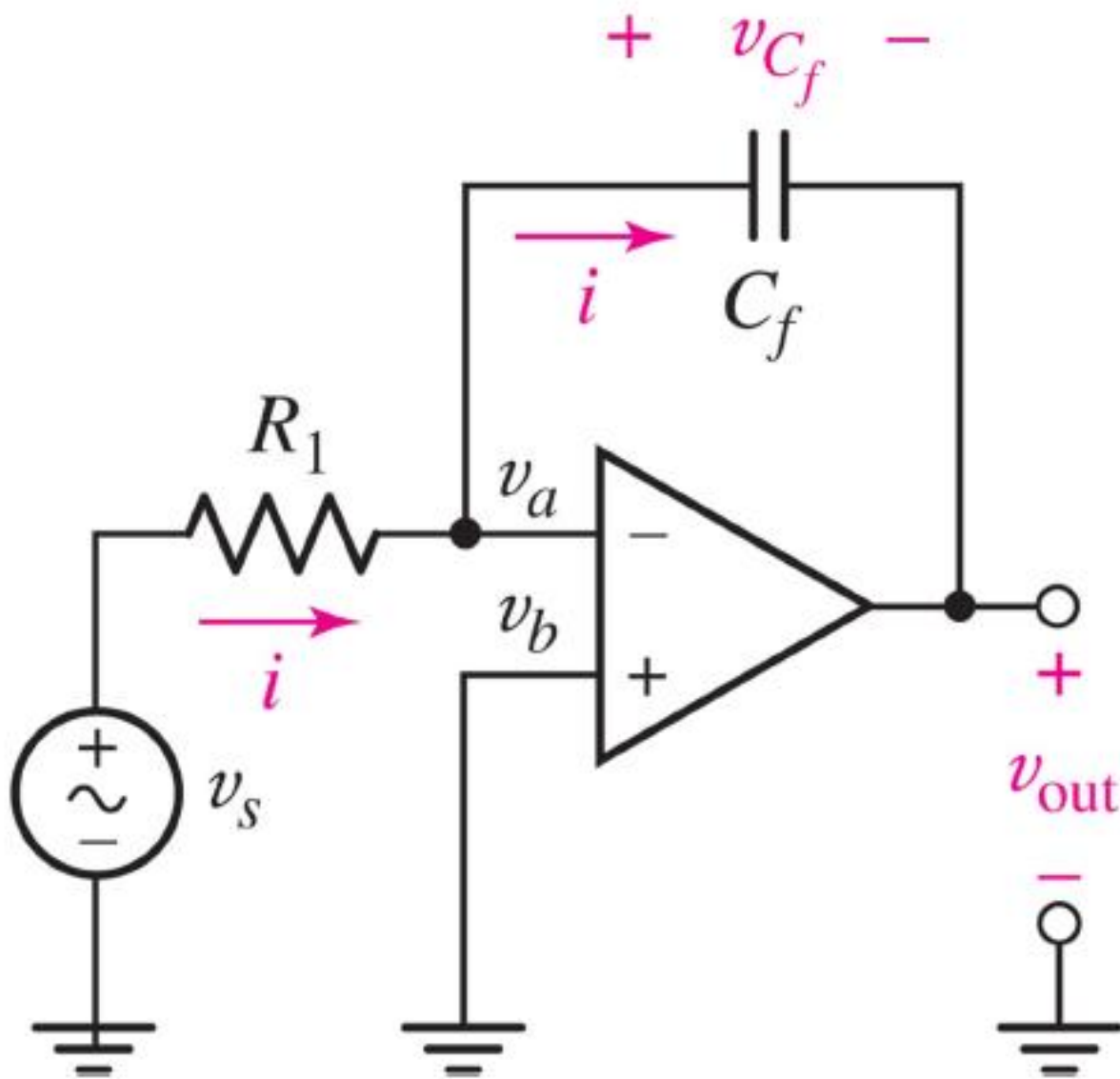

$$v_{out} = -\frac{1}{R_1 C_f} \int_0^t v_s dt' - v_{C_f}(0)$$

۳

مدار انتگرال گیر

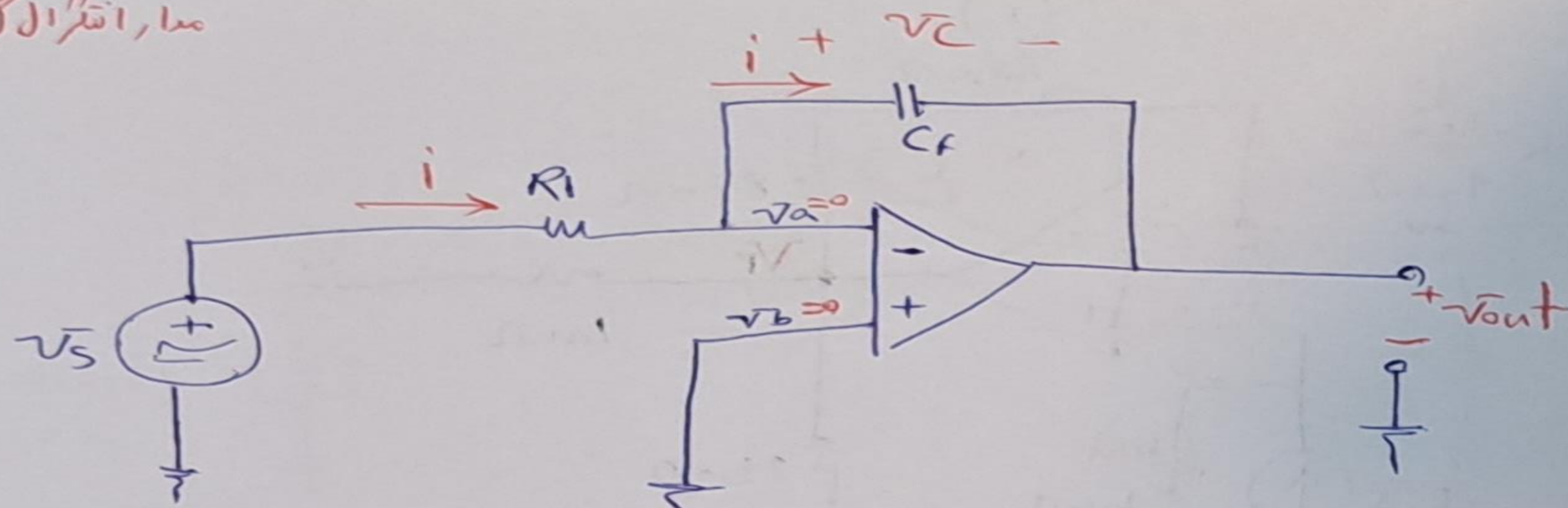

$$i = \frac{v_s}{R_1}$$

جریان خازن

$$i = C_f \frac{dv_c}{dt}$$

$$i = C_f \frac{dv_c}{dt} \Rightarrow \frac{dv_c}{dt} = \frac{i}{C_f}$$

$$\frac{dv_c}{dt} = \frac{v_s}{R_1 C_f}$$


$$v_c = \frac{1}{C_f} \int i dt + v_c(0^+)$$

$$-v_{out} - v_c = 0 \Rightarrow v_{out} = -v_c$$


$$v_{out} = -\frac{1}{C_f} \int \frac{v_s}{R_1} dt - v_c(0^+) = -\frac{1}{R_1 C_f} \int v_s dt - v_c(0^+)$$

Class Exercise 4

$V_{out} = ?$

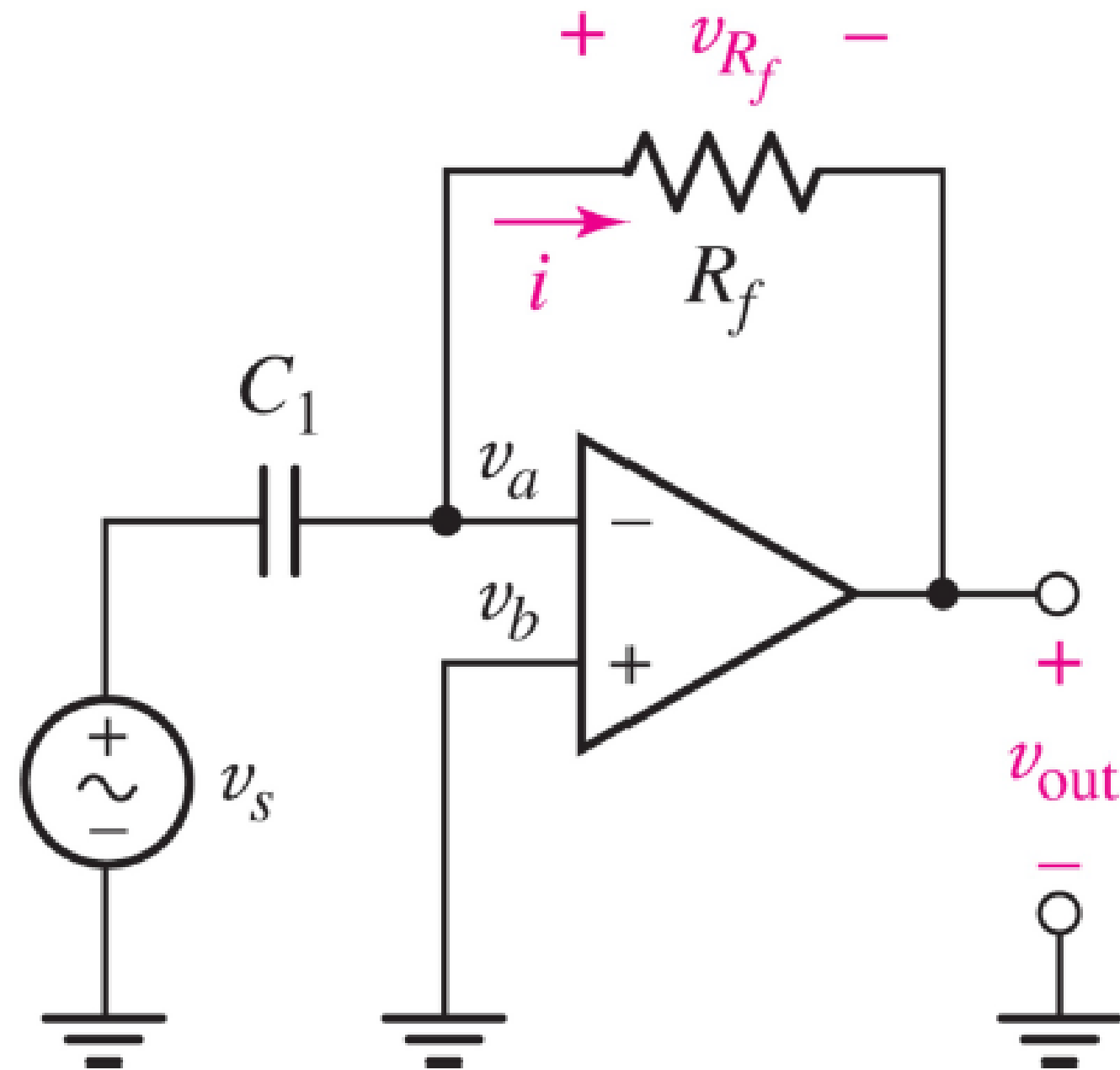

$$v_{out} = -C_1 R_f \frac{dv_s}{dt}$$

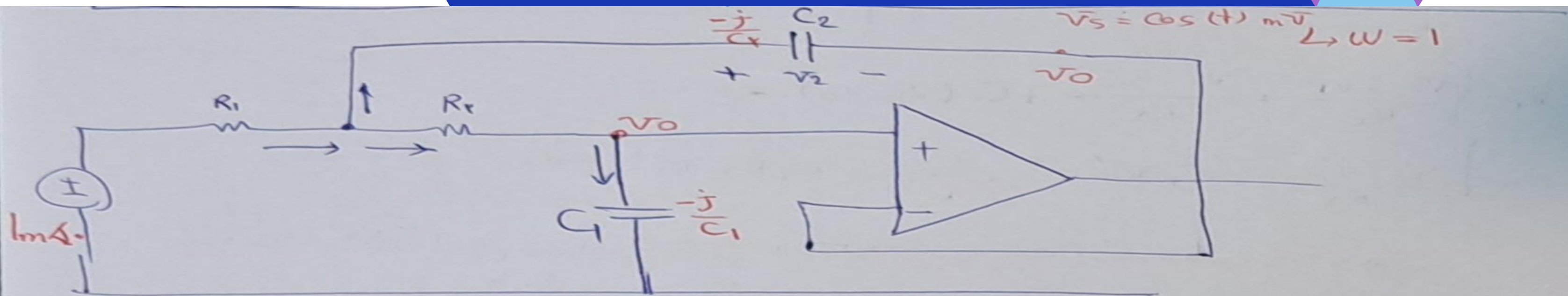

$$KCL V_1: \begin{cases} \frac{1m - V_1}{R_1} + \frac{V_1 - V_0}{R_2} + \frac{V_1 - V_0}{-j/C_2} \\ \frac{V_1 - V_0}{R_2} = \frac{V_0}{-j/C_1} \end{cases}$$

با استفاده از این معادله می توان V_1 را حذف کرد \Rightarrow


با جایگذاری در رابطه دوم می توان V_0 را به حسب معادله ثابت بدست آورد.

V_0 یک عدد مختلط \leftarrow که باید به حوزه زمان برده شود.


$$Ae^{j\theta} \longrightarrow A \cos(t + \theta)$$

Class Exercise 5



$$v_x = ?$$

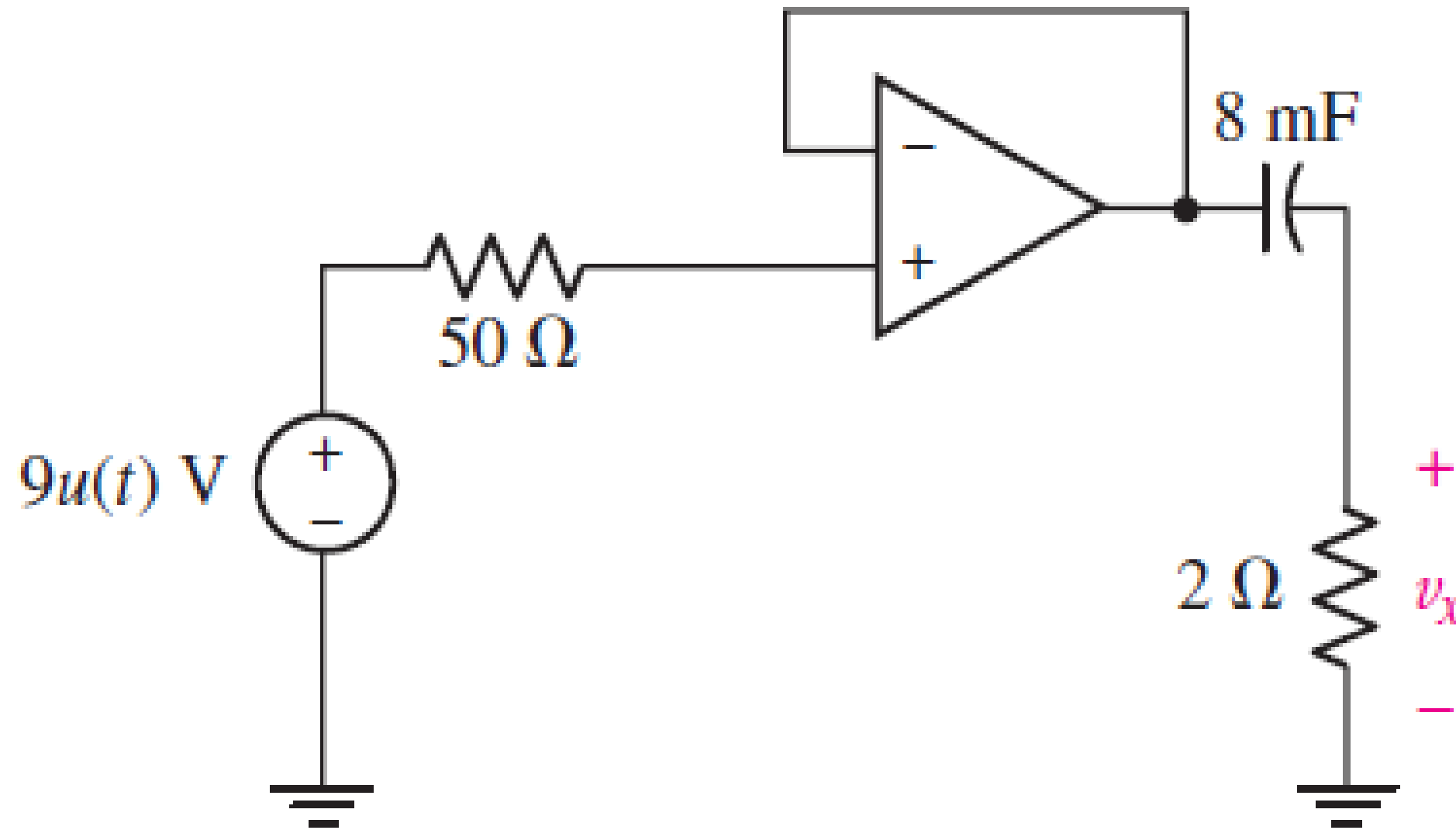

سؤال ۵

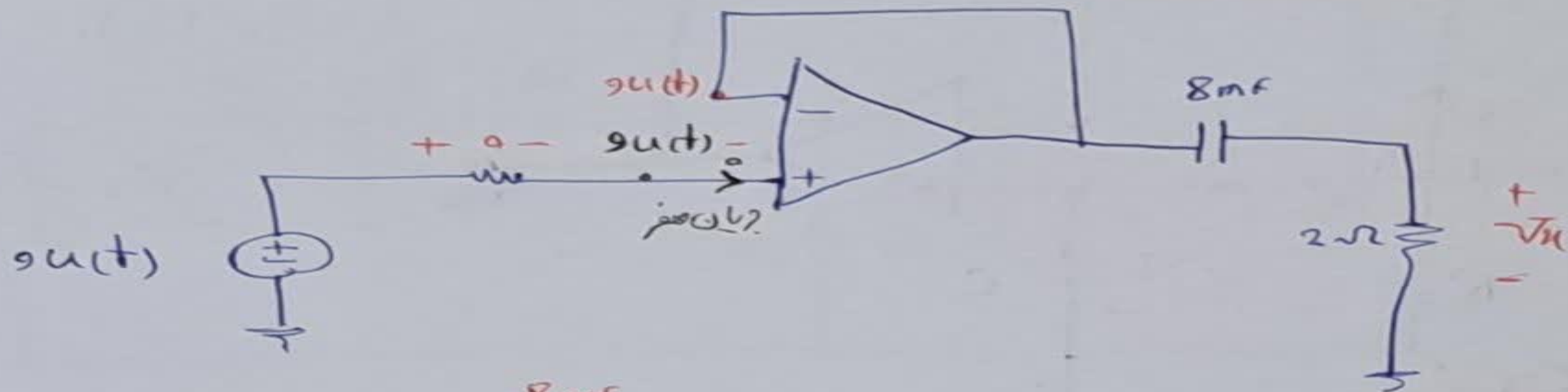

معادل زینر

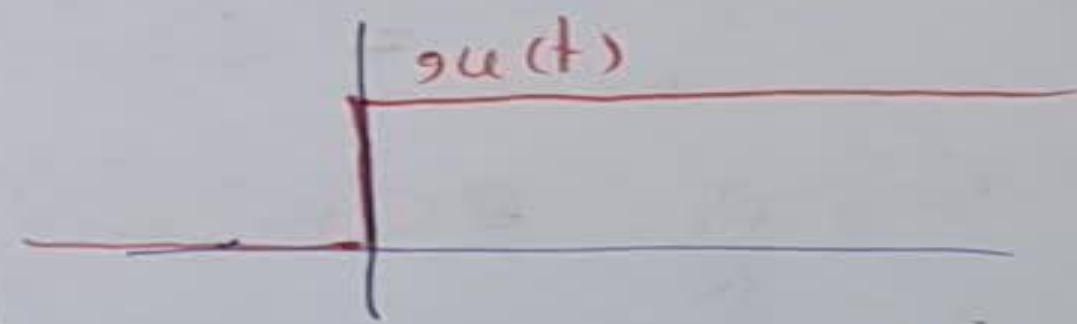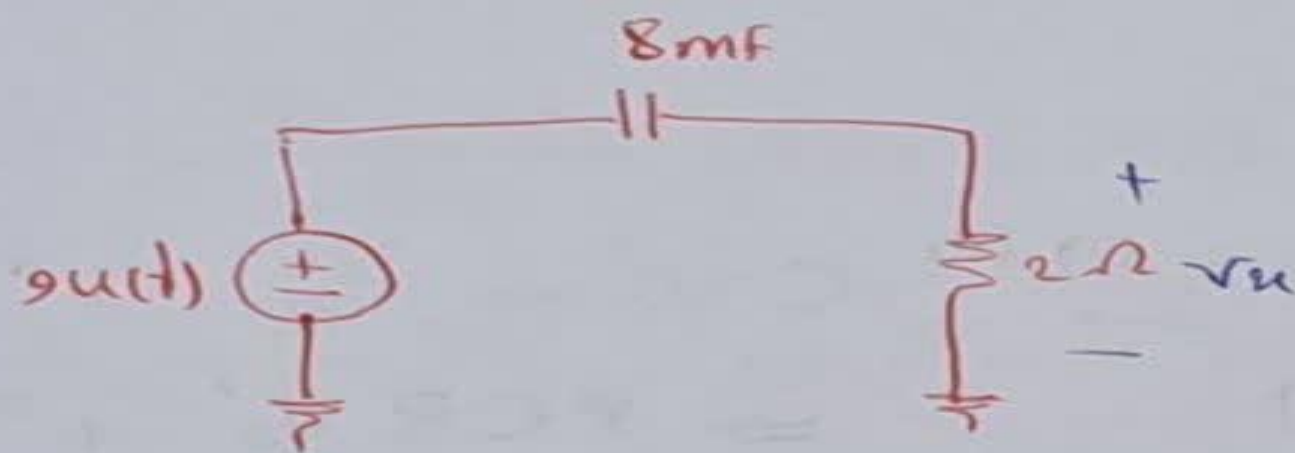

$$v_u = \cancel{v_\infty} + (\cancel{v_c} - \cancel{v_\infty}) e^{-\frac{t}{16m}} = 9e^{-\frac{t}{16m}}$$

در لحظه صفر متغیر v_c در مدار است، در نتیجه $v_c(0) = 0$


$v_c(-) = v_c(+)$ و در دو صفر هستند

در نتیجه در لحظه صفر میست ۹- روی دو سه مقاومت است

و لذا دو هم خازن مدار باز شده
در نتیجه $v_\infty = 0$
 $v_\infty = 0$
 $v_u(t) = 9$

Class Exercise 6

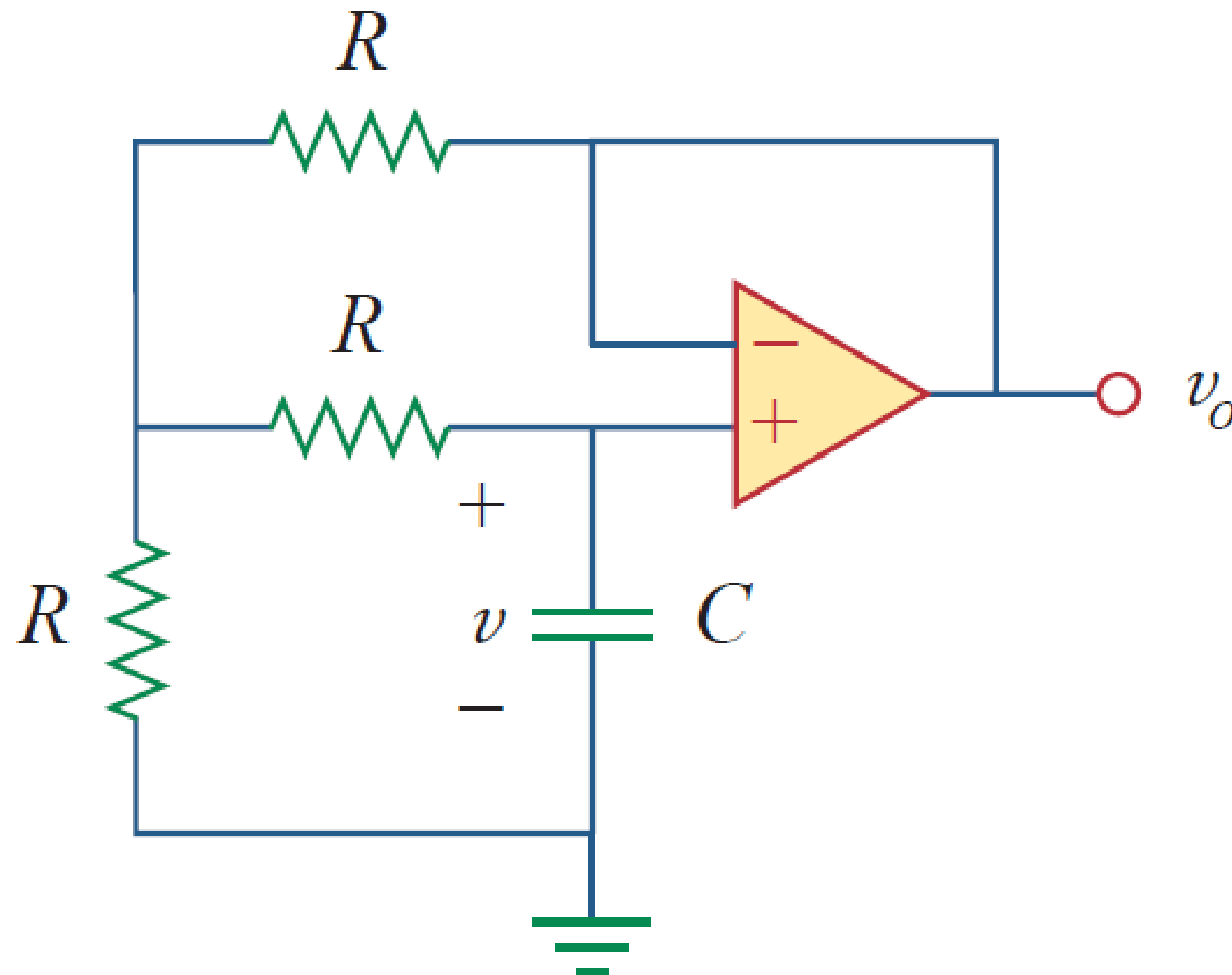
If the initial voltage across the capacitor at time $t = 0$ is 10 volts, determine the output voltage v_o .



سؤال (6)

اندازه، در لحظه $t=0$ برابر ۱۰ ولت باشد؟

$$V(0^+) = 10 \quad V_0 = ?$$

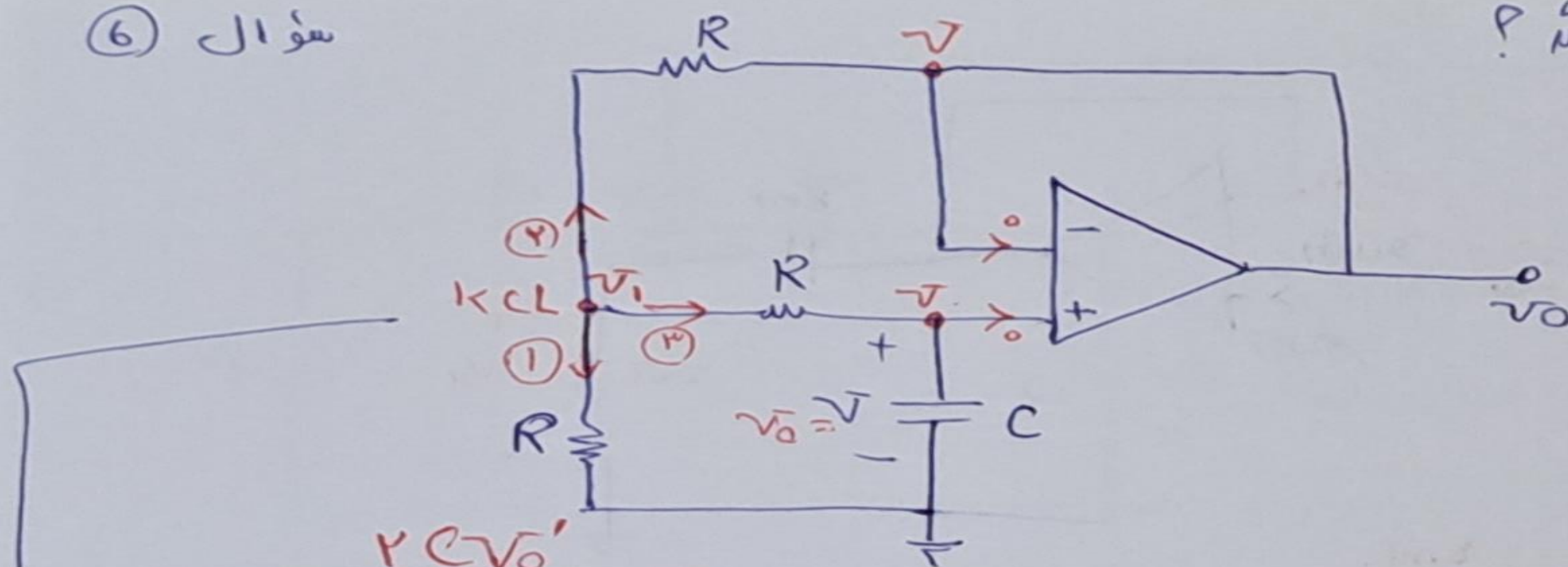

$$V_0 = V$$

$$V_0 - V_0'$$

$$\frac{V_1}{R} + \frac{V_1 - V_0}{R} + \frac{V_1 - V_0}{R} \quad (1)$$

جریان (۳)

$$\frac{V_1 - V_0}{R} = C V_0' \quad (2)$$

$$V_1 = C V_0' + \frac{V_0}{R} \quad (3)$$

(۱) و (۳)

$$C V_0' + \frac{V_0}{R} + 2C V_0' = 0$$

$$\Rightarrow 3CR V_0' + V_0 = 0$$

↓


$$3CRS + 1 = 0 \Rightarrow S = \frac{-1}{3RC}$$

$$\Rightarrow V_0 = 10 e^{\frac{-t}{3RC}}$$


Class Exercise 7

➤ $v_s = 10u(t)mV$, $R_1 = R_2 = 10K\Omega$, $C_1 = 20\mu F$, $C_2 = 100\mu F$

➤ $v_o = ?$

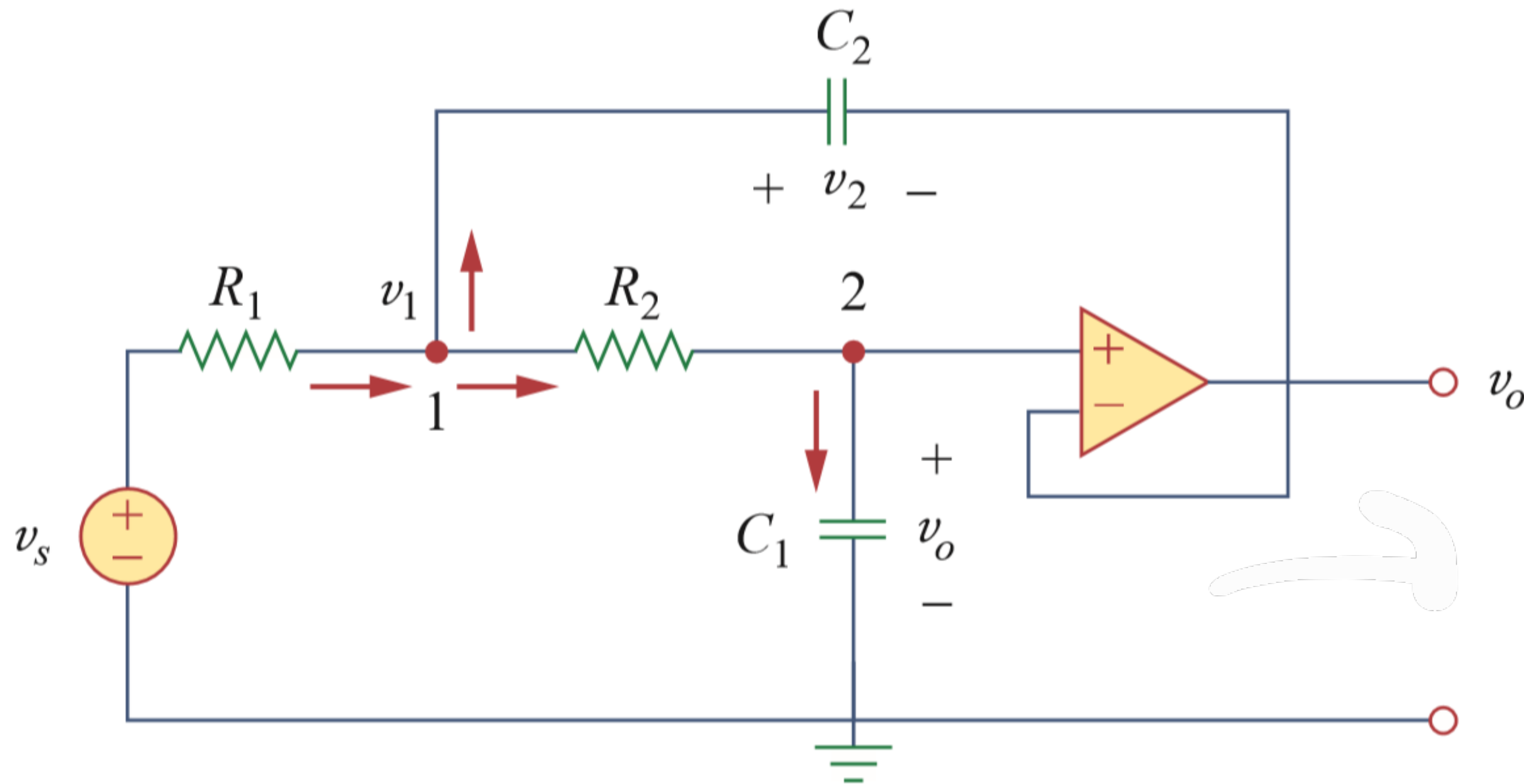

۷

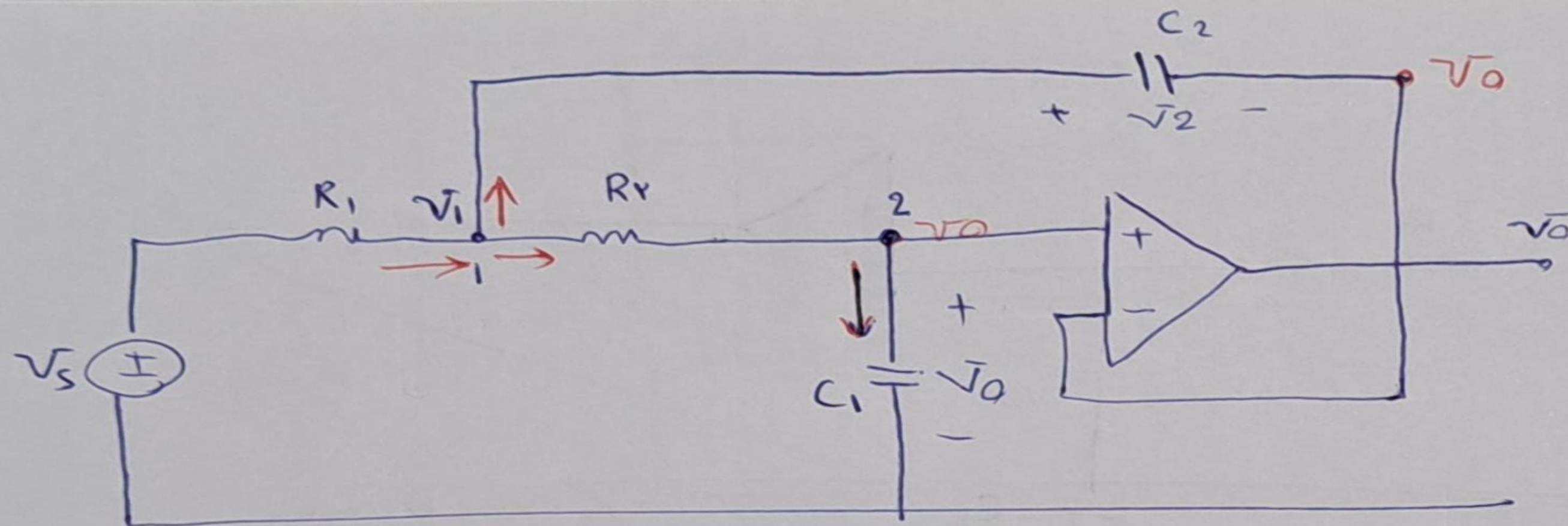


$$\text{KCL } v_1 : \begin{cases} \frac{V_s - v_1}{R_1} + \frac{v_1 - v_o}{R_2} + C_2 (v_1 - v_o)' = 0 \\ \frac{v_1 - v_o}{R_2} = C_1 v_o' \end{cases} \Rightarrow \boxed{v_1 = C_1 R_2 v_o' + v_o}$$

یک دستگاه معادله داریم می توان آنرا حذف کرد و v_o را به حسب v_s نوشت.


↓ ادامه آن مشابه میان دوم ~~میباشد~~ مدار مرتبه دوم پس باید یاد بگیریم مدار مرتبه دوم را چگونه حل کنیم.

Class Exercise 8



- $v_s = \cos(t)mV$, $R_1 = R_2 = 10K\Omega$, $C_1 = 20\mu F$, $C_2 = 100\mu F$
- $v_o = ?$ (Use phasors).

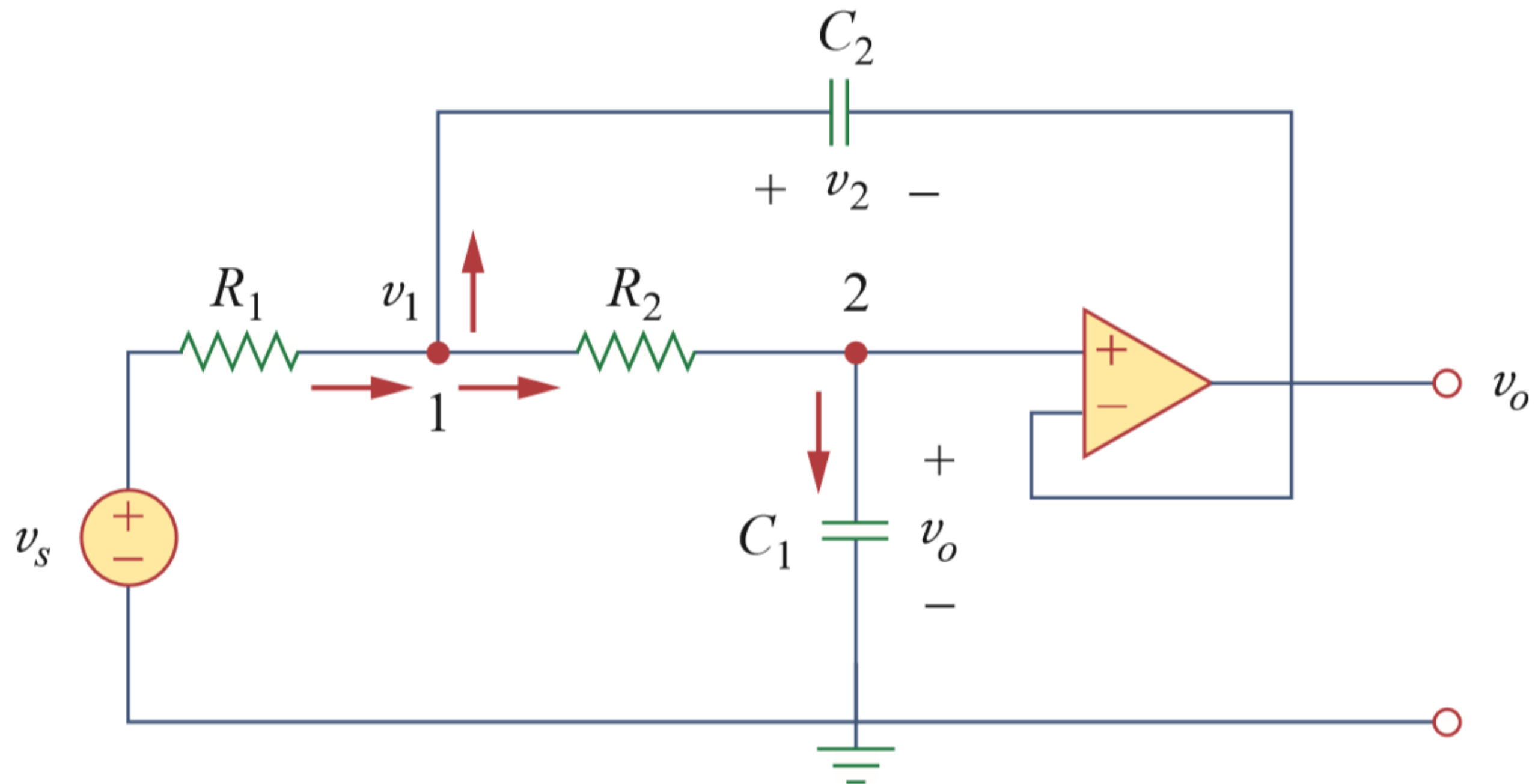

سؤال ۵

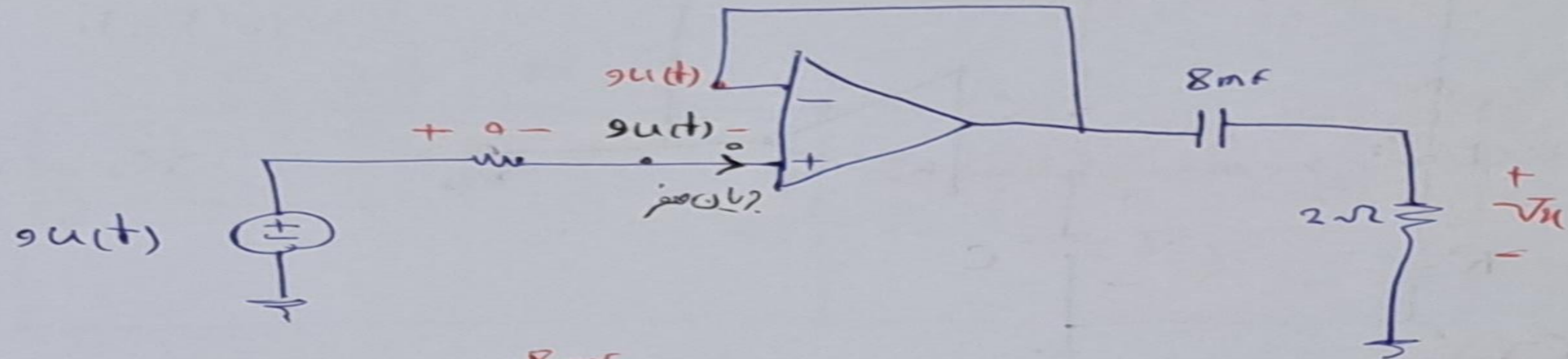

معادله بار

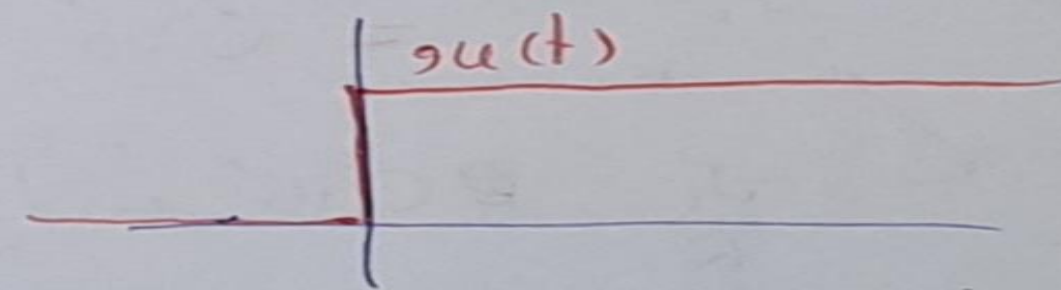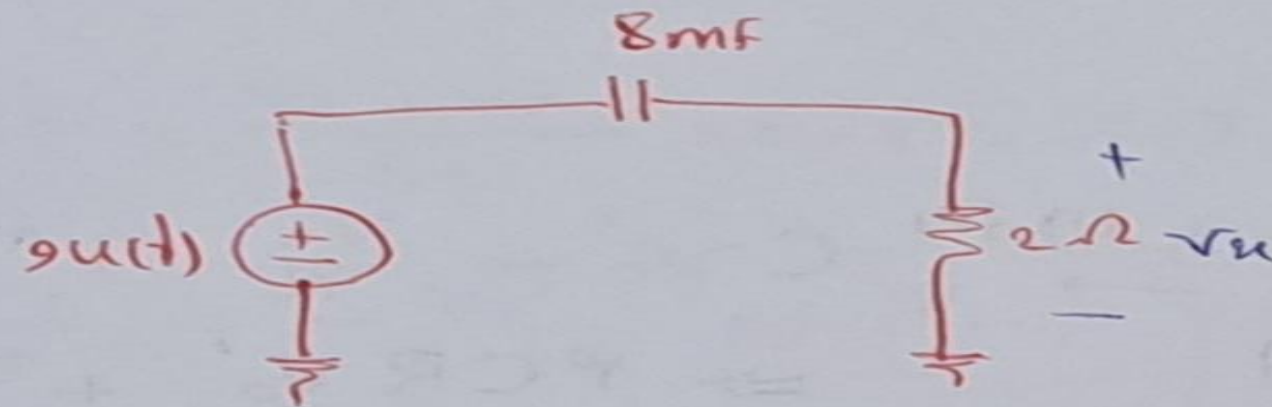

در لحظه صفر منفی ^{منفی} ~~منفی~~ در مدار ^{منفی} در نتیجه $v_c(0^-) = 0$

$$v_c(0^-) = v_c(0^+) \text{ و در دو منفی هستند}$$

در نتیجه در لحظه صفر مثبت v_c روی دو سه مقاومت است


$$v_u = \cancel{v_\infty} + (\cancel{v_c} - \cancel{v_\infty}) e^{-\frac{t}{16m}} = 9e^{-\frac{t}{16m}}$$

و لذا دو هم خازن مدار باز شده
در نتیجه $v_\infty = 0$

$$v_u(0^+) = 9$$


Class Exercise 9

If $v_{in} = \sin(200\pi t)$, plot the output voltage v_{out} .

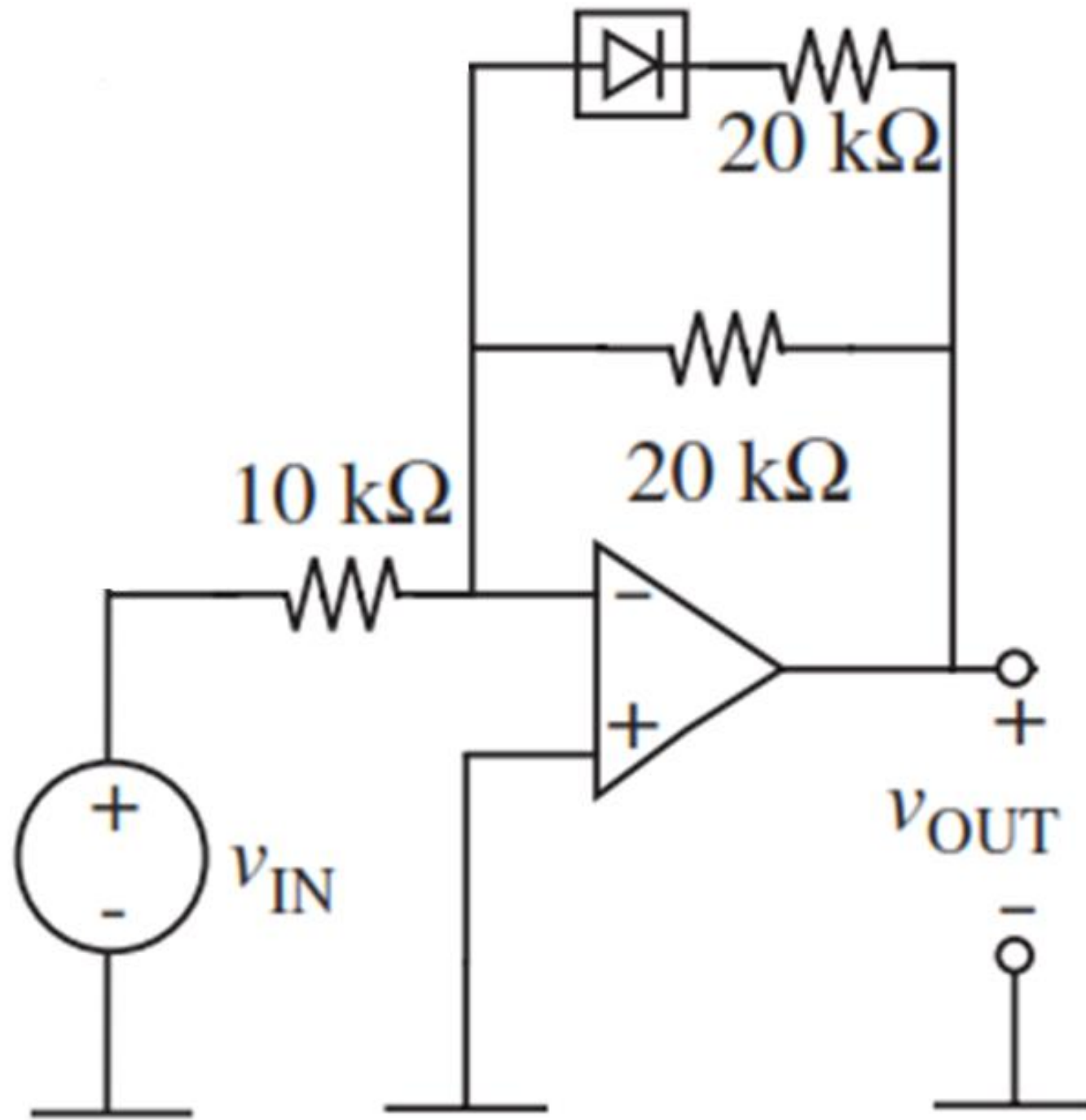

سوال ۹. مدل ایده آل.

$$V_{in} = \sin(200\pi t)$$

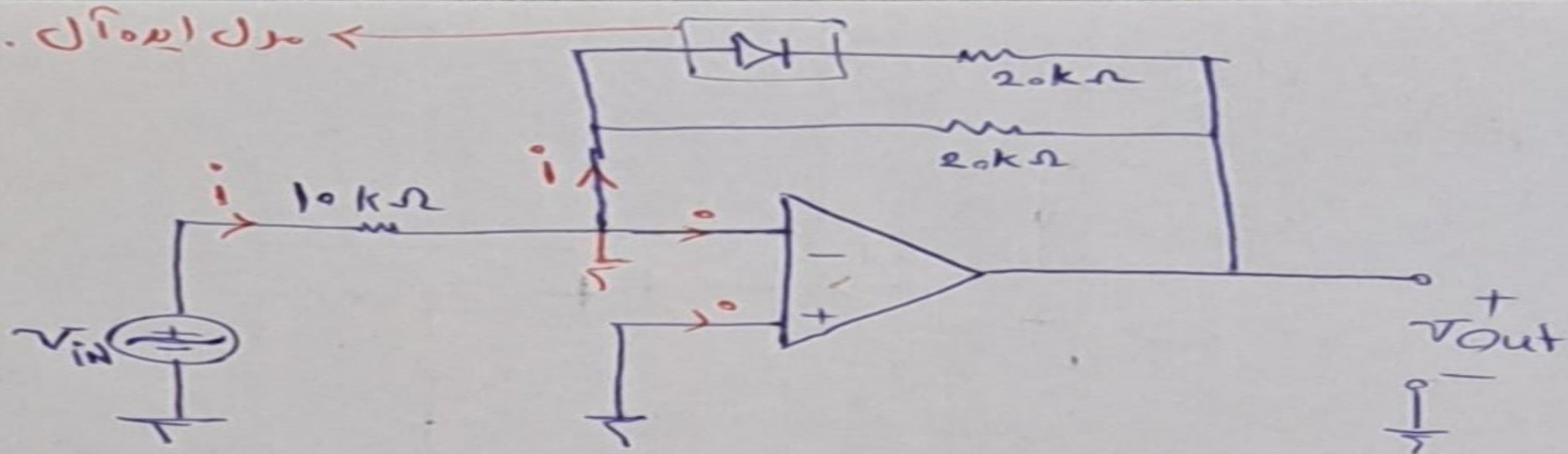


دیود ایده آل

$$\begin{aligned} V &= 0 \\ i &= 0 \end{aligned}$$

یا حالت فرستادن دیود
خاموش

یا استرلاک می کشیم که اگر دیود بخواهد روشن باشد یا مدبر بماند آن صفت باشد بران آن هم

$$i = \frac{V_{in}}{10k}$$

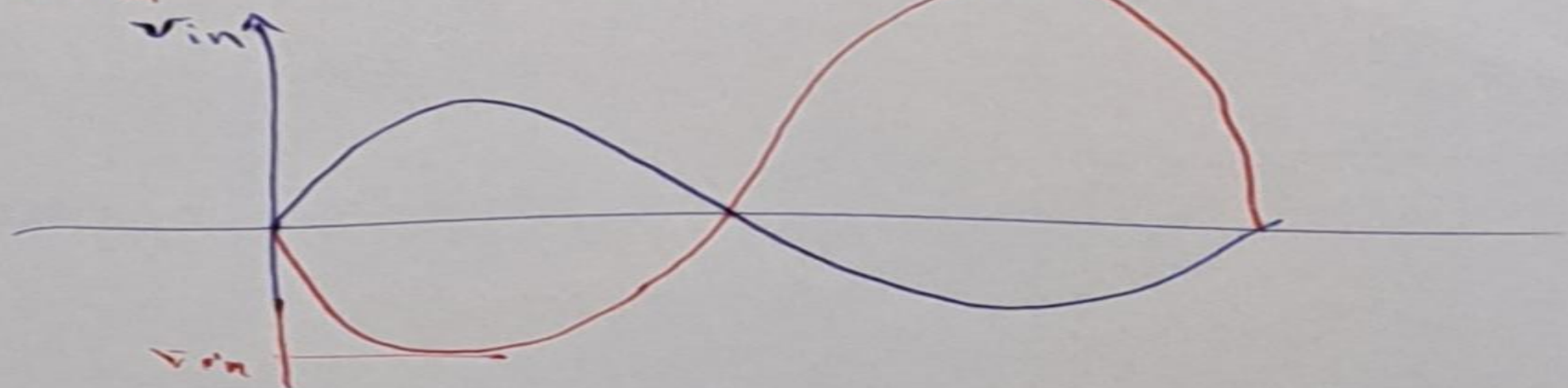

یا دیود وصل

$$20 \parallel 20 = 10k$$

$$V_{out} = \frac{-10k}{10k} V_{in}$$


یا دیود قطع

$$20$$

$$V_{out} = -2 V_{in}$$


Class Exercise 10

- Plot the diagram of v_{out} as a function of v_{in} .

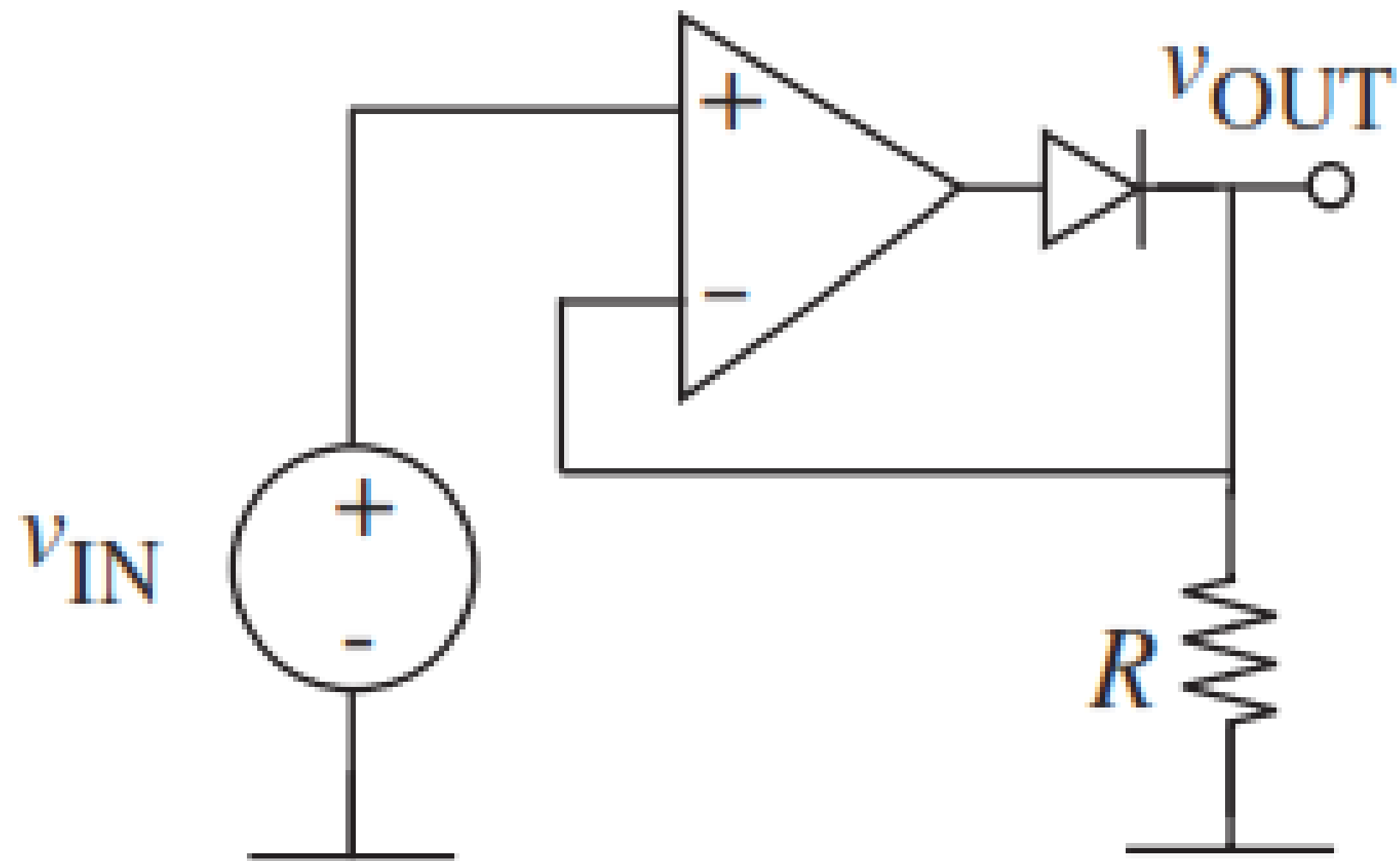

سؤال ۱۰

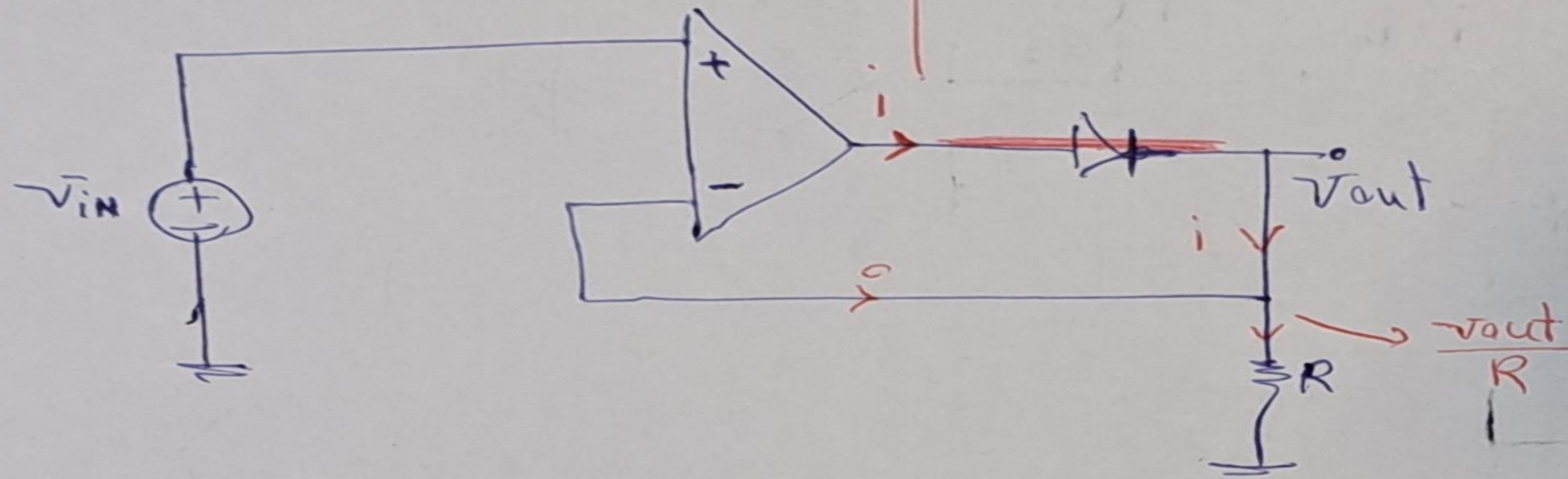روشن یا خاموش بودن به این بیان وابسته شده تا امکان در مورد آن
حرف نزنه بعدیم .




$$v_{out} = v_{in}$$

وضعیت ۱) روشن باشد. در نتیجه

$$i = \frac{v_{out}}{R} = \frac{v_{in}}{R}$$

v_{in} که همیشه مثبت نیست.

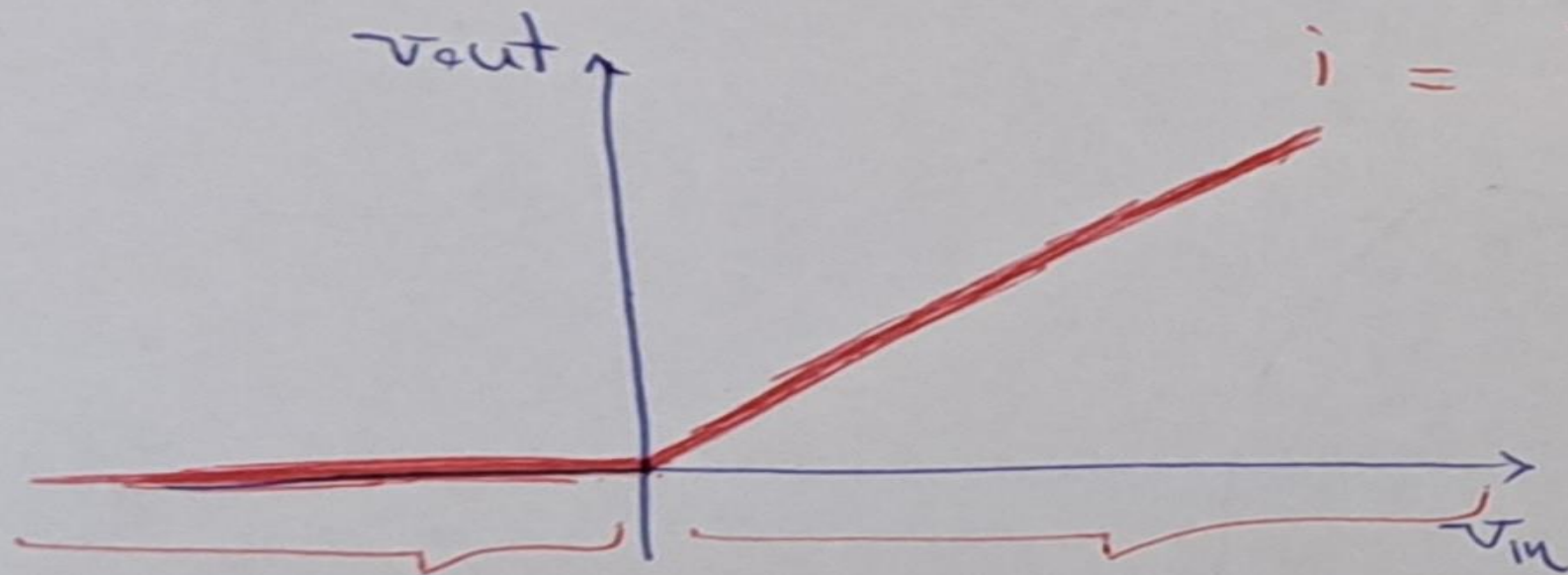


$i > 0$ شرط روشن بودن


در نتیجه برای $v_{in} > 0$ می توان $v_{out} = v_{in}$

Class Exercise 11

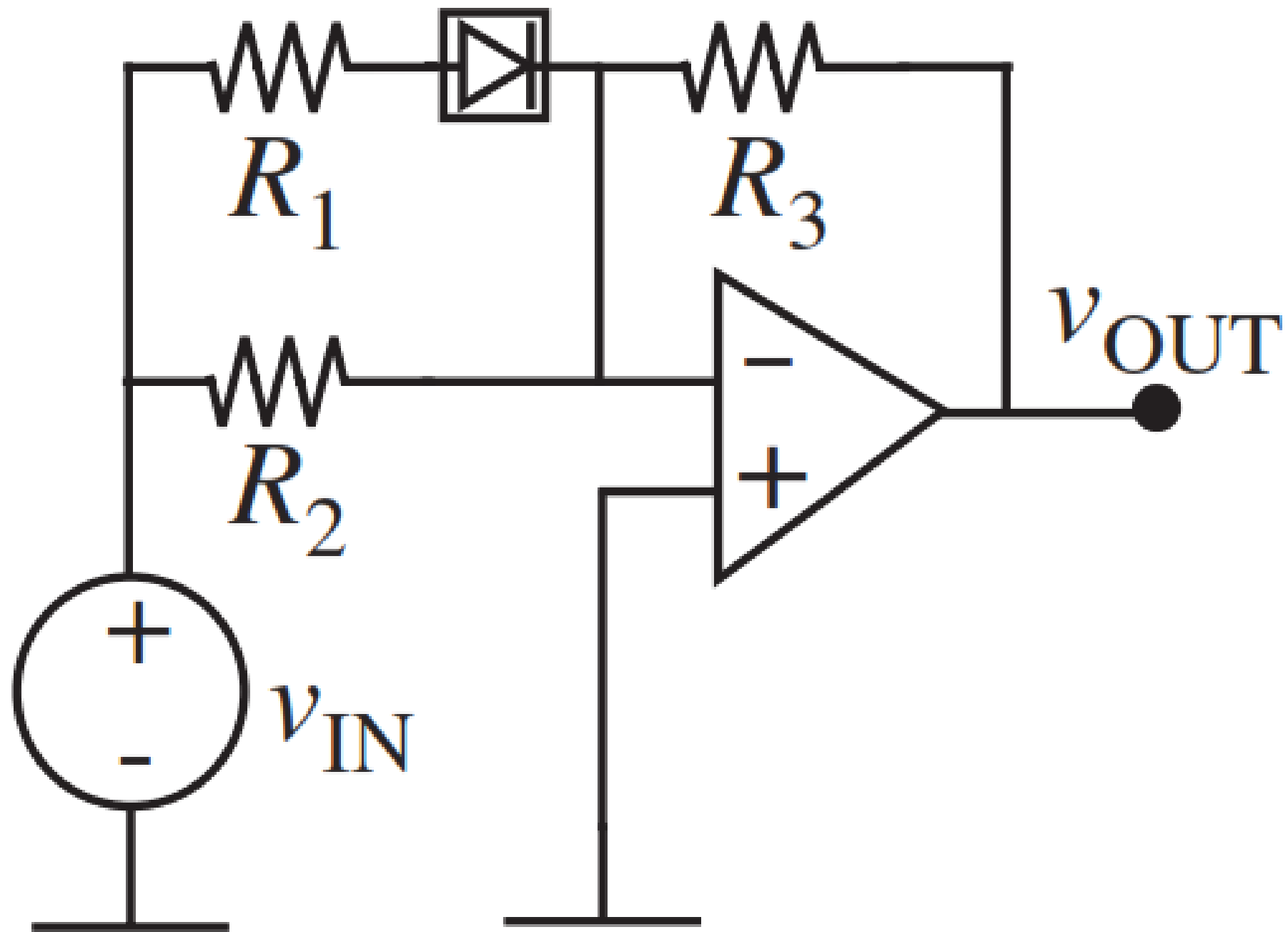- Plot the diagram of v_{out} as a function of v_{in} .



II

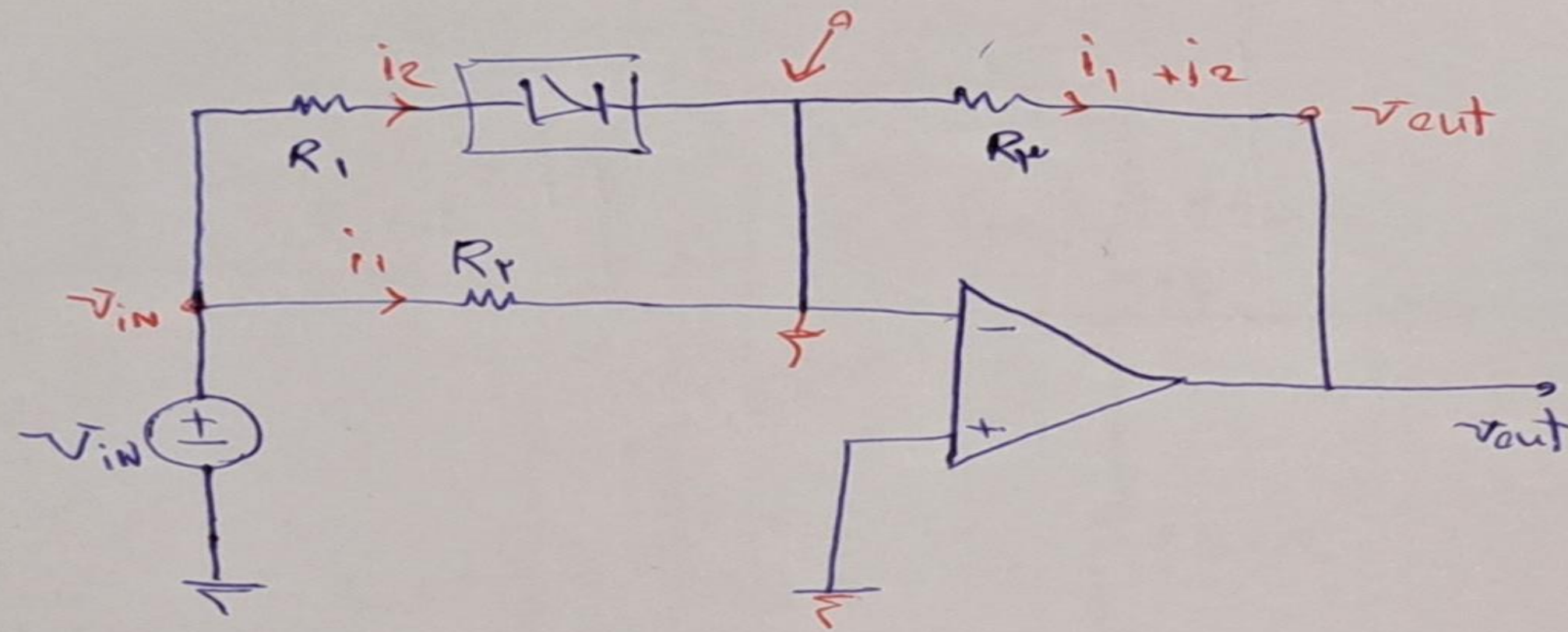

فرض کنیم D روشن باشد.

$$KCL: \frac{0 - V_{in}}{R_1 \parallel R_r} + \frac{0 - V_{out}}{R_f} = 0 \Rightarrow$$


$$V_{out} = -\frac{R_f}{R_1 \parallel R_r} V_{in}$$

تقویت کننده معکوس کننده

سره روشن بودن $i_2 > 0 \leftarrow V_{in} > 0$

سره خاموش $V_{in} < 0 \leftarrow$


$$V_{out} = -\frac{R_f}{R_r} V_{in}$$

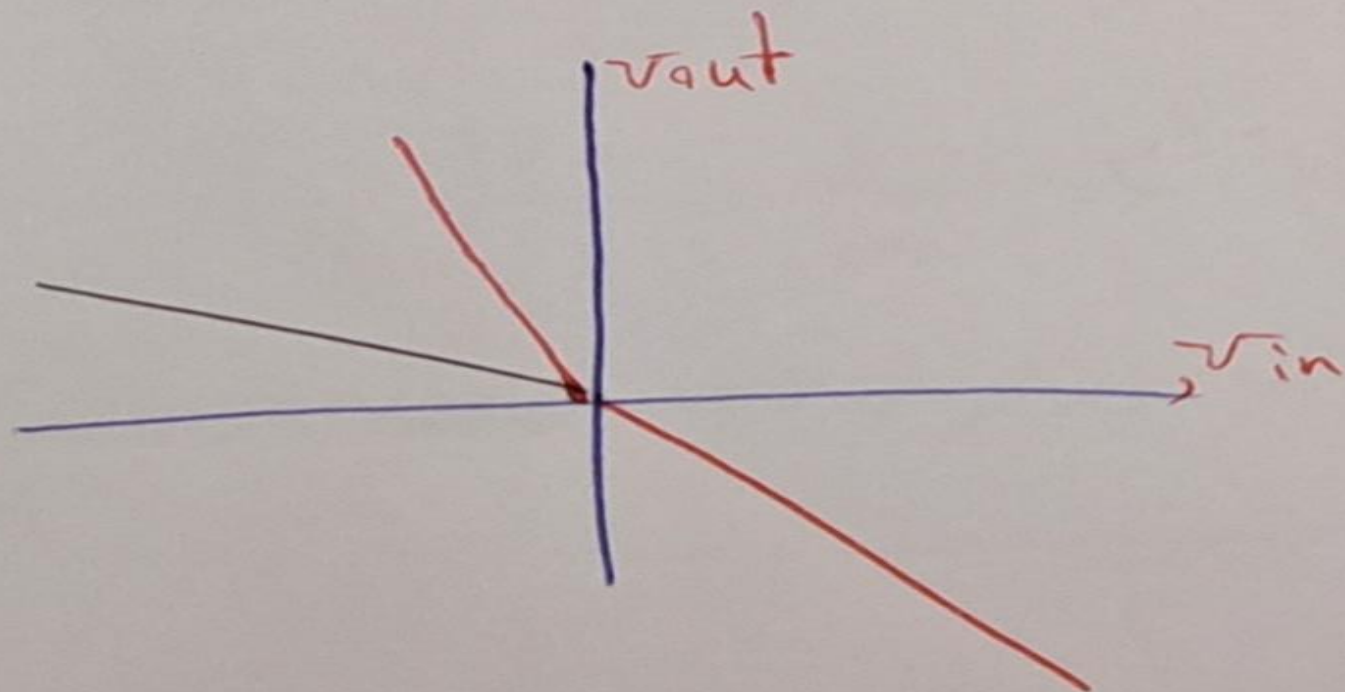


Class Exercise

This is an active filter (using an op-amp in a frequency filter). Calculate:

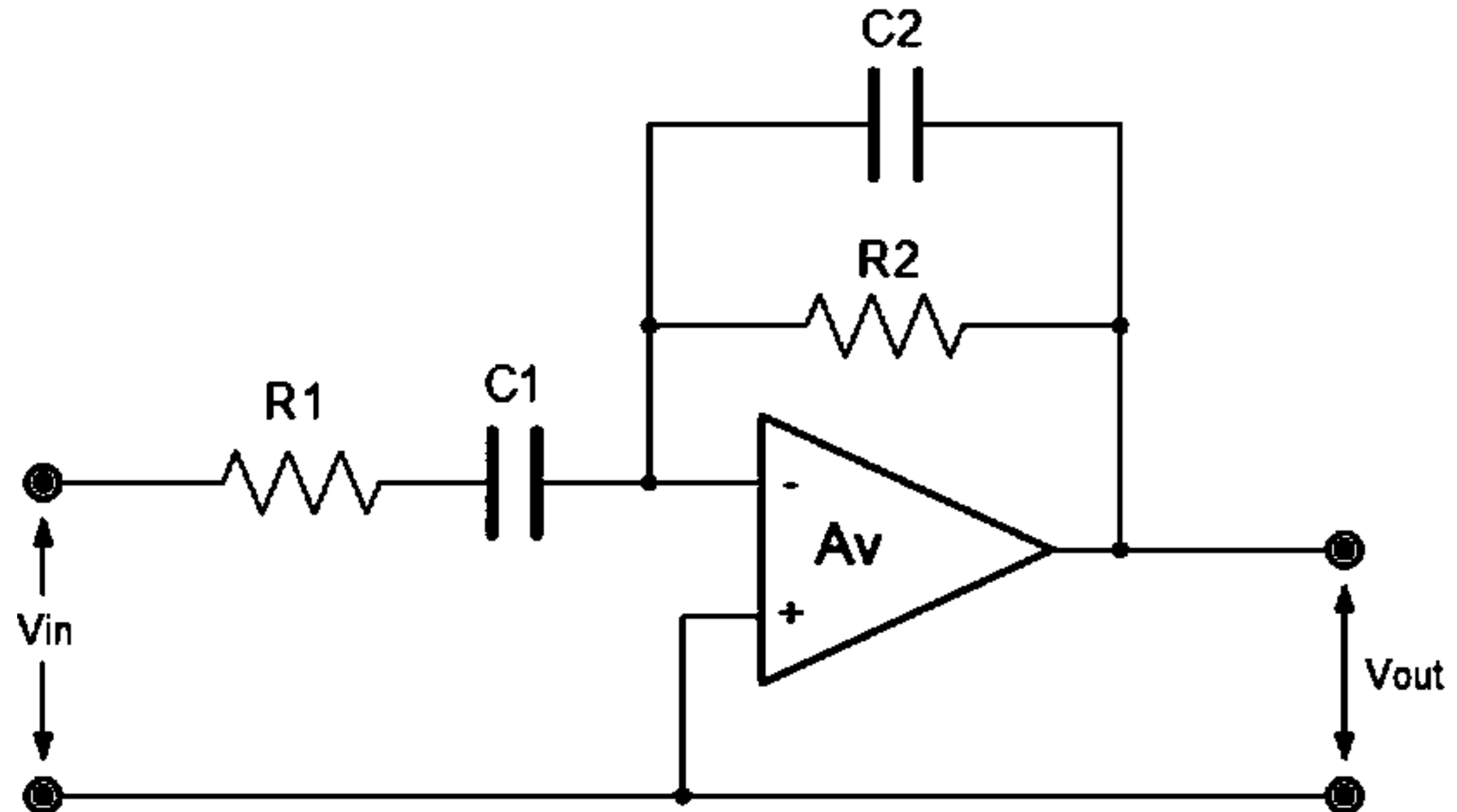- ✓ The type of filter
- ✓ The filter gain
- ✓ The cut-off frequency



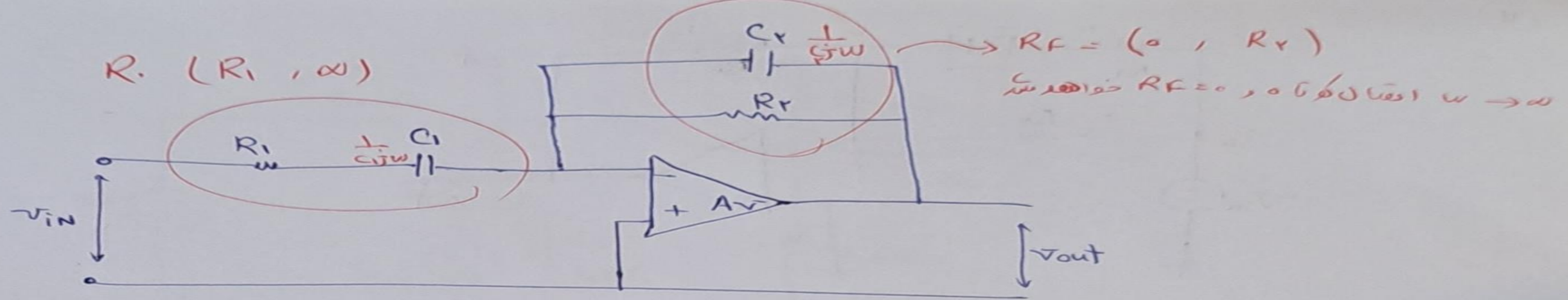

$$V_{out} = -\frac{R_f}{R_i} V_{in}$$

به تقویت کننده عکس کننده است.

مثال: مقاومت متغیر با فرکانس.

که R و R_f در فرکانس های مختلف تغییر می کنند.

$$V_{out} = -\frac{R_f}{R_i} V_{in}$$

در فرکانس پایین

$$R_f = 0$$

$$R = R_i$$

$$\Rightarrow A = \frac{0}{R_i} = 0$$

در فرکانس بالا

$$\Rightarrow A = \frac{R_f}{\infty} = 0$$



$$\frac{1}{\sqrt{2}}$$

ادامه آن مثل قبل خواهد شد A ، ادا ریم در واقع تابع انتقال را داریم

بگذاریم و فرکانس قطع را حساب کنیم.



Thanks
