



دانشگاه صنعتی امیر کبیر
(پلی تکنیک تهران)

Electrical and Electronic Circuits

chapter 7. RLC Circuits

Afarghadan@aut.ac.ir



عظیم فرقدان 

مهر ۱۴۰۳



Objectives of the Lecture

- Application of RL and RC circuits
- Second order circuits: RLC
 - Parallel RLC circuit without source
 - Series RLC circuit without source
 - Complete response in the presence of source and initial conditions
 - How to calculate initial conditions

The RL and RC Circuit

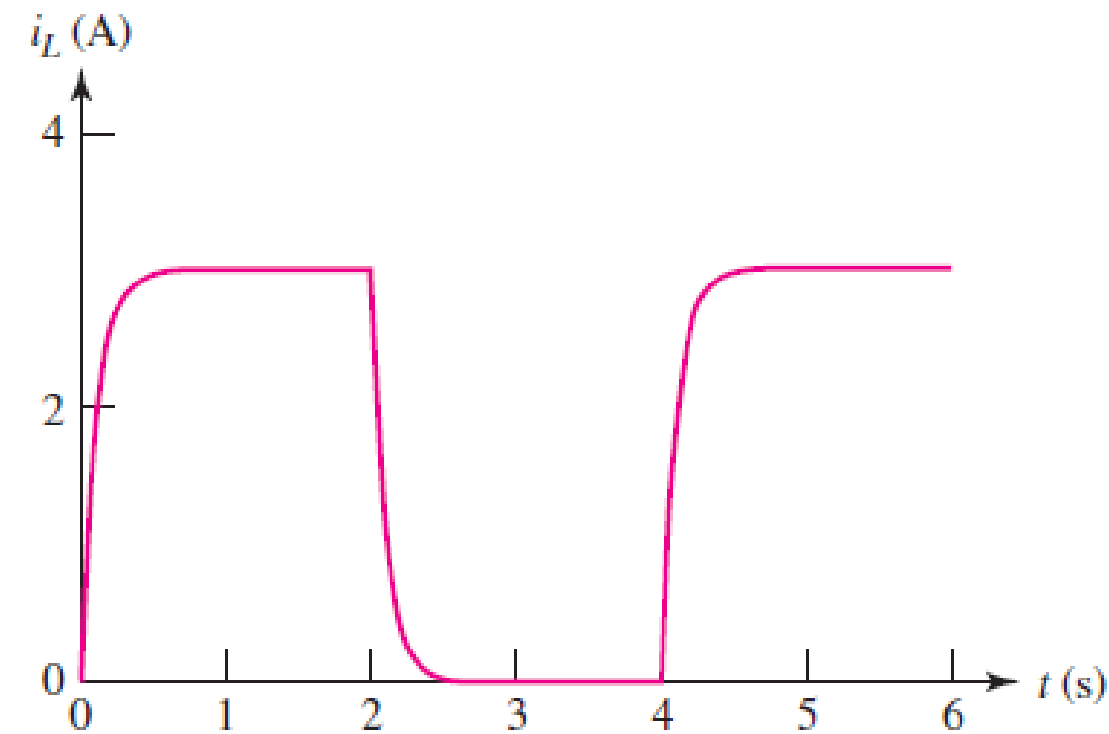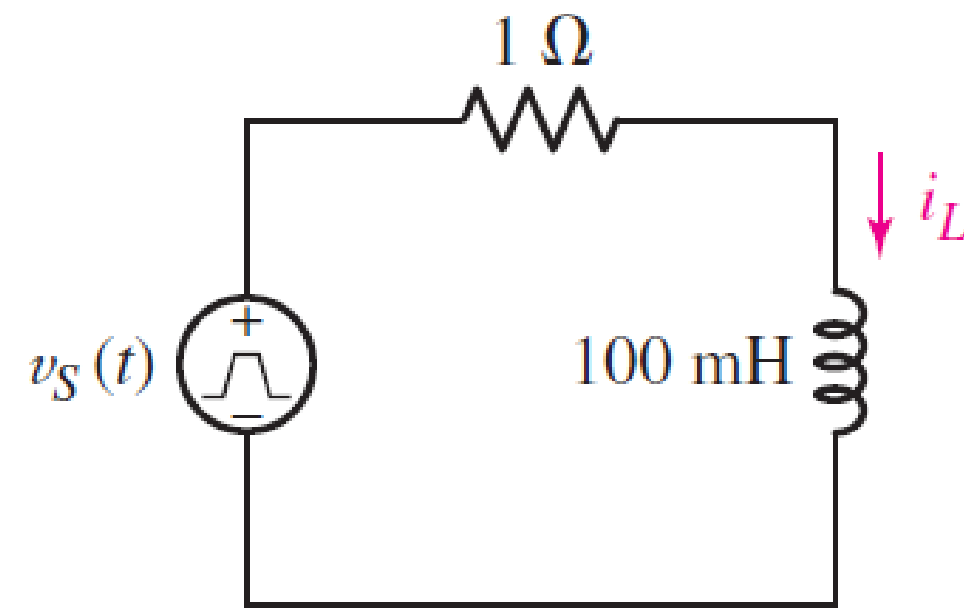
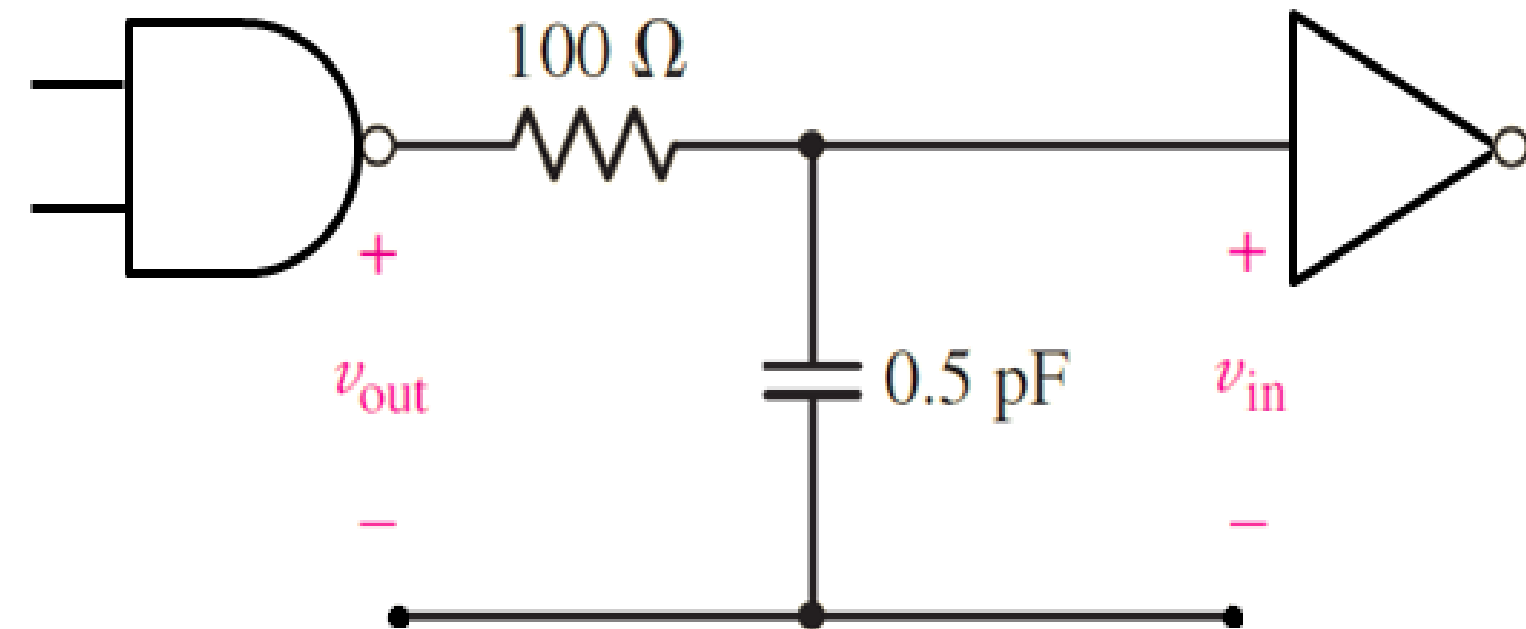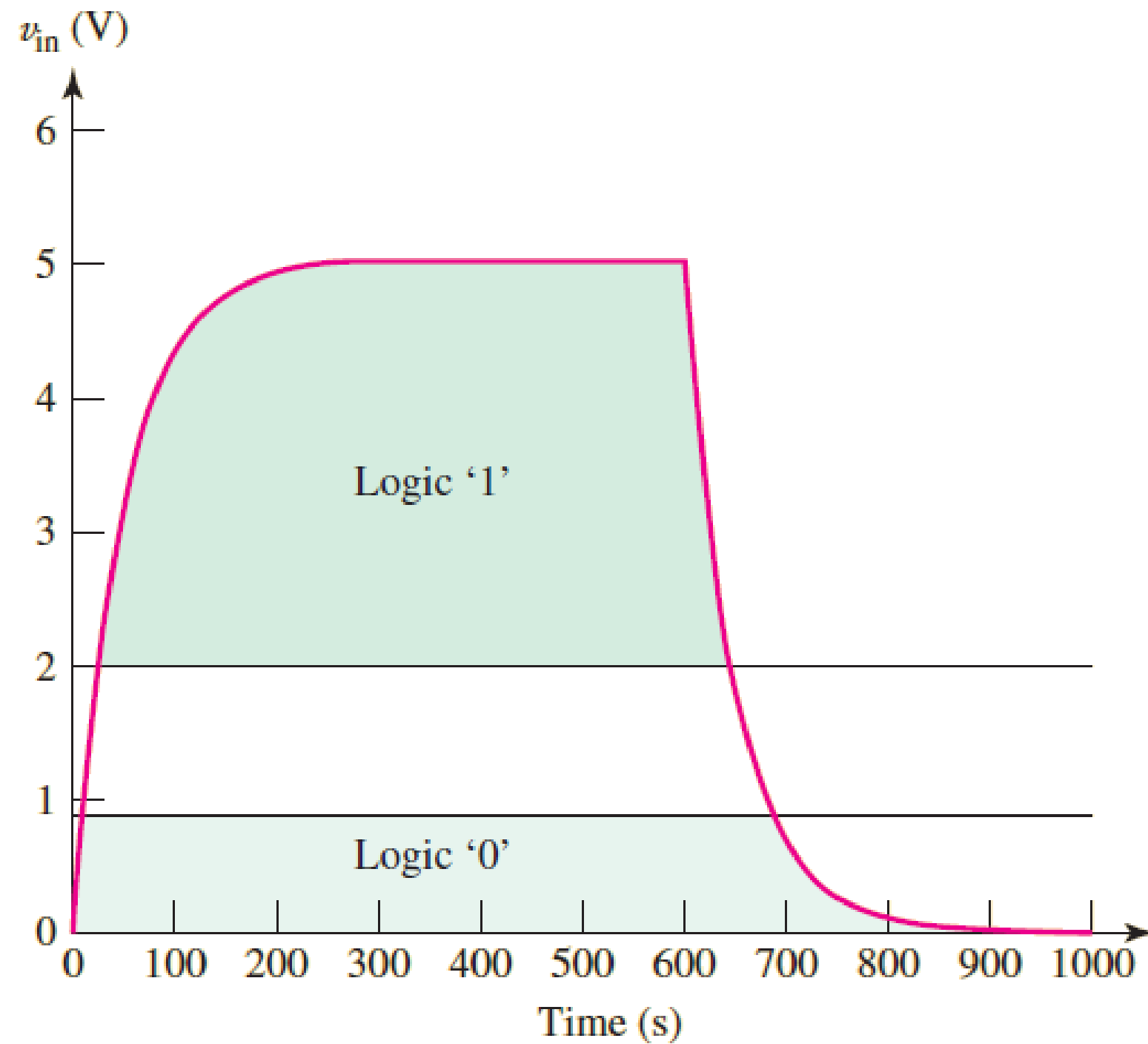
$$i_L(t) = \frac{V_0}{R} \left(1 - e^{-Rt/L}\right) u(t)$$




- The parasitic resistance and capacitor of the wire connecting two logic gates increases the delay.
- Maximum allowed frequency:


$$f_{max} = \frac{1}{2 \times 5\tau} = 2\text{Ghz}$$

Application as a frequency filter




- A low-pass filter

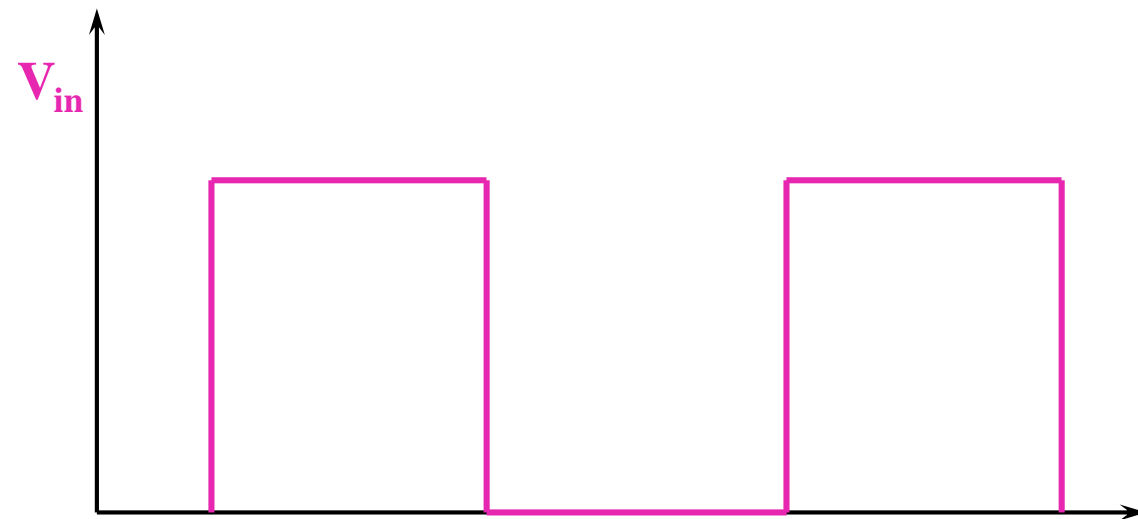



Low frequency

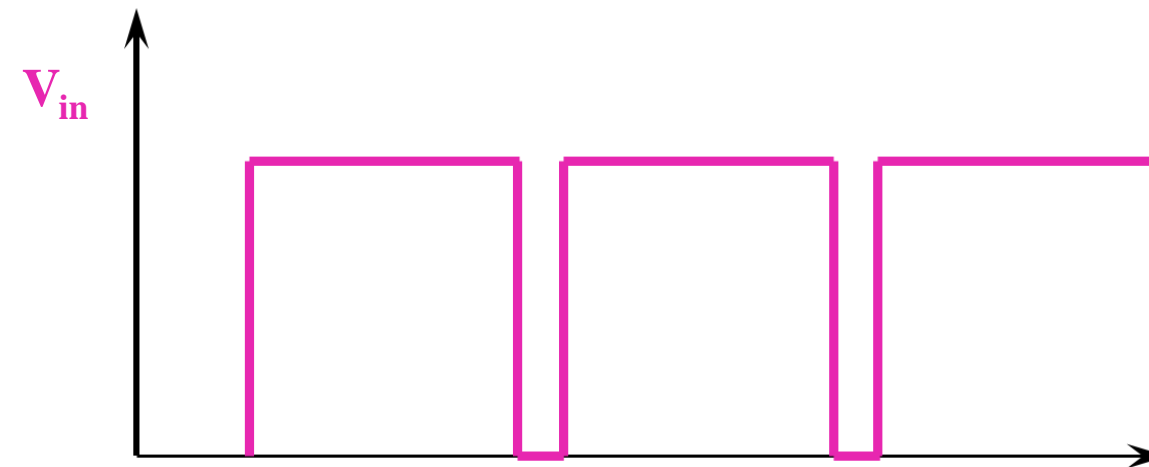

High frequency

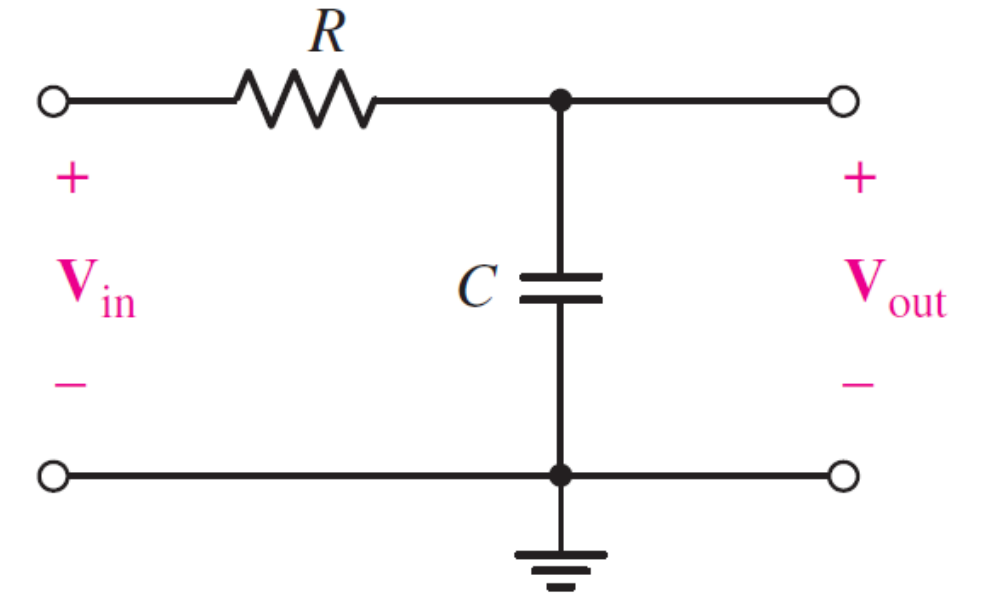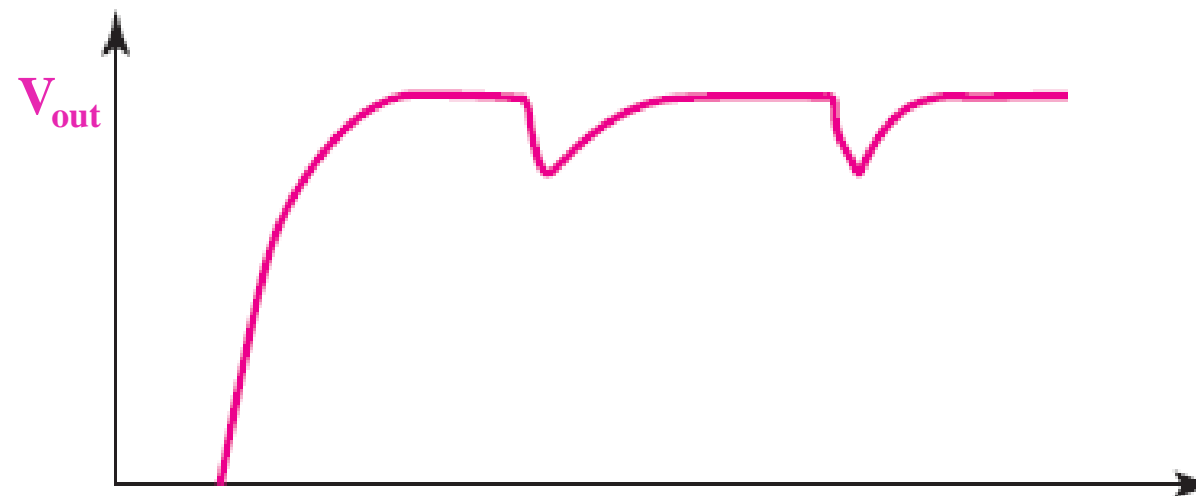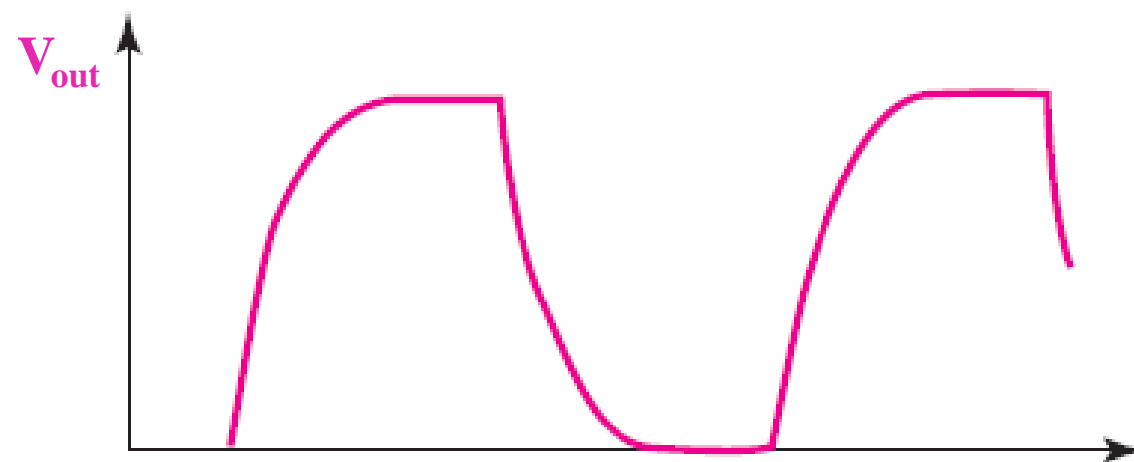

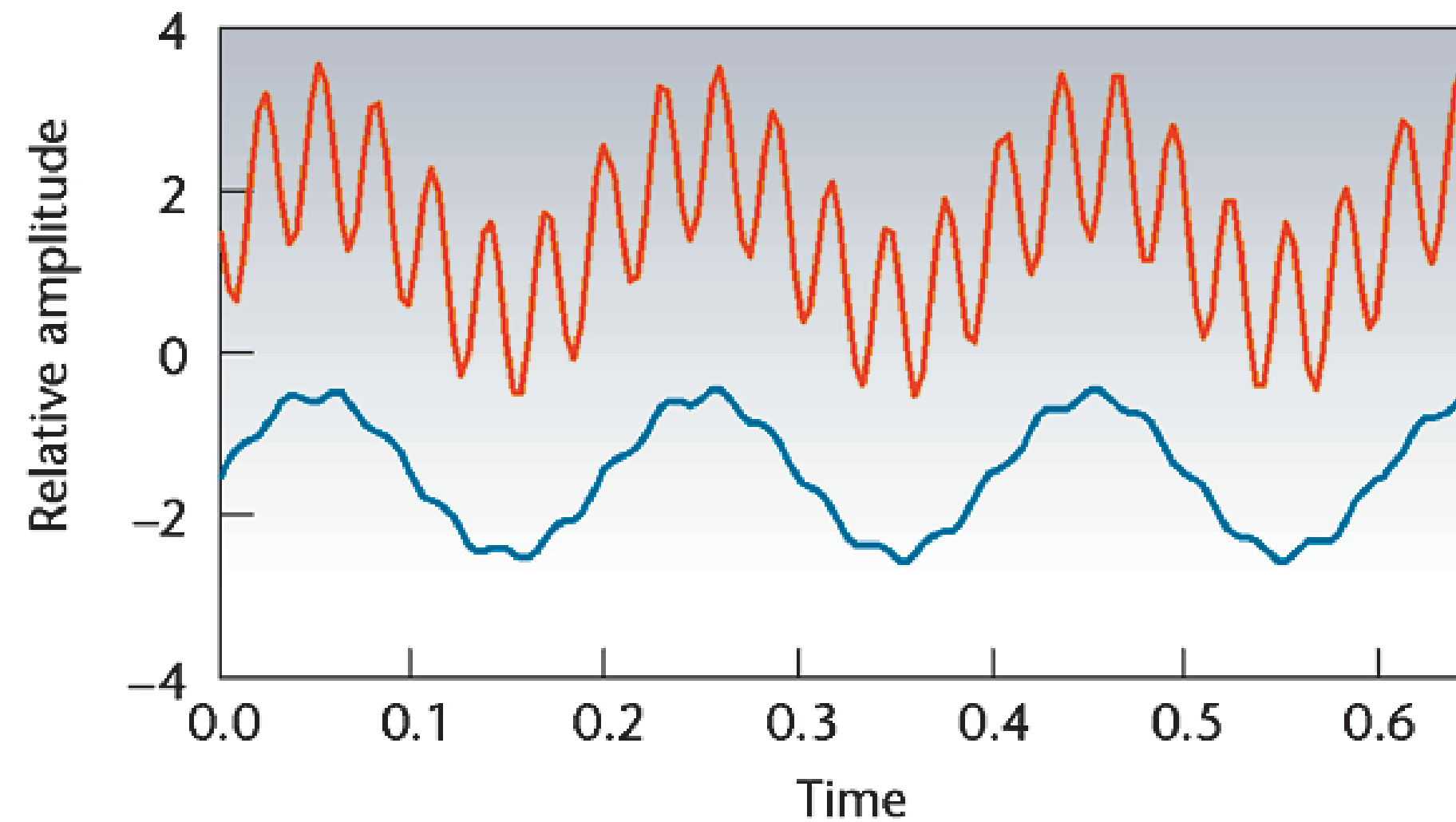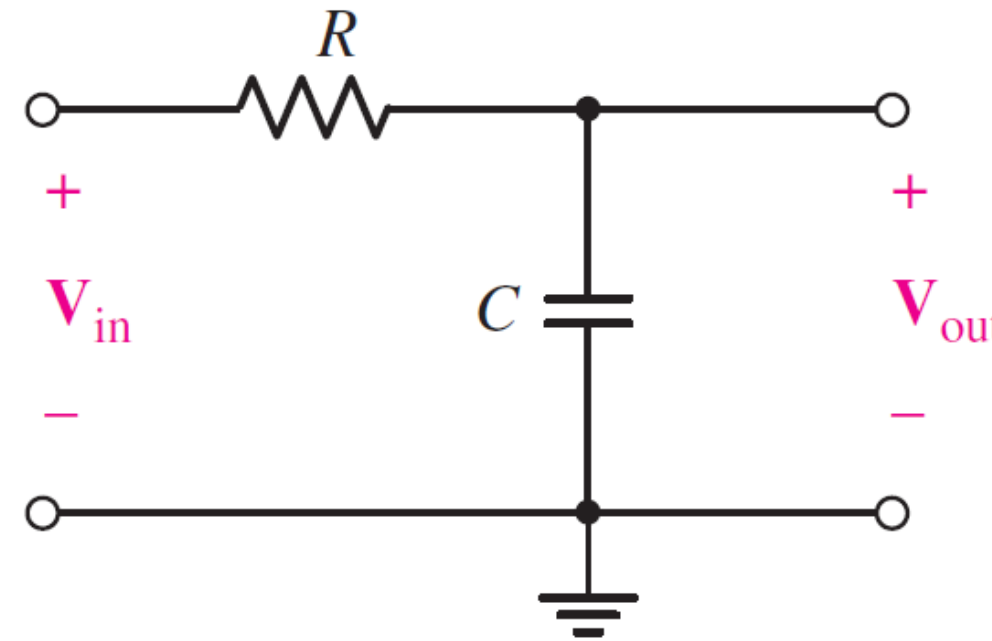Application as a frequency filter: noise removal




The RLC circuit

- An RLC circuit has **both an inductor and a capacitor**.
- If it has only one inductor and one capacitor, the circuit will be second order.
- Of course, a second-order circuit can be made with two capacitors or two inductors.
- RLC circuits have many different applications:
 - **Oscillator**: A circuit that produces an alternating pulse (to make a clock)
 - **Frequency filter**: For example, to remove noise
 - **Analog radio** receiver and...
- It is also possible to model the behaviour of car suspension system, elevator, airplane, temperature controller, etc. using an RLC circuit.

The Source-Free RLC Parallel Circuit

Applying KCL differentiate to show:

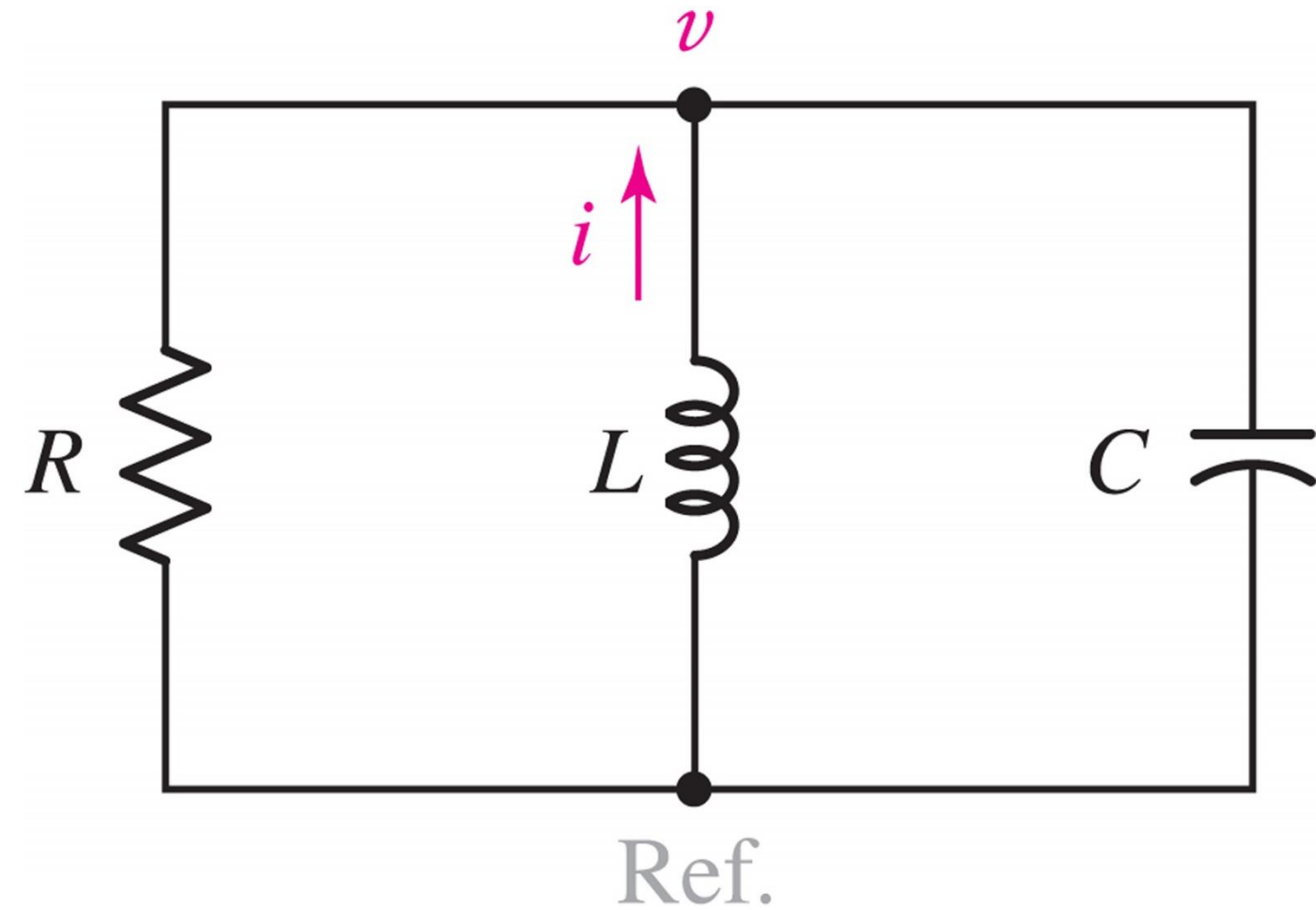

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

Solving the Differential Equation

To solve, assume $v=Ae^{st}$.

The solution must then satisfy:

$$Cs^2 + \frac{1}{R}s + \frac{1}{L} = 0$$

which is called the *characteristic equation*.

If s_1 and s_2 are the solutions, then the natural response is

$$v(t) = A_1e^{s_1t} + A_2e^{s_2t}$$

Exploring the Solution

The solutions to the characteristic equation are:

$$s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

Define ω_0 *the resonant frequency*:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

and α *the damping coefficient*:

$$\alpha = \frac{1}{2RC}$$

With these definitions, the solutions can be expressed as:

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

The constants A_1 and A_2 are determined by the initial conditions.

Types of Responses

- If $\alpha > \omega_0$ the solutions are real, unequal and the response is termed *overdamped*.
 - The response does not have an oscillatory state. Like dropping a pendulum in a container of grease, or dropping a very stiff spring.
- If $\alpha = \omega_0$ the solutions are real and equal and the response is termed *critically damped*.
 - The circuit is on the verge of oscillating, but it is not yet oscillating.
- If $\alpha < \omega_0$ the solutions are complex conjugates and the response is termed *underdamped*.
 - The response of the circuit is in the form of oscillatory damping. Like dropping a pendulum

Both roots are real and distinct.

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$


$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

The normal response form is as follows.


$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Overdamped Parallel RLC

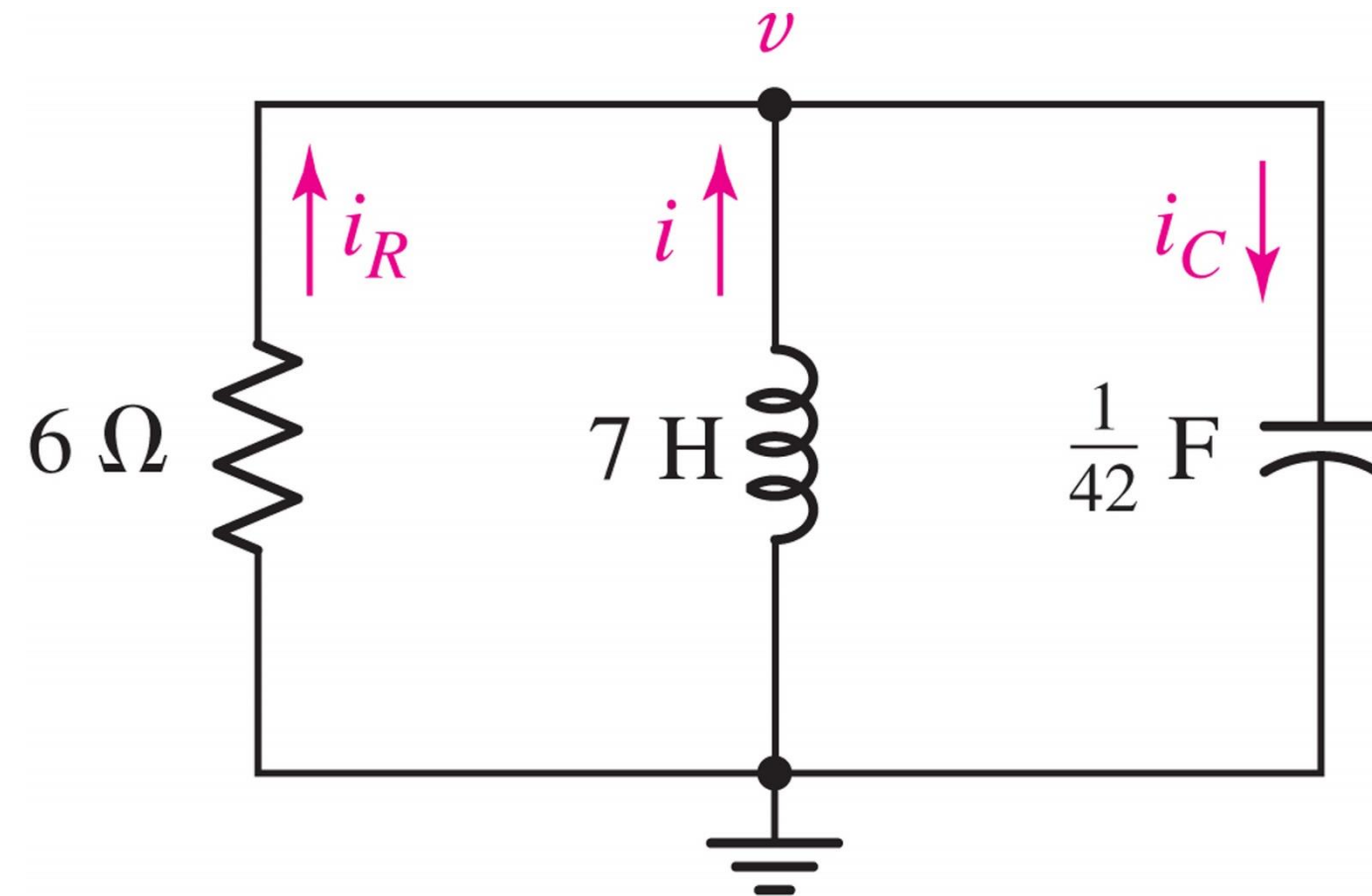Show that $v(t) = 84(e^{-t} - e^{-6t})$ when $i(0^+) = 10$ A and $v(0^+) = 0$ V.




Graphing the Response

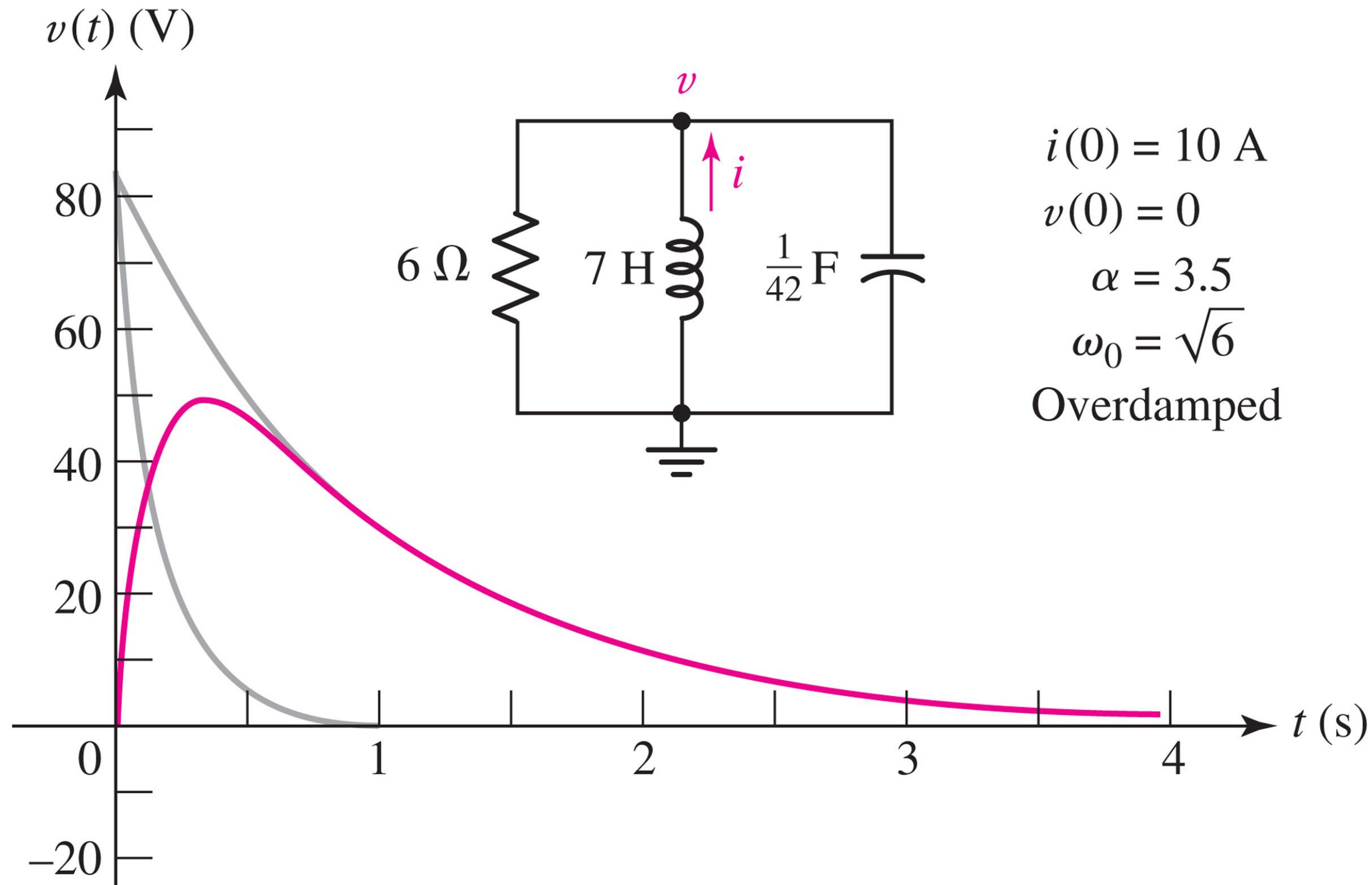

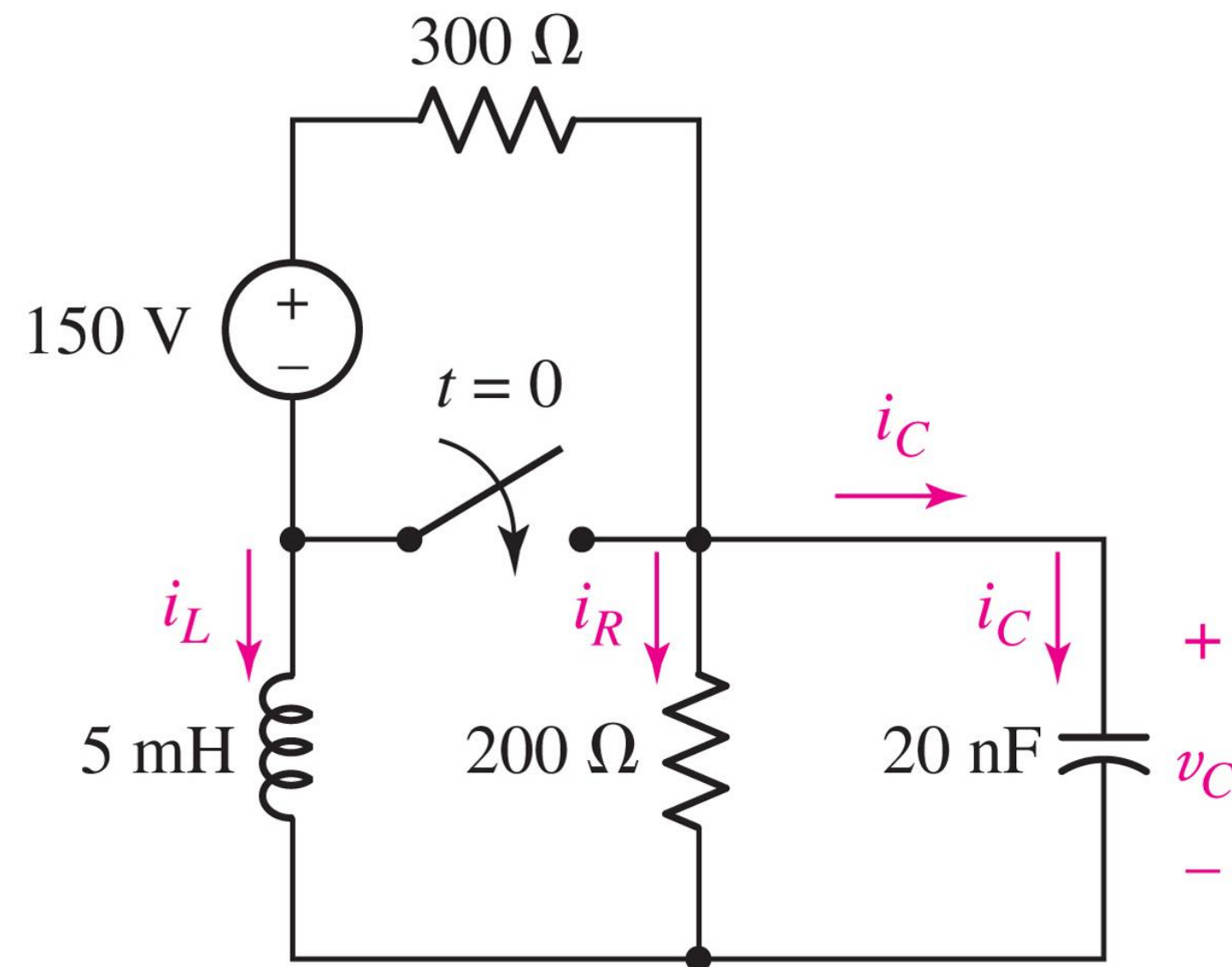Example 2: overdamped RLC Circuit

Show that $v_C(t) = 80e^{-50,000t} - 20e^{-200,000t}$ V for $t > 0$.



A double real root:

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$
$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$


$$s_1 = s_2 = -\alpha$$

The normal response form is as follows:

$$v(t) = e^{-\alpha t} (A_1 t + A_2)$$

Critical Damping ($\alpha=\omega_0$)

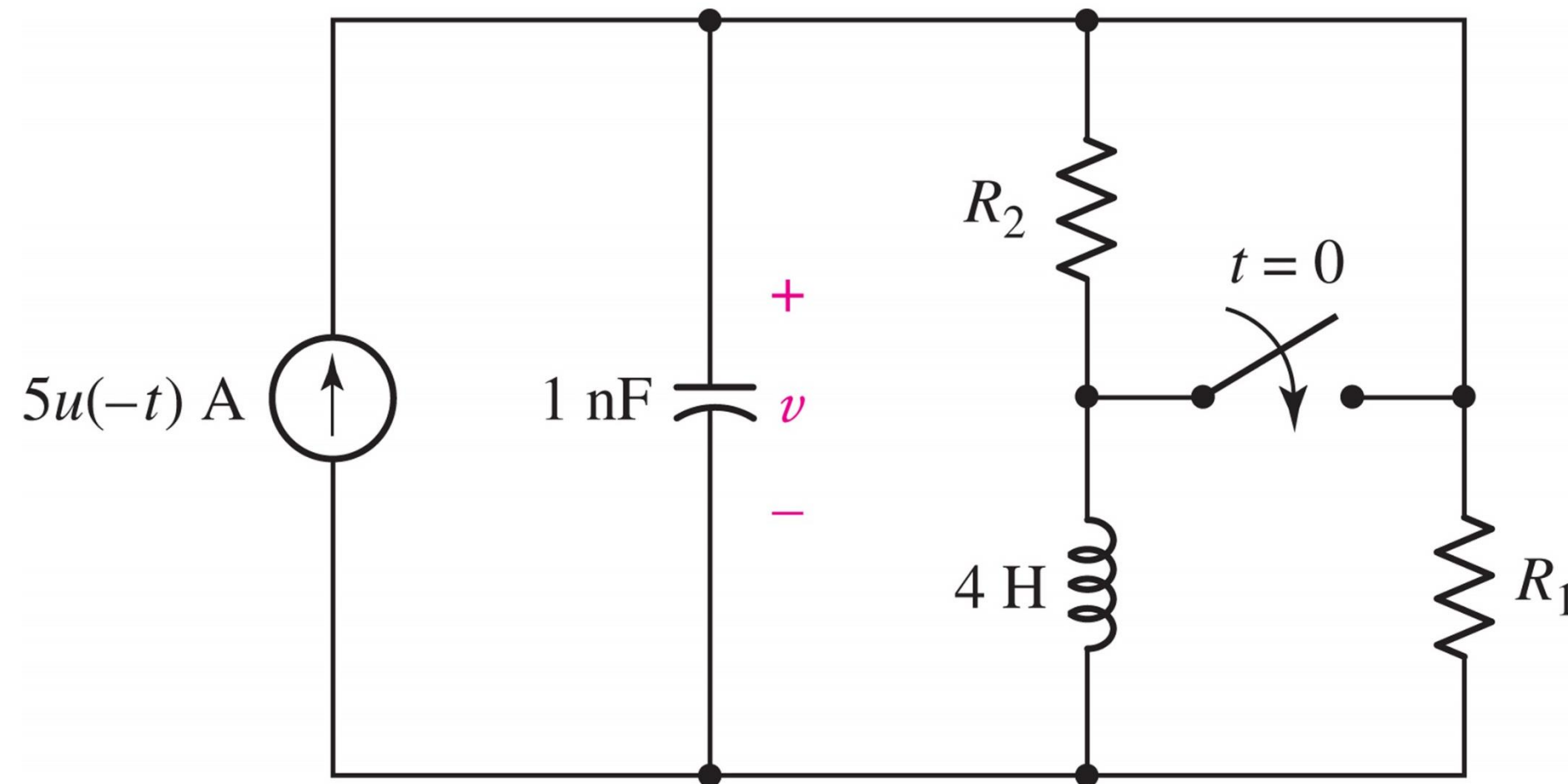Find R_1 such that the circuit is critically damped for $t>0$ and R_2 so that $v(0)=2$ V.



Answer: $R_1 = 31.63$ k Ω , $R_2=0.4\Omega$

The Underdamped Response ($\alpha < \omega_0$)

If $\alpha < \omega_0$, define:

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$


and the solution is

$$v(t) = e^{-\alpha t} \left(A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t} \right)$$

or equivalently


$$v(t) = e^{-\alpha t} \left(B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t) \right)$$

Example: Underdamped Response

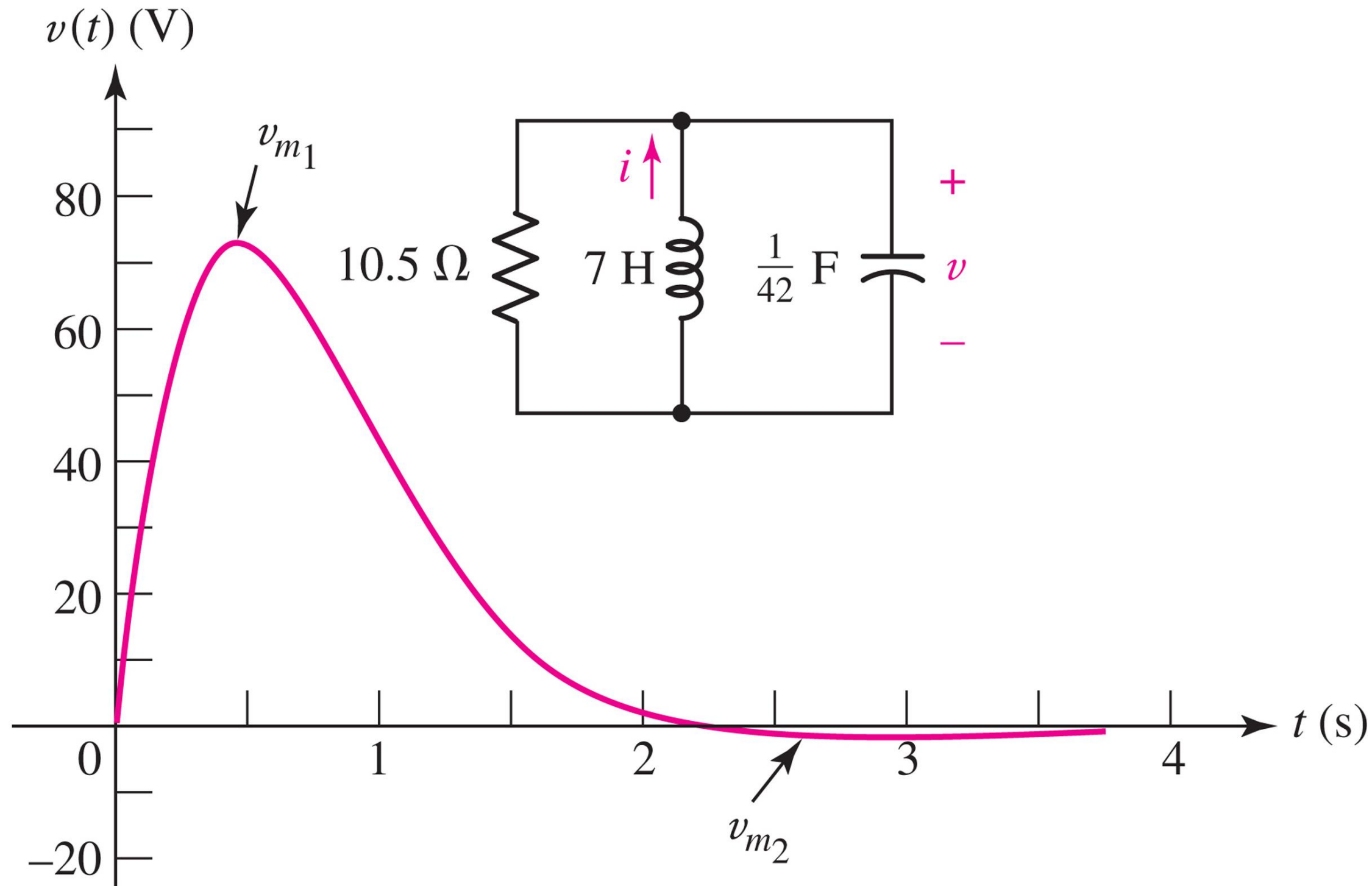

$$v(t) = 210\sqrt{2}e^{-2t} \sin \sqrt{2}t$$



Comparing the Responses

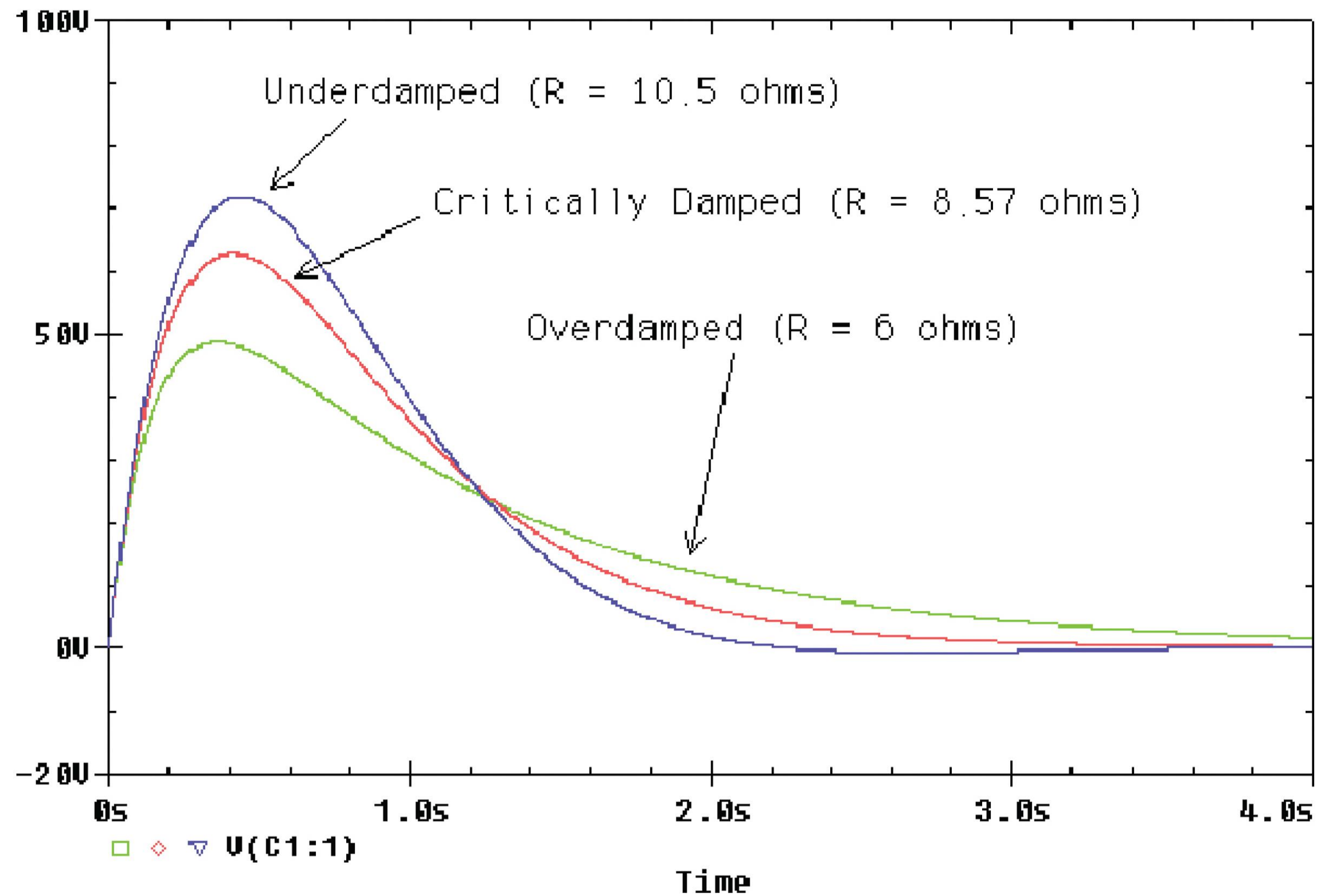

Determining the Response: Underdamped Example


Show for $t > 0$
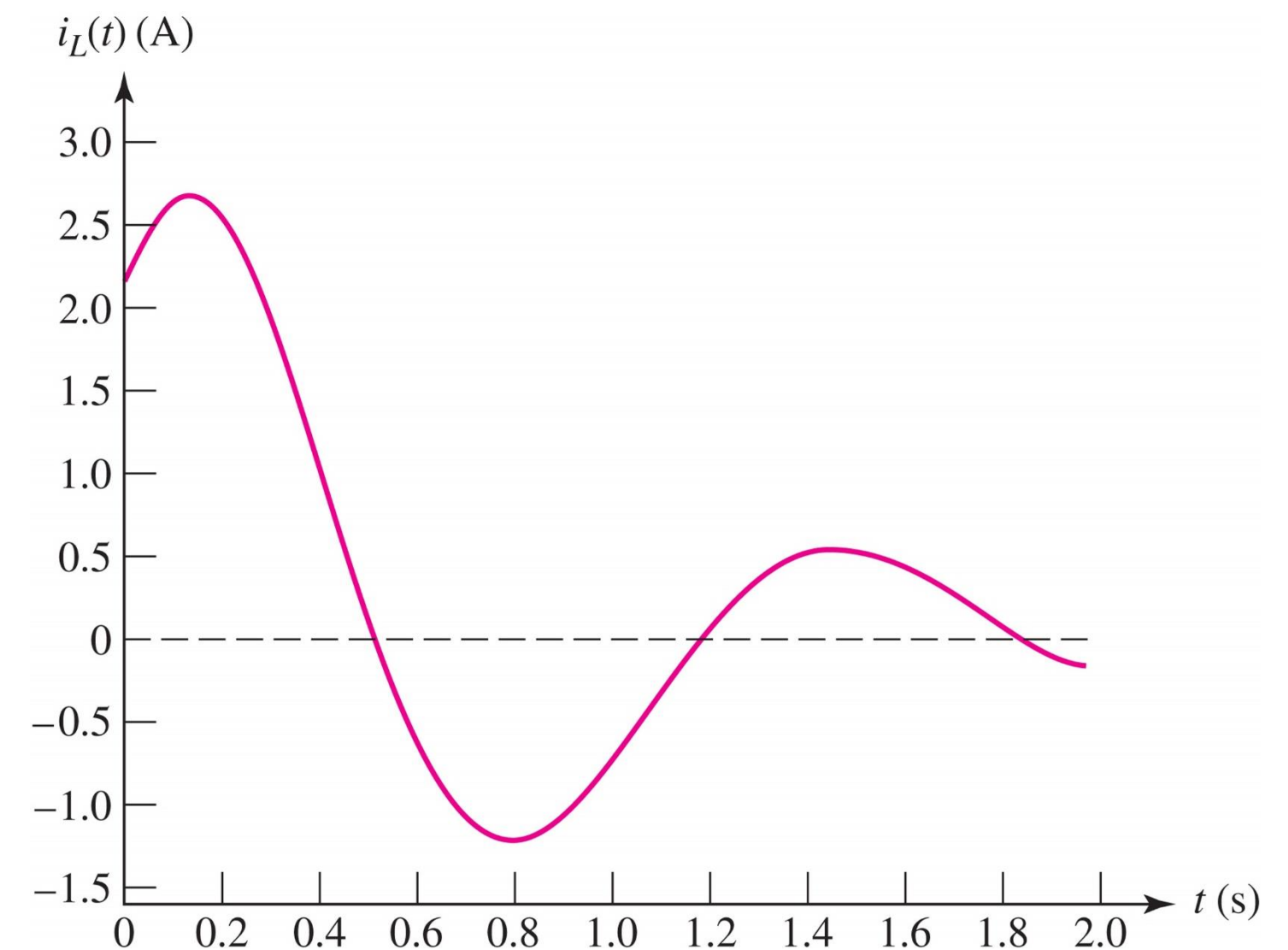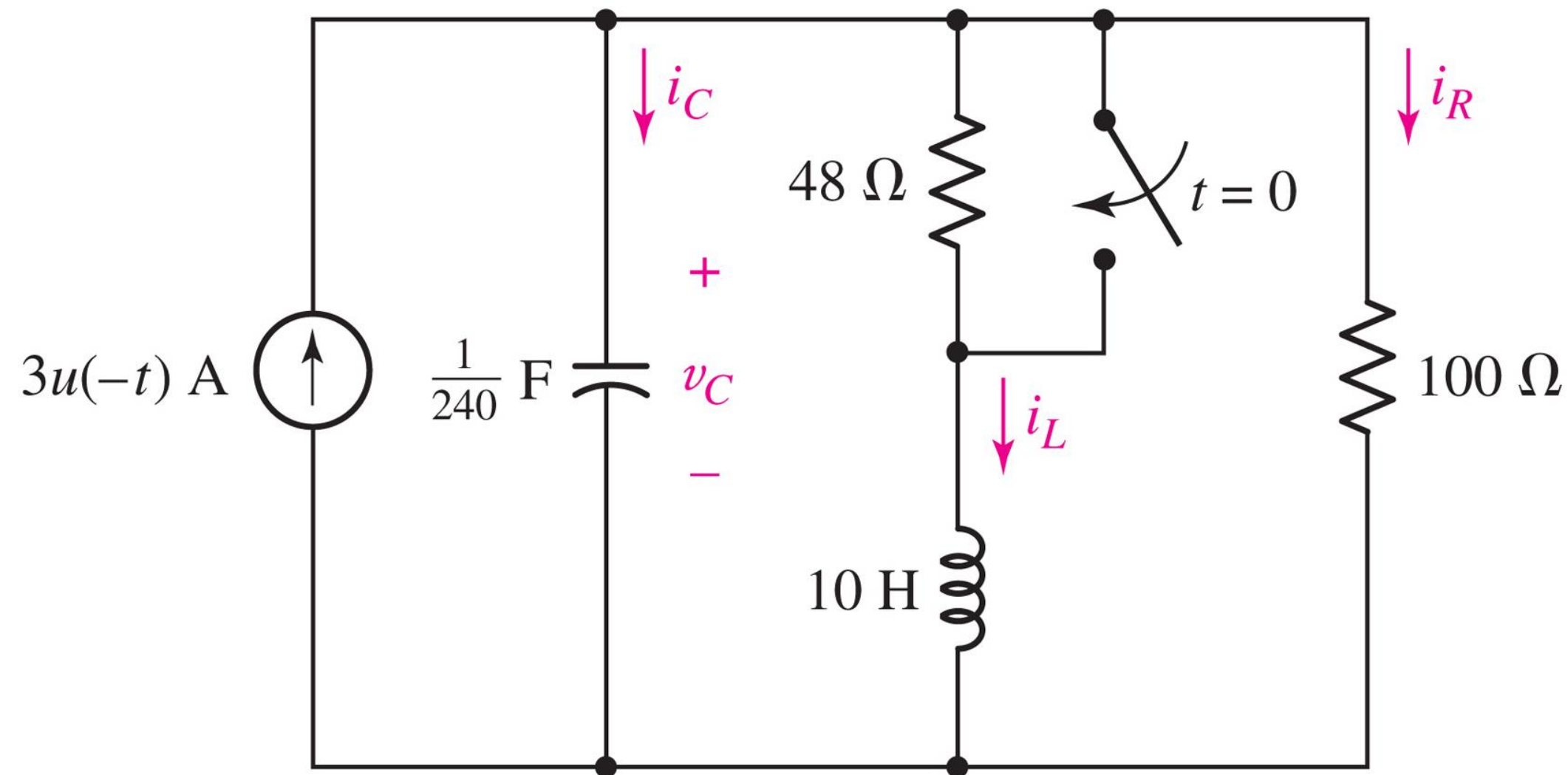
$$i_L = e^{-1.2t} (2.027 \cos 4.75t + 2.561 \sin 4.75t)$$



For the series RLC circuit,
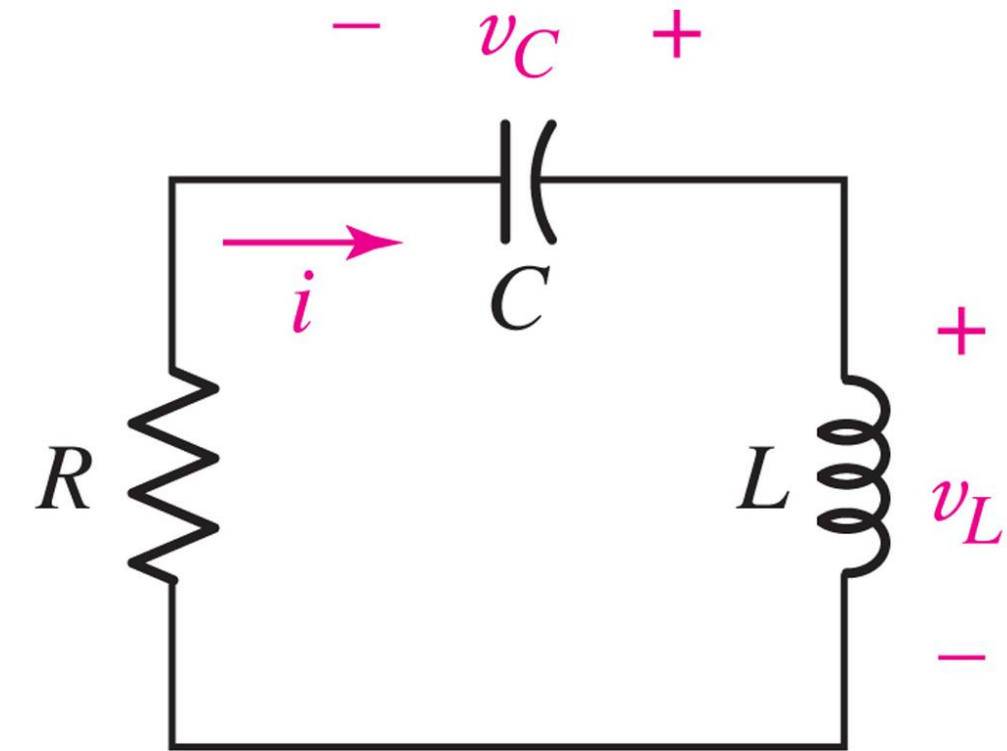
$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$



This circuit is the dual of the parallel RLC circuit.

The characteristic equation is:

$$Ls^2 + Rs + \frac{1}{C} = 0$$

Where:

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Define $\omega_0 = 1/\sqrt{LC}$ and $\alpha = \frac{R}{2L}$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Then if

$\alpha > \omega_0$ (overdamped):

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$\alpha = \omega_0$ (critically damped):


$$v(t) = e^{-\alpha t} (A_1 t + A_2)$$

$\alpha < \omega_0$ (underdamped):


$$v(t) = e^{-\alpha t} (B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t))$$

Underdamped ($R=100\ \Omega$)

$$C = 100\text{nF}, L = 7\mu\text{H}$$

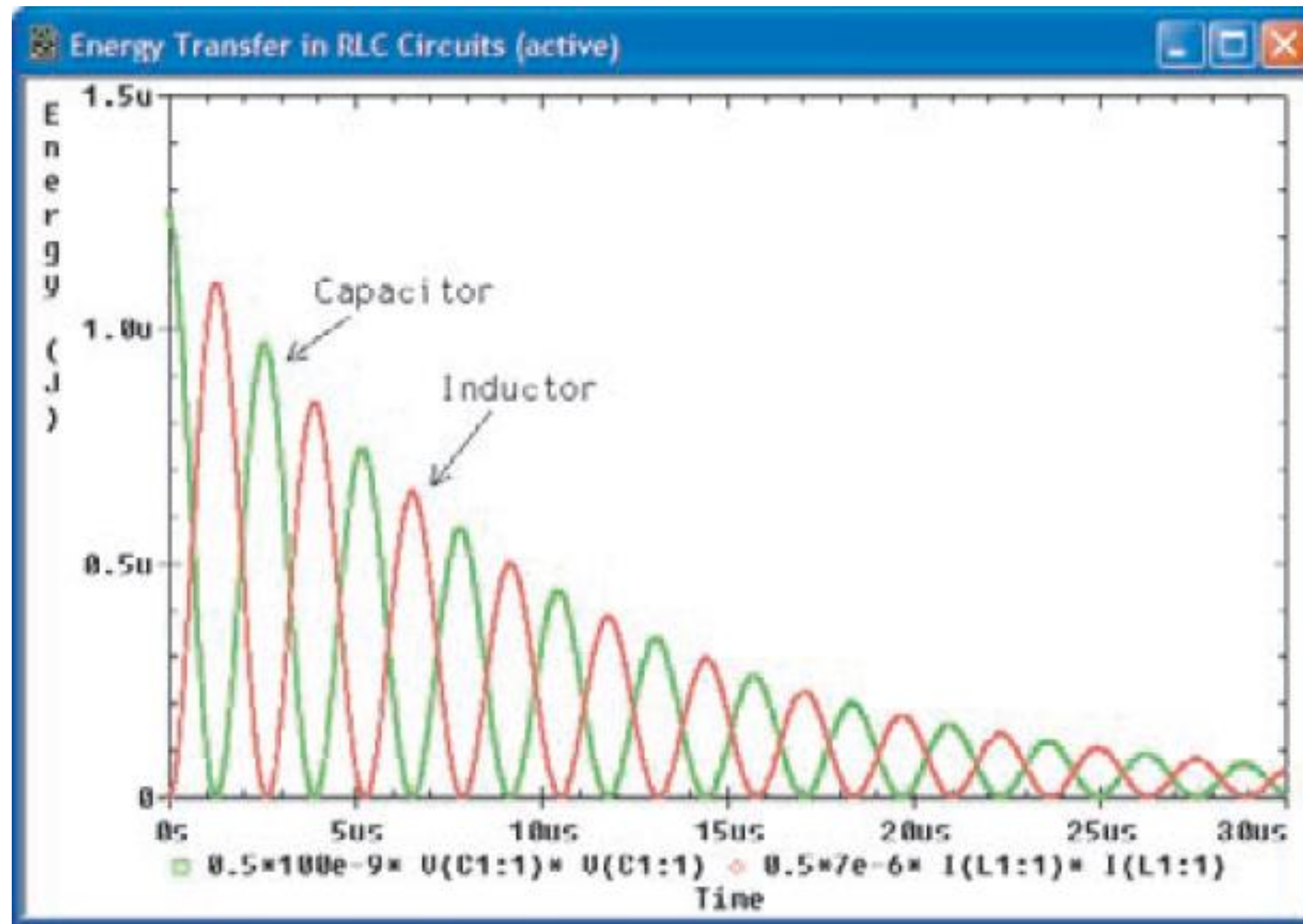


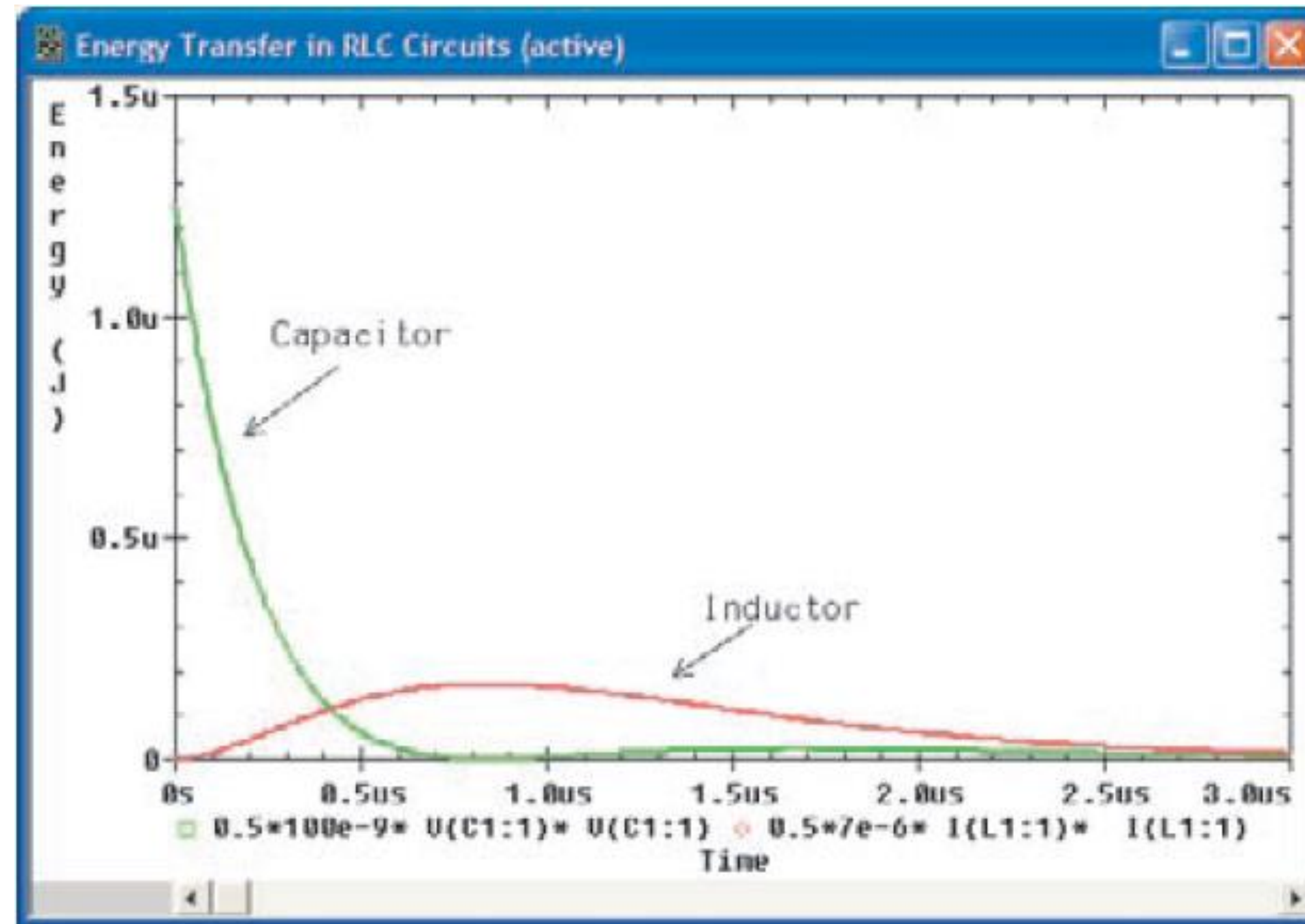critically damped ($R=100\ \Omega$) $C = 100\text{nF}, L = 7\mu\text{H}$



Overdamped ($R=100\ \Omega$)
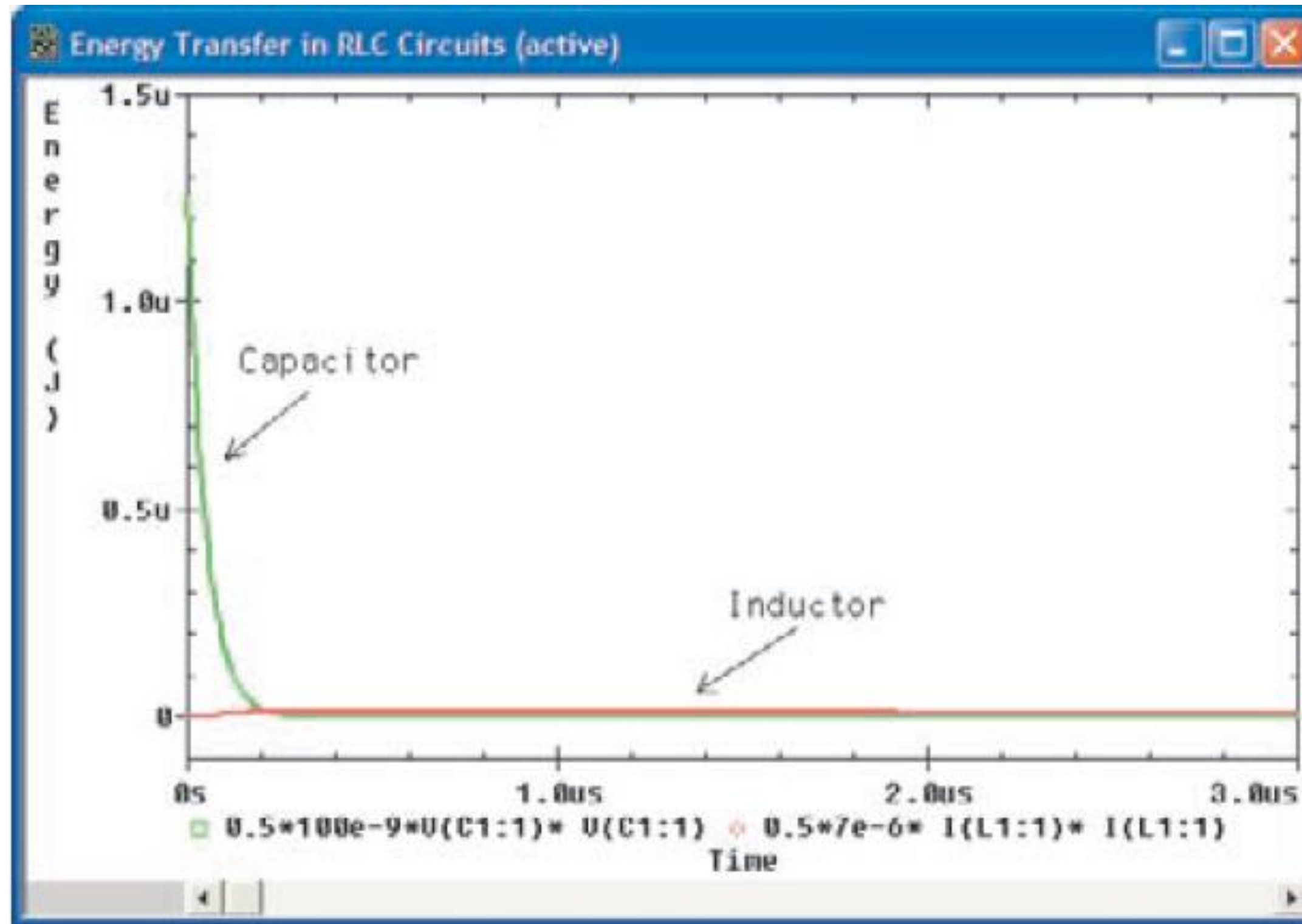
$$C = 100\text{ nF}, L = 7\ \mu\text{H}$$



نوع	وضعیت	شرط	α	ω_0	فرم پاسخ طبیعی
موازی	Overdamped	$\alpha > \omega_0$	$\frac{1}{2RC}$	$\frac{1}{\sqrt{LC}}$	$A_1 e^{s_1 t} + A_2 e^{s_2 t}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
سری			$\frac{R}{2L}$		
موازی	Critically damped	$\alpha = \omega_0$	$\frac{1}{2RC}$	$\frac{1}{\sqrt{LC}}$	$e^{-\alpha t} (A_1 t + A_2)$
سری			$\frac{R}{2L}$		
موازی	Underdamped	$\alpha < \omega_0$	$\frac{1}{2RC}$	$\frac{1}{\sqrt{LC}}$	$e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$
سری			$\frac{R}{2L}$		

The Complete response

The response of RLC circuits with DC sources and switches will consist of the natural response and the forced response:

$$v(t) = v_f(t) + v_n(t)$$

The complete response must satisfy both the initial conditions $v(0^+)$ and $\frac{dv}{dt}(0^+)$ or the forced response.

For example in the presence of DC sources:

A natural response :

$$v_n(t) = Ae^{s_1 t} + Be^{s_2 t}$$

Full answer:


$$v(t) = K + Ae^{s_1 t} + Be^{s_2 t}$$

Applying the basic conditions:

$$v(0^+) = V_f + A + B, \quad \frac{dv}{dt}(0^+) = As_1 + Bs_2$$

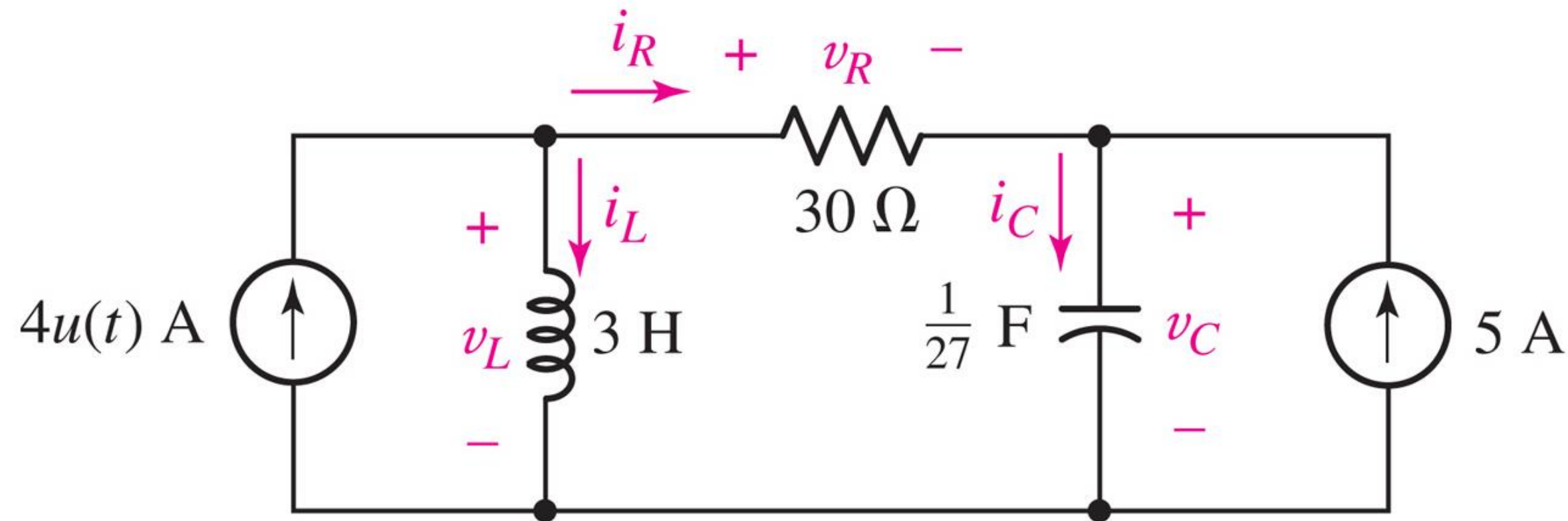Example: Initial Conditions

Find the labeled voltages and currents at $t=0^-$ and $t=0^+$.



Answer:

$$i_R(0^-) = -5\text{ A}$$

$$v_R(0^-) = -150\text{ V}$$

$$i_R(0^+) = -1\text{ A}$$

$$v_R(0^+) = -30\text{ V}$$

$$i_L(0^-) = 5\text{ A}$$

$$v_L(0^-) = 0\text{ V}$$

$$i_L(0^+) = 5\text{ A}$$

$$v_L(0^+) = 120\text{ V}$$

$$i_C(0^-) = 0\text{ A}$$


$$v_C(0^-) = 150\text{ V}$$

$$i_C(0^+) = 4\text{ A}$$

$$v_C(0^+) = 150\text{ V}$$

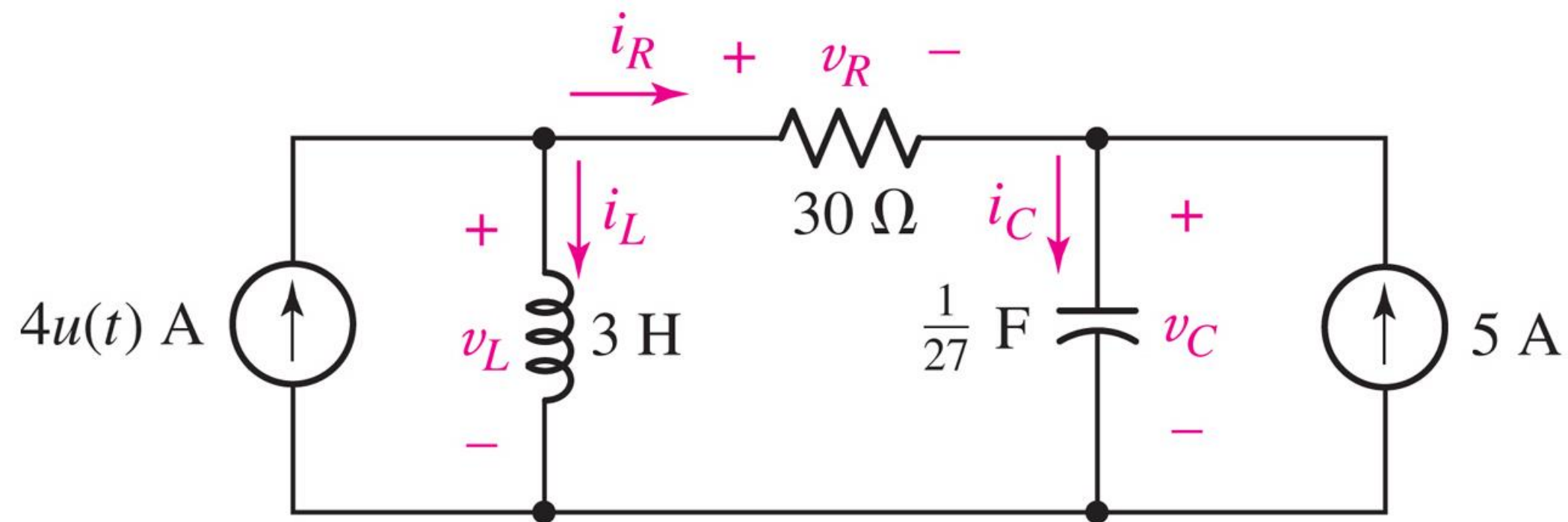Example: Initial Slopes

Find the first derivatives of the labeled voltages and currents at $t=0^+$.



Answer:

$$di_R/dt(0^+) = -40 \text{ A/s}$$

$$dv_R/dt(0^+) = -1200 \text{ V/s}$$

$$di_L/dt(0^+) = 40 \text{ A/s}$$

$$dv_L/dt(0^+) = -1092 \text{ V/s}$$


$$di_C/dt(0^+) = -40 \text{ A/s}$$

$$dv_C/dt(0^+) = 108 \text{ V/s}$$

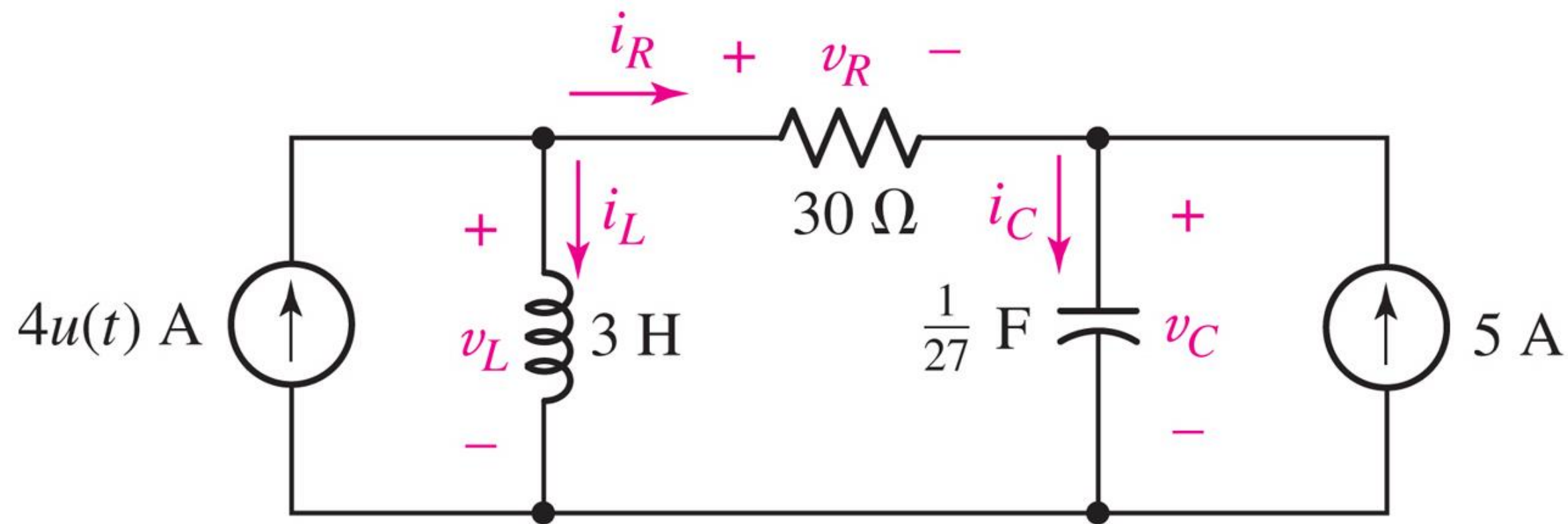Example: Complete Response

Show that for $t > 0$

$$v_C(t) = 150 + 13.5(e^{-t} - e^{-9t}) \text{ volts}$$




The Lossless LC Circuit

- The resistor in the RLC circuit serves to dissipate initial stored energy.
- When this resistor becomes 0 in the series RLC or infinite in the parallel RLC, the circuit will oscillate.

Example: for $t > 0$, if $i(0) = -1/6$ A and $v(0) = 0$ V


$$v(t) = 2 \sin 3t$$

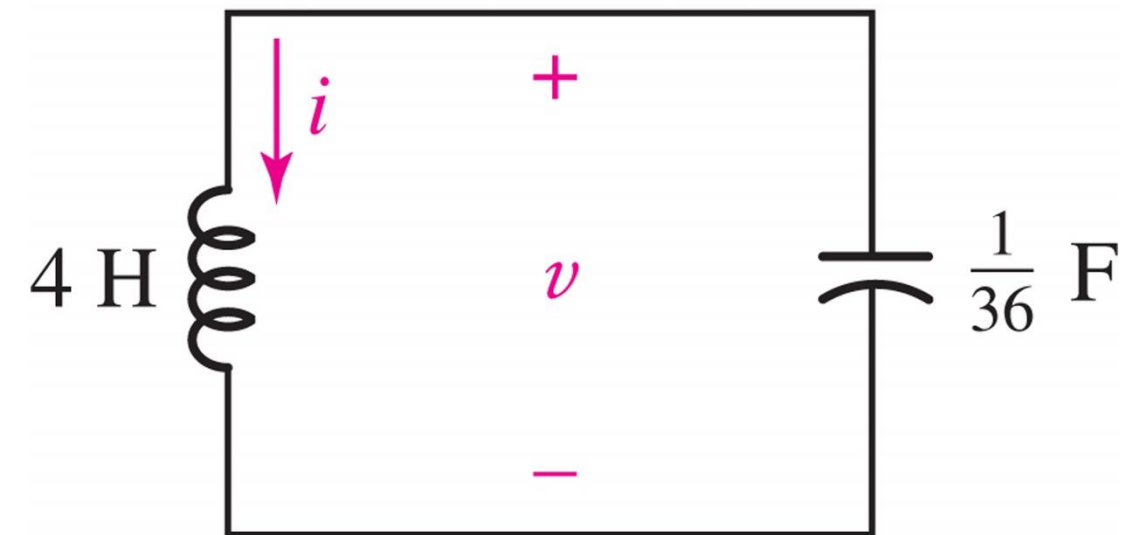

Practice 1

Show that:


$$v_C(t) = -e^{-0.8t}(5 \cos 9.97t + 0.4 \sin 9.97t)V$$

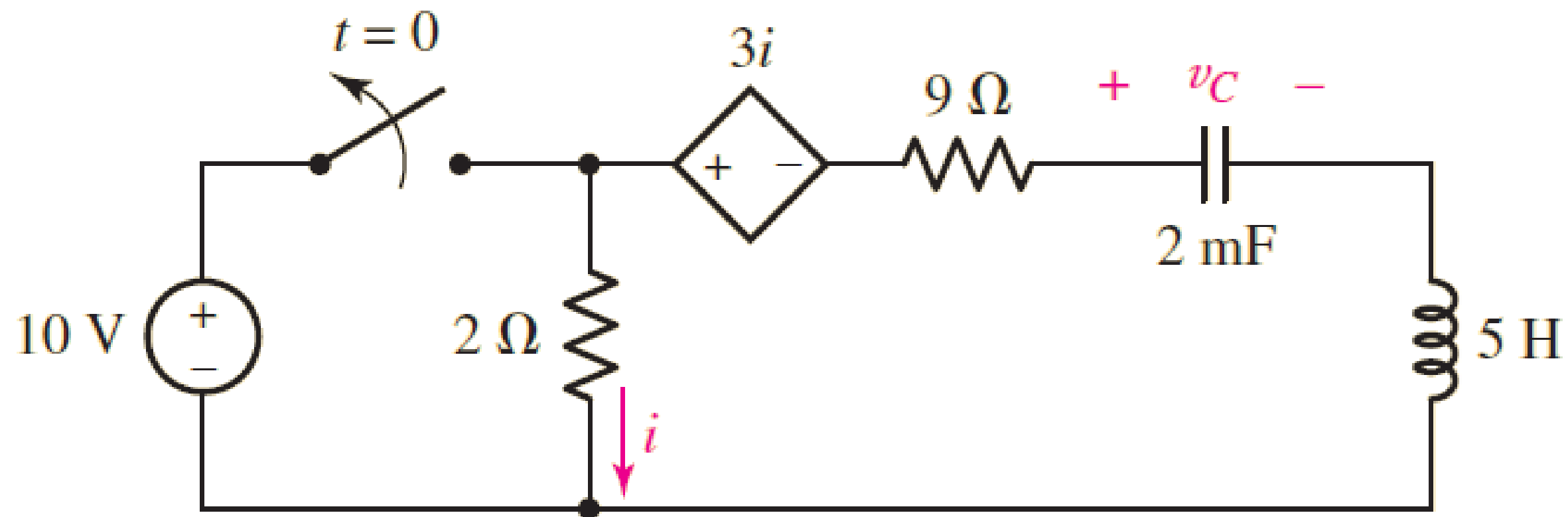

Practice 2


The key is closed at time $t=0$. Find R , L and C such that:

$$v(t) = 5e^{-400t}\cos(300t)$$

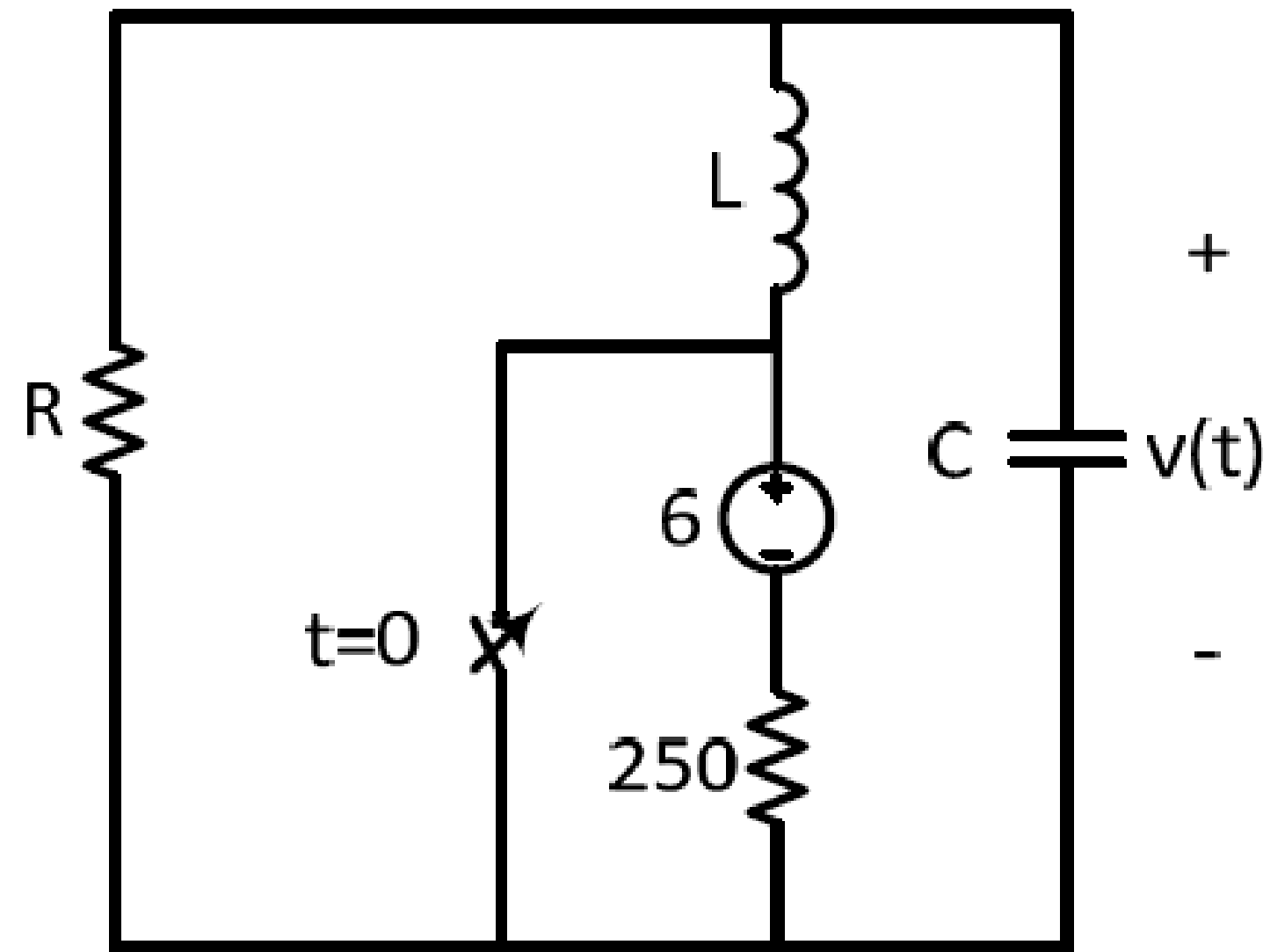

Practice 3

Find $v_C(t)$.

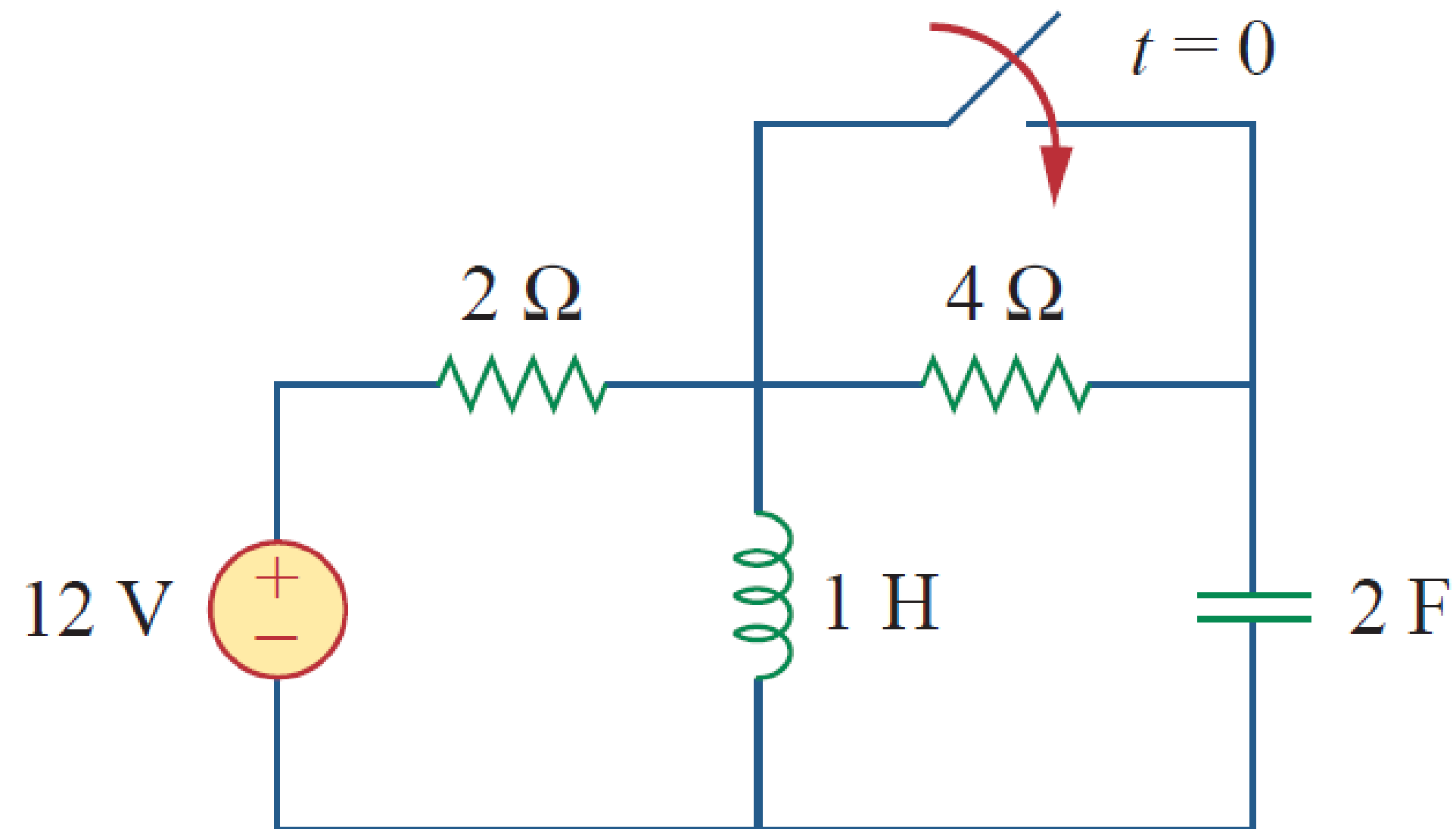



Thanks
