



دانشگاه صنعتی امیر کبیر  
( پلی تکنیک تهران )

# Electrical and Electronic Circuits

## chapter 10. Diodes

Afarghadan@aut.ac.ir


عظیم فرقدان 

مهر ۱۴۰۳

# Objectives of the Lecture


- Introduction to Diodes and Their Applications
- Voltage-Current Characteristics of Diodes and Their Models
- Analysis of Diode Circuits

# semiconductor

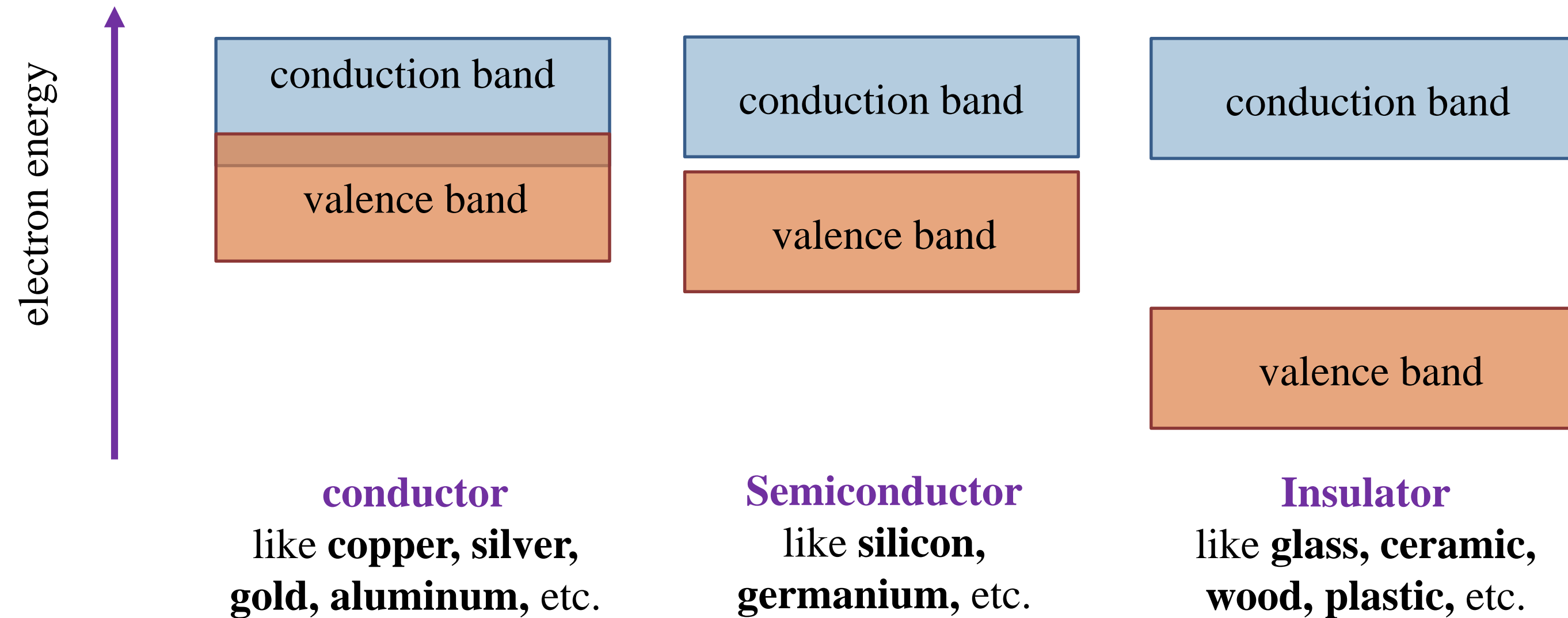

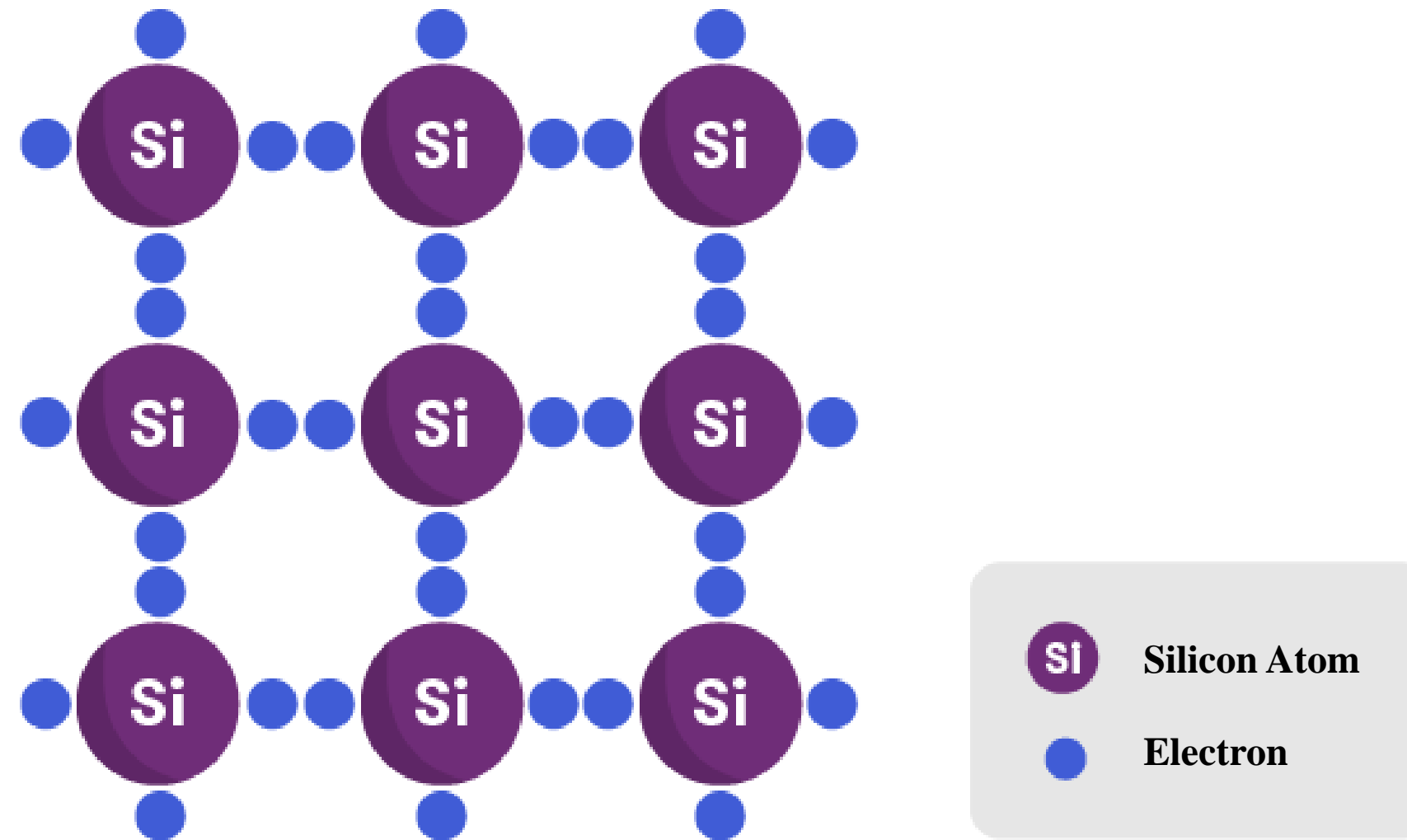
## ➤ Atomic Structure

- Contains 4 electrons in the valence shell



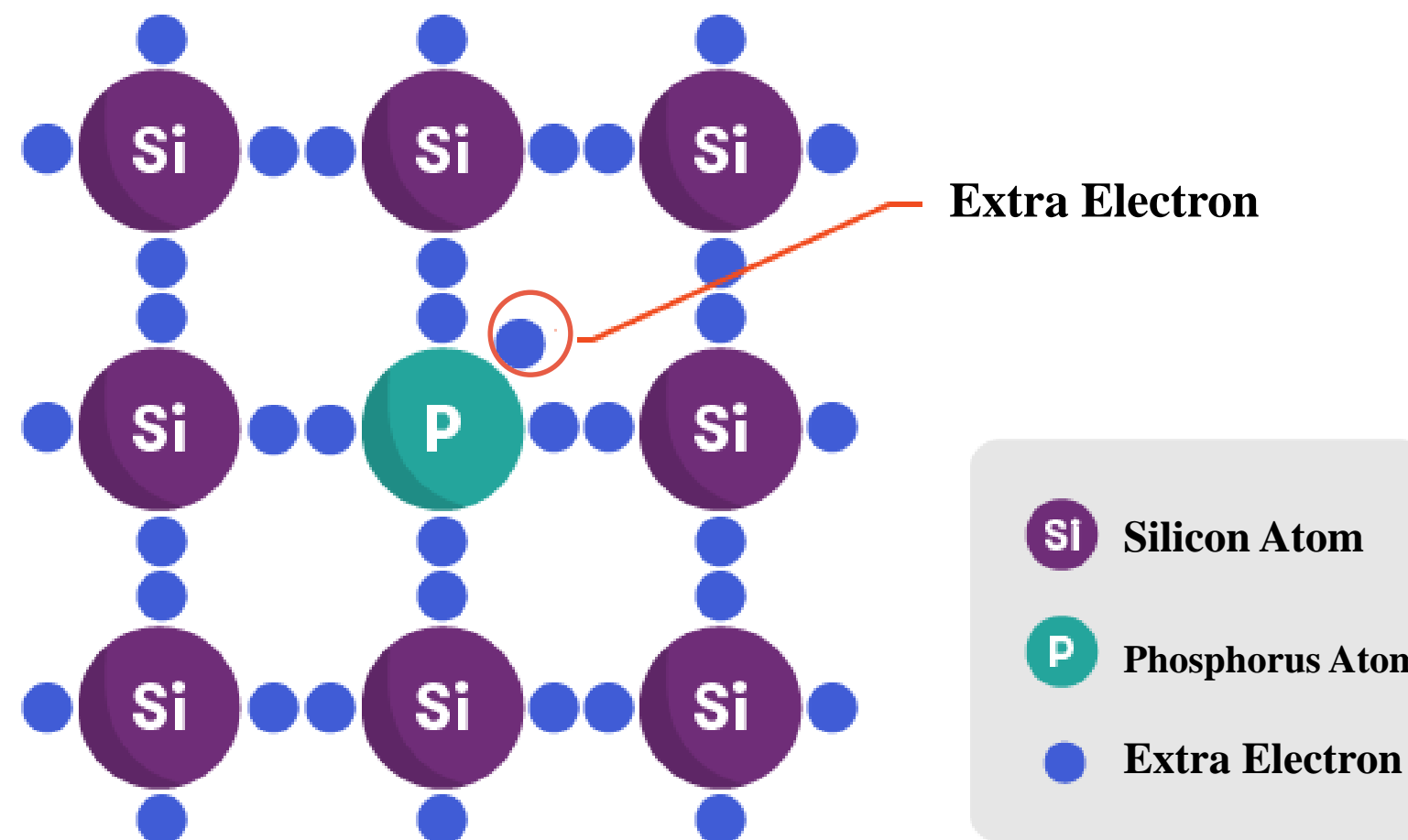
# N-Type Semiconductor

- ✓ In an **N-type semiconductor**, several phosphorus atoms replace silicon atoms.
- ✓ A phosphorus atom has **5 electrons in its valence shell**, so one electron can move freely.




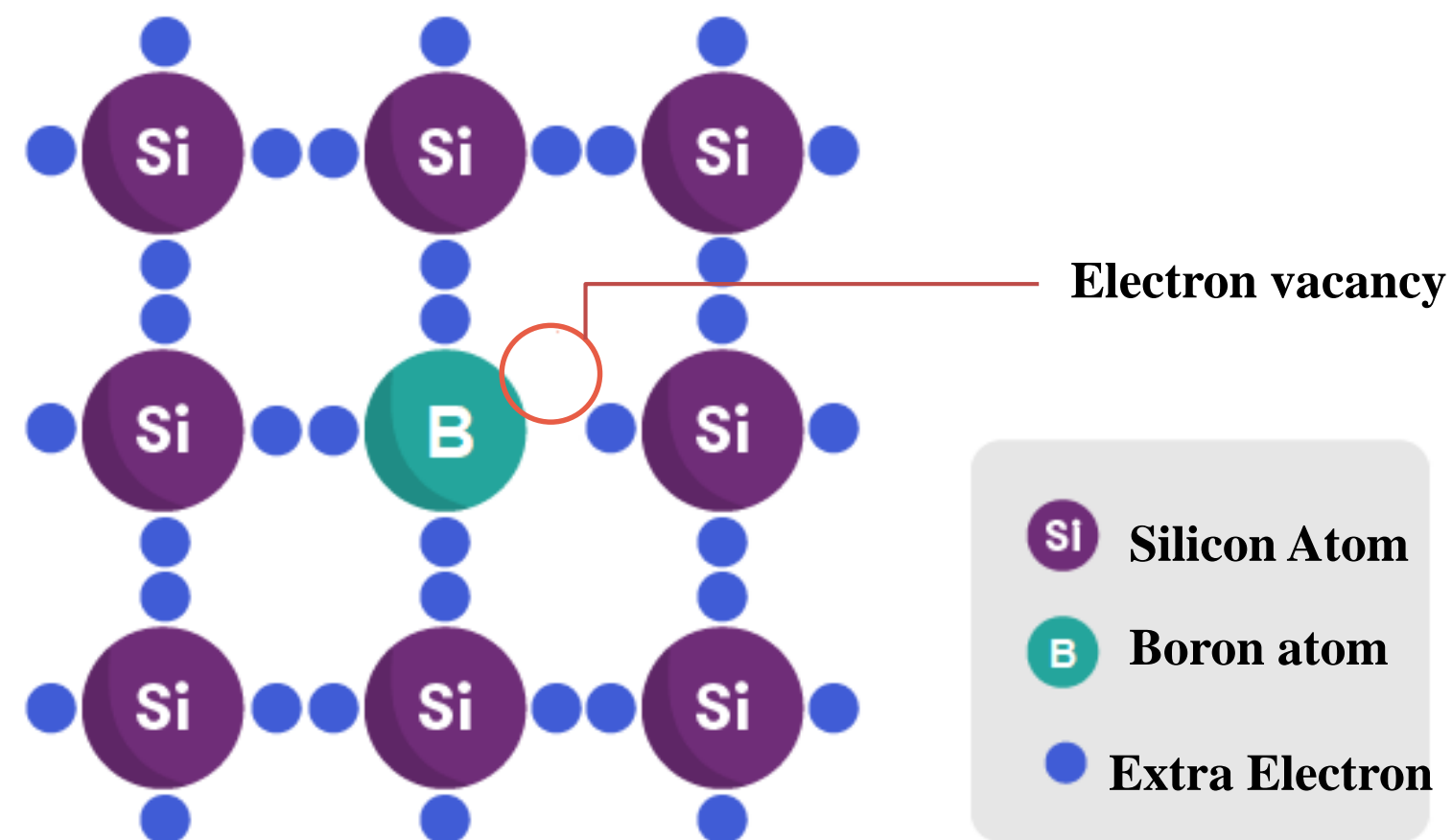
# P-type semiconductor

- ✓ In a p-type semiconductor, some boron atoms are substituted for silicon atoms.
- ✓ A boron atom has 3 electrons in its valence shell, resulting in a vacancy for one electron.



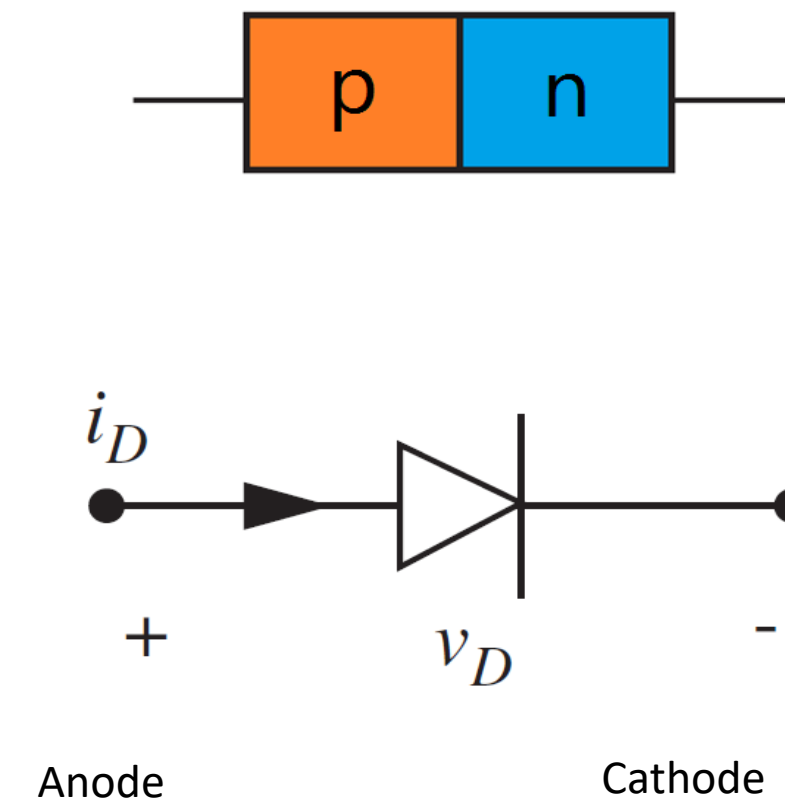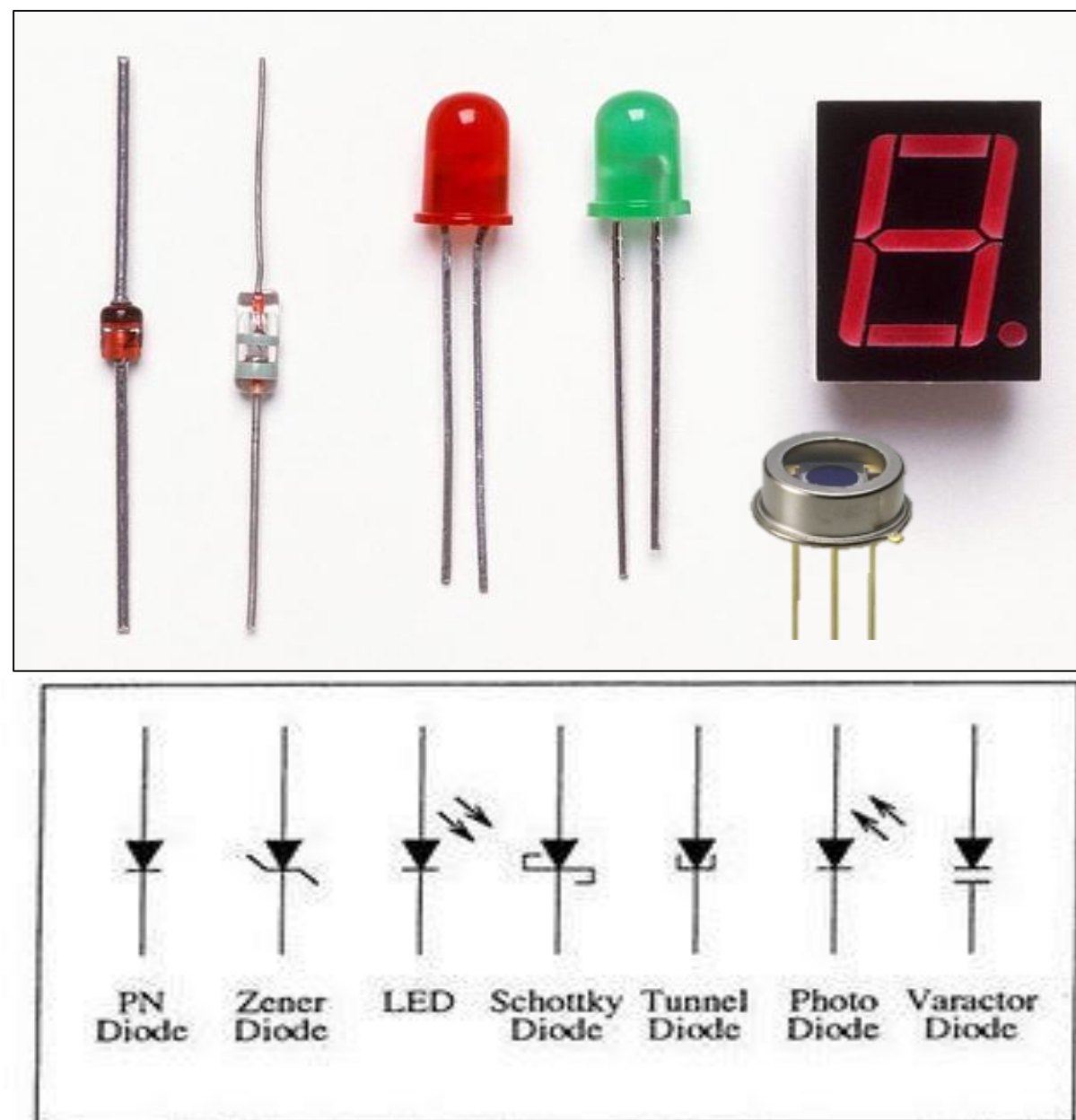
# Diode

- A PN diode is a device formed by the junction of **p-type** and **n-type** semiconductors.




## ➤ Rectifier Circuit

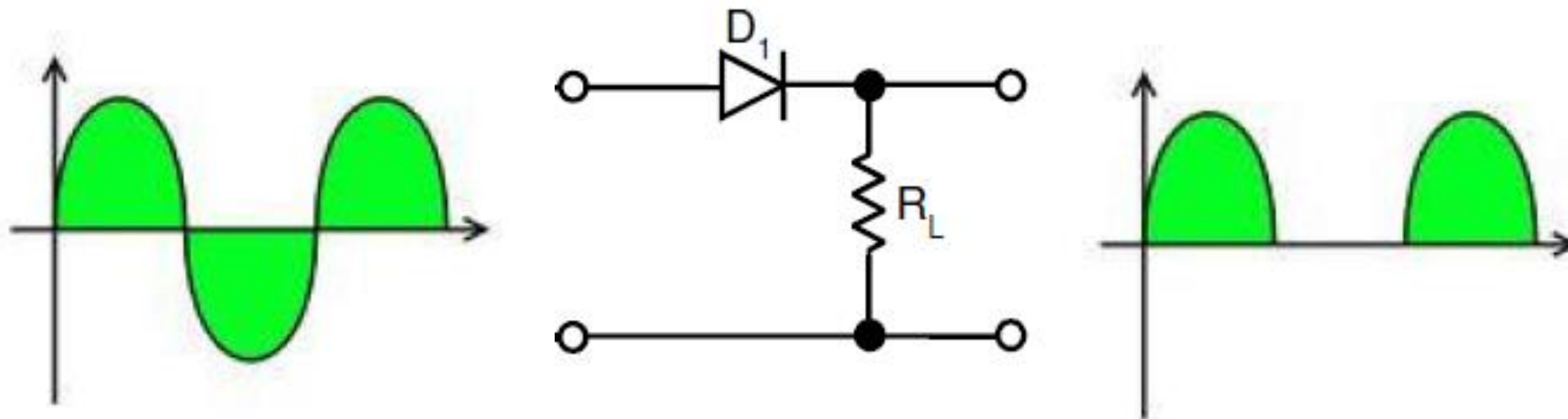





## ➤ Peak detector

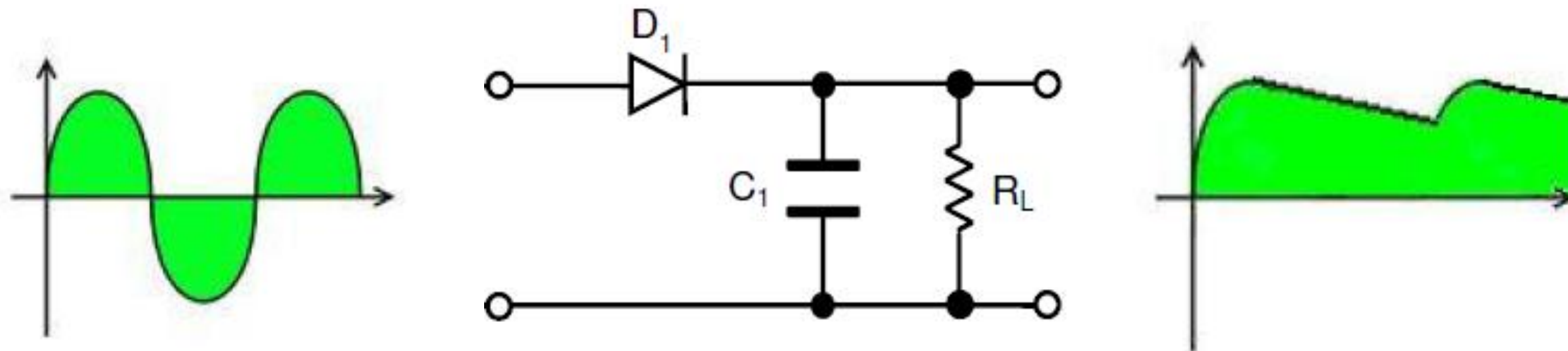


Example: For converting an AC wave to DC.

## ➤ Clamper Circuit

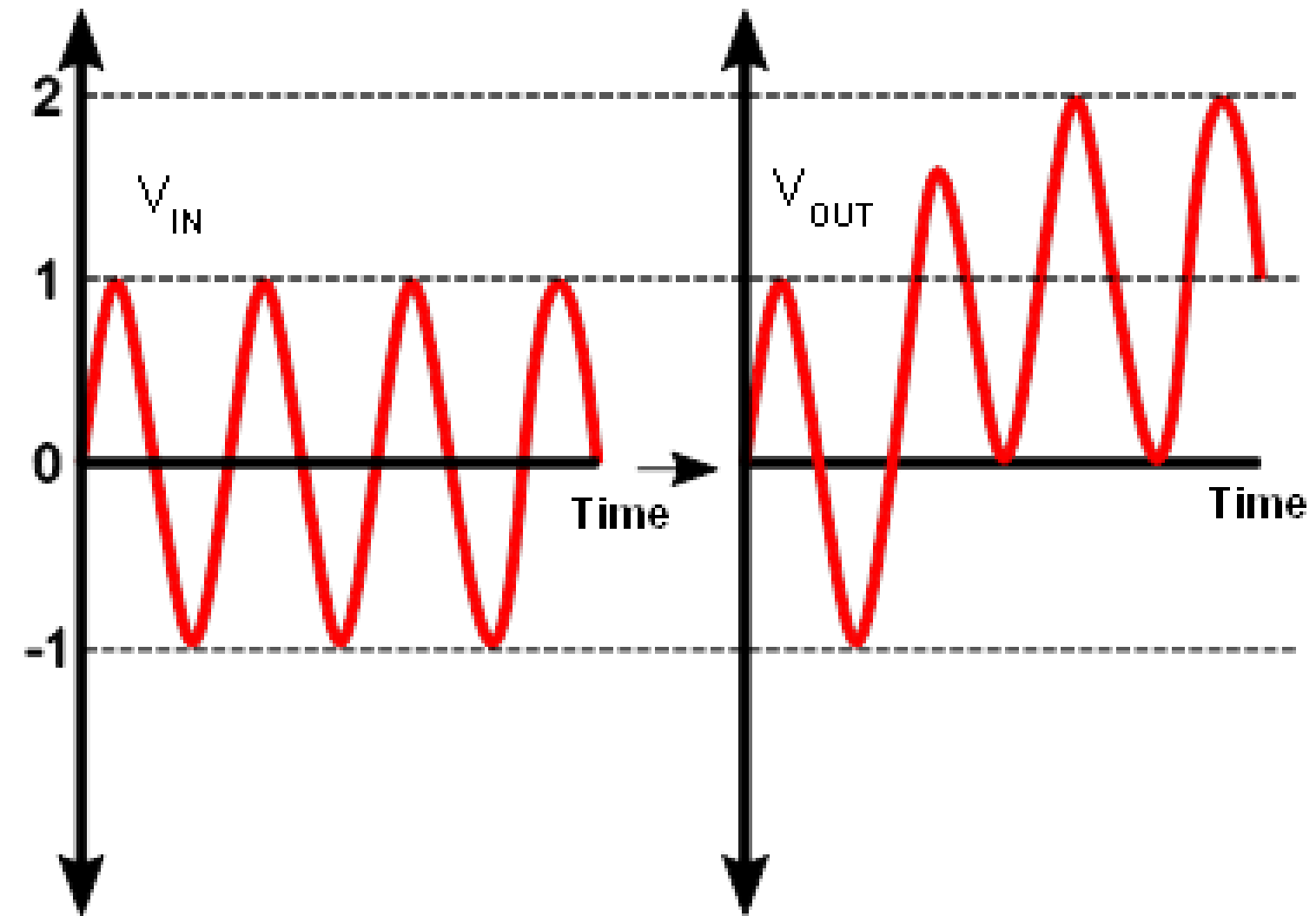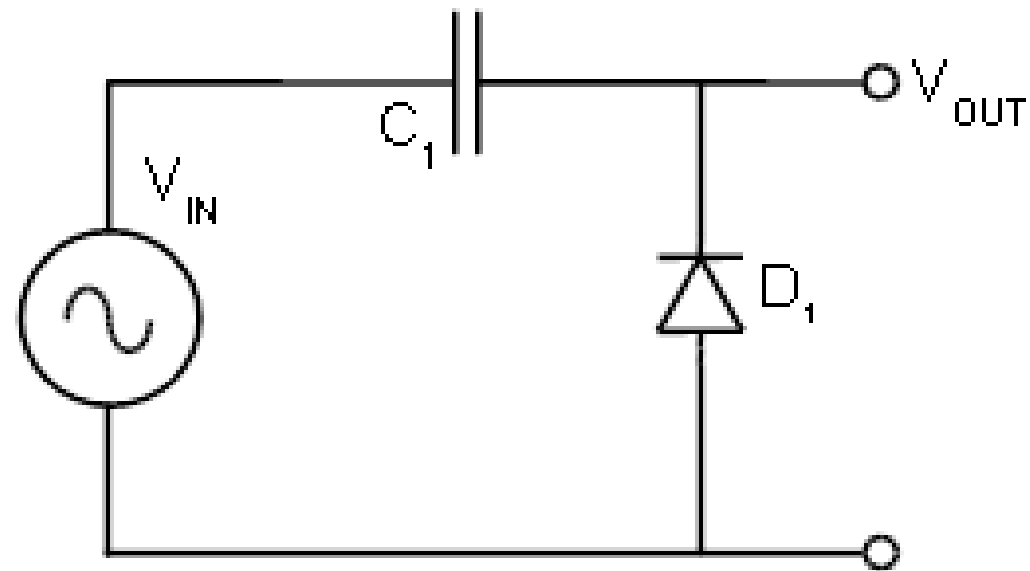




Example: For voltage multiplication.

## ➤ Clipper/Limiter Circuit

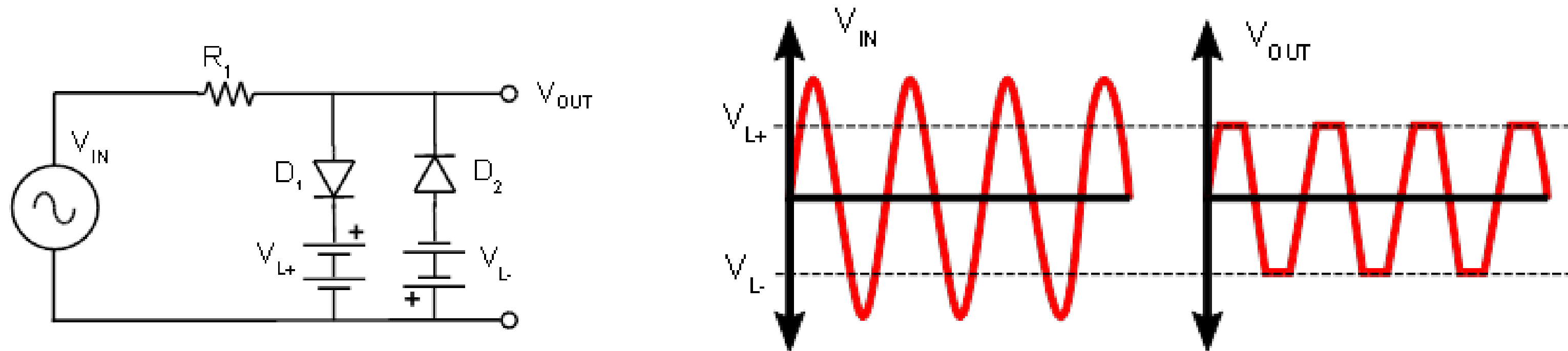


Example: For removing noise spikes.


## ➤ Voltage Regulator

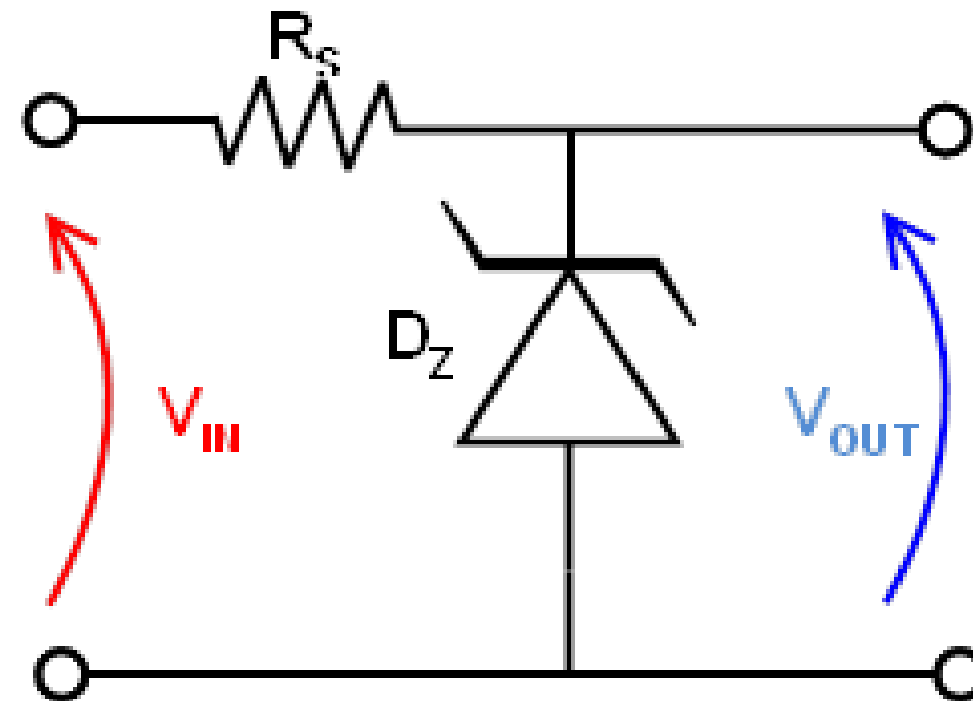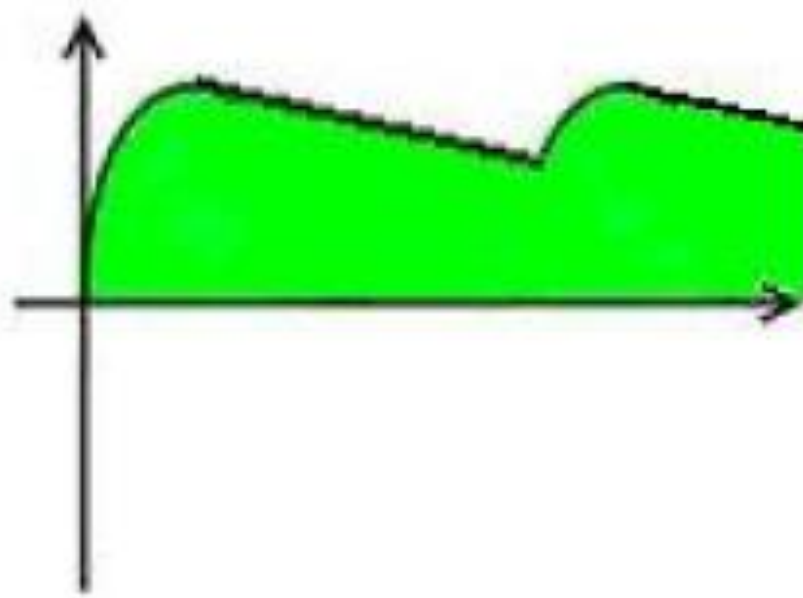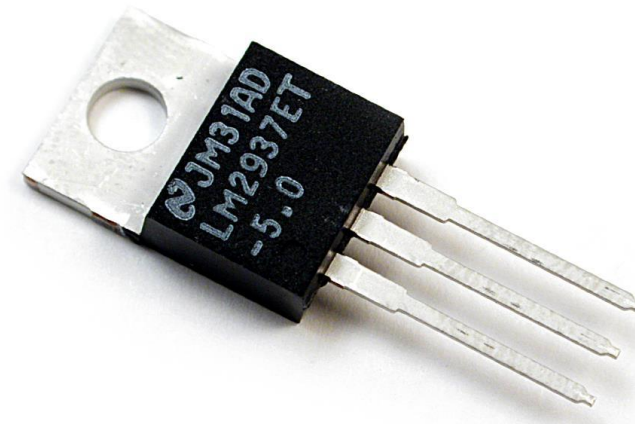

## ➤ Infrared Transmitter/Receiver


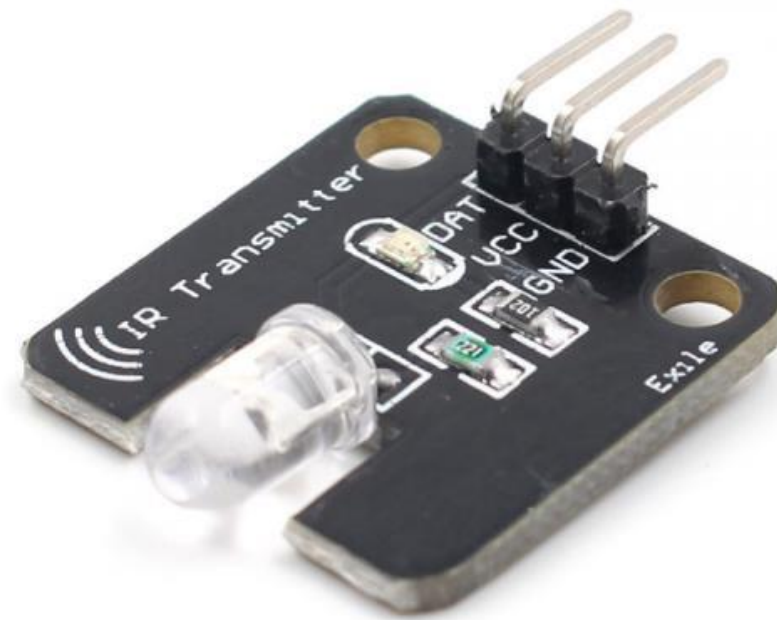


Light Emitting  
Diode (LED)

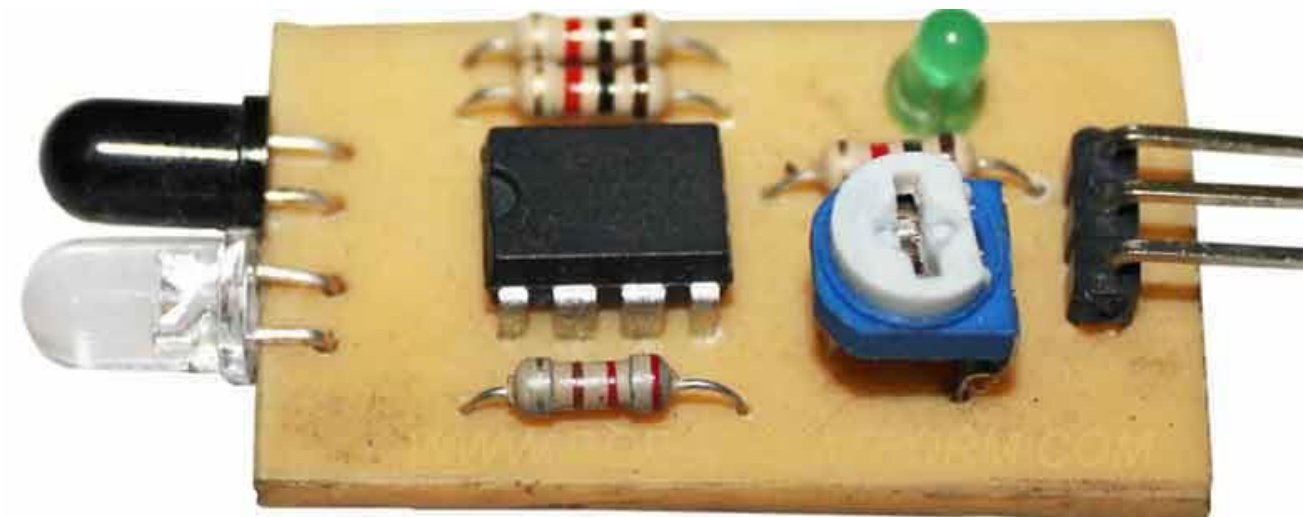


IR SENSOR (TRANSCEIVER)


➤ For constructing logic gates.

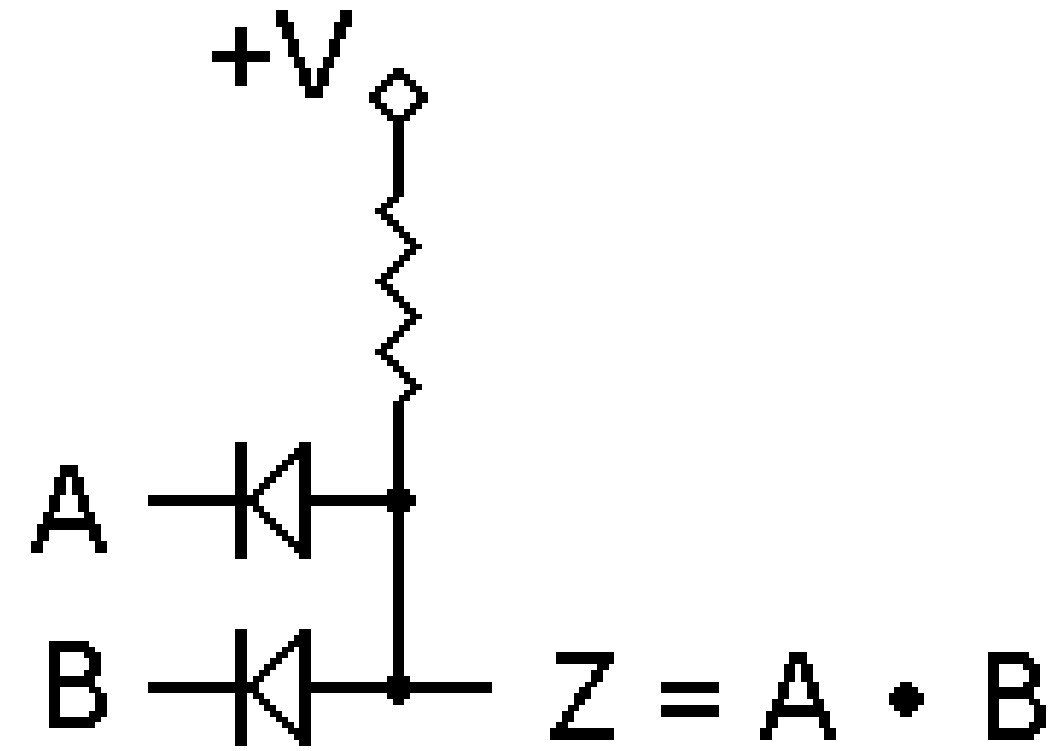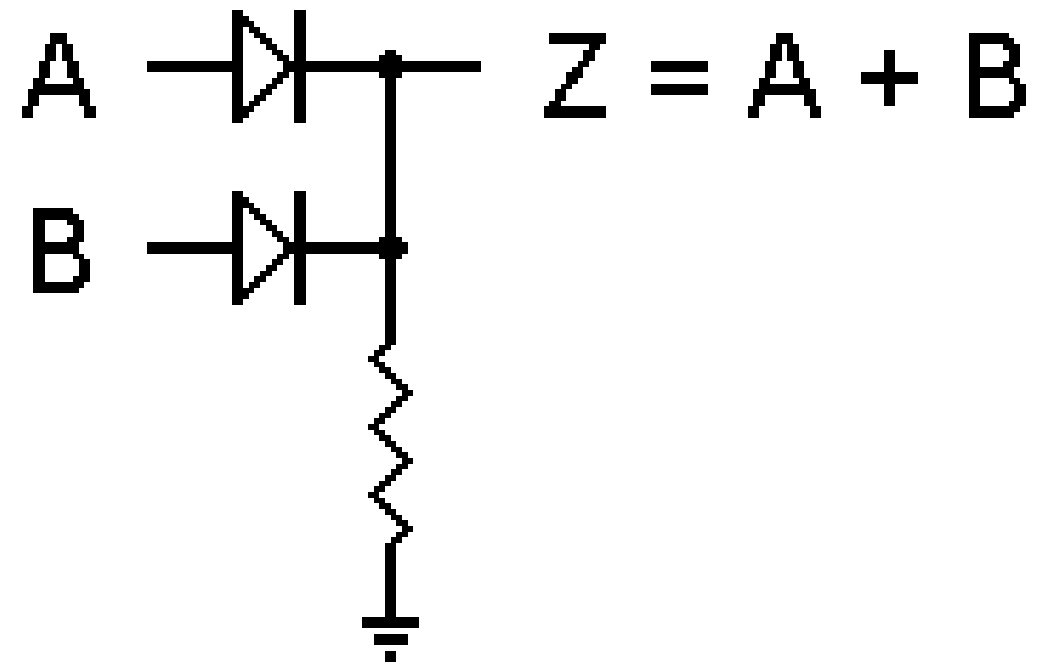


# Voltage-Current Characteristic

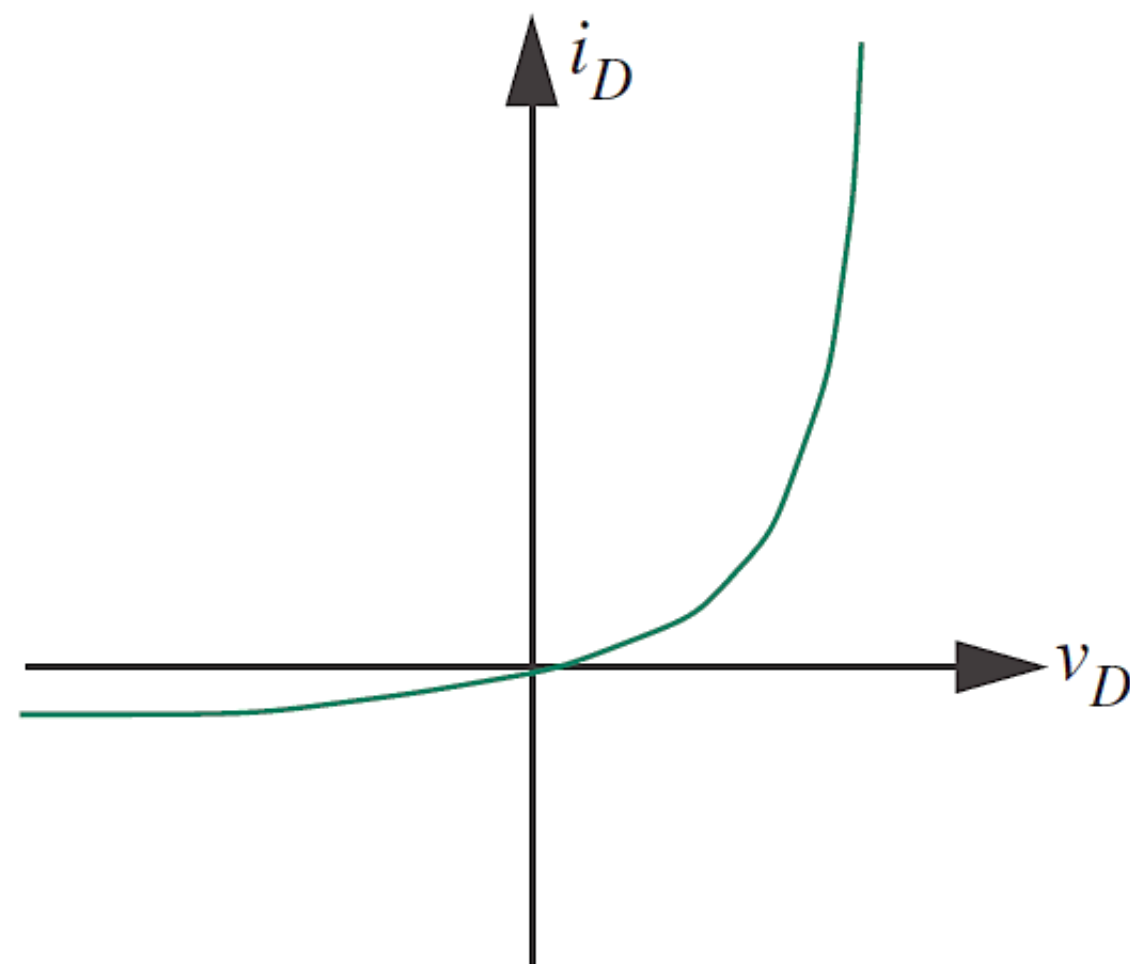

PN Diode


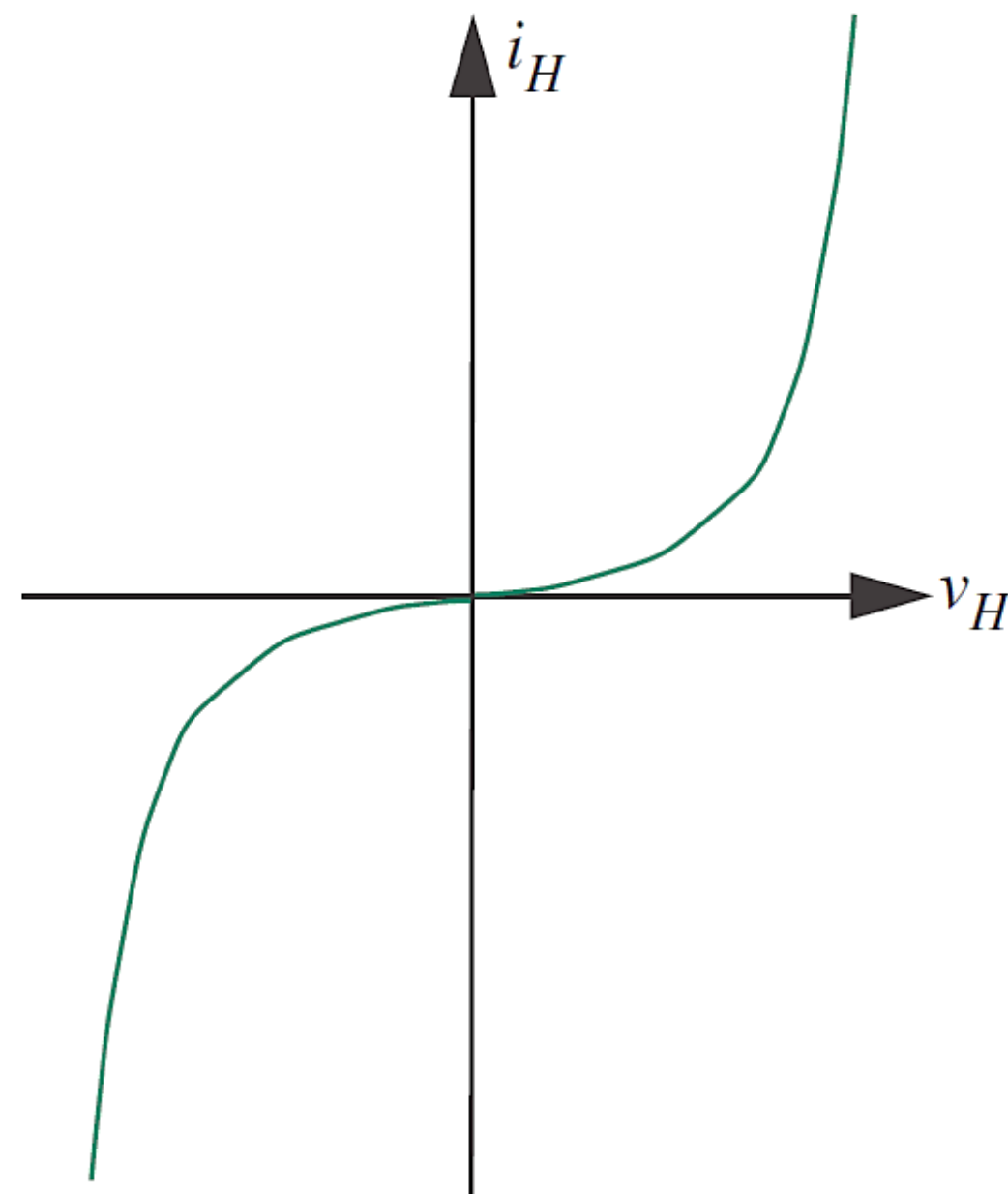


Zener Diode

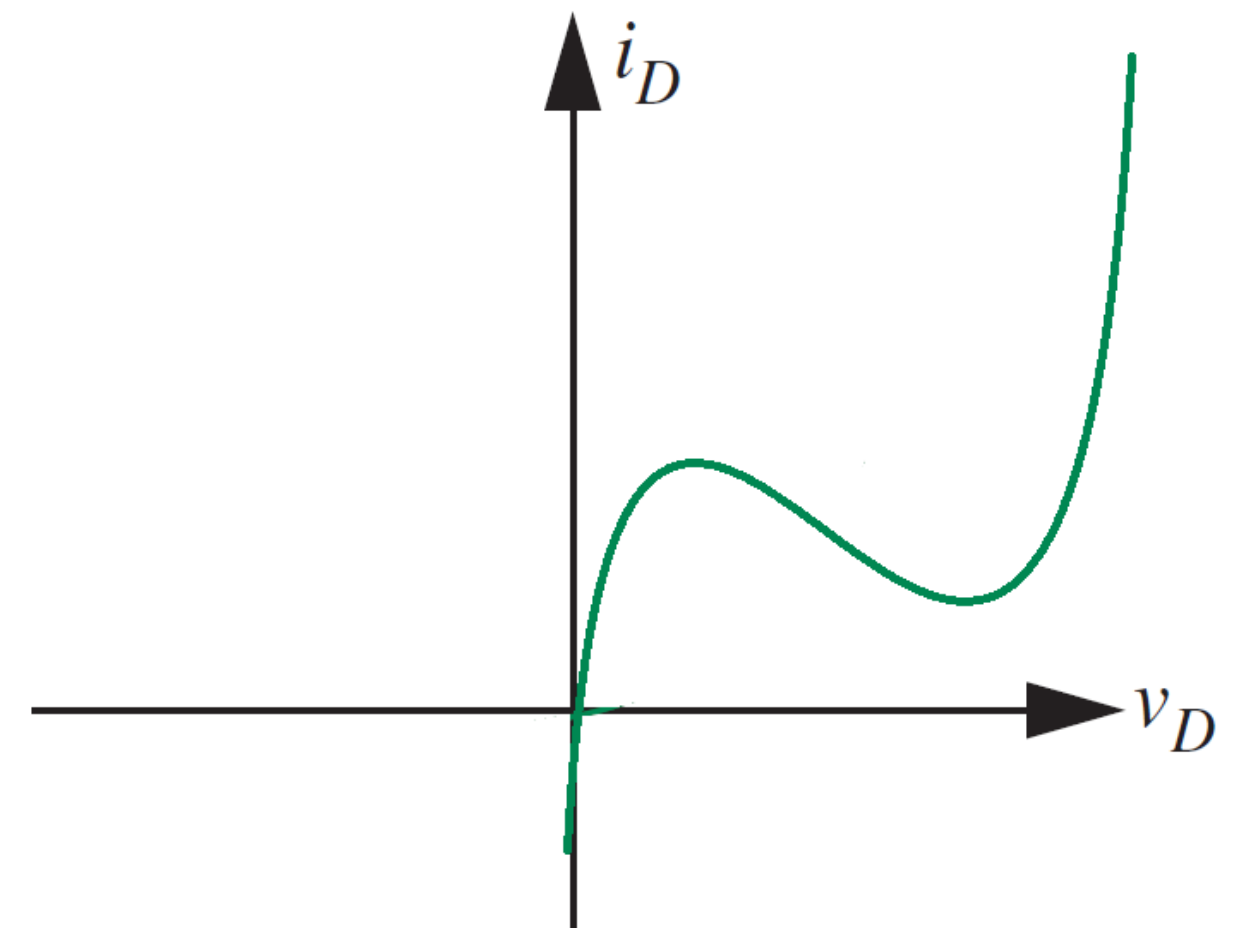

Tunnel Diode

## ❖ Exact Model

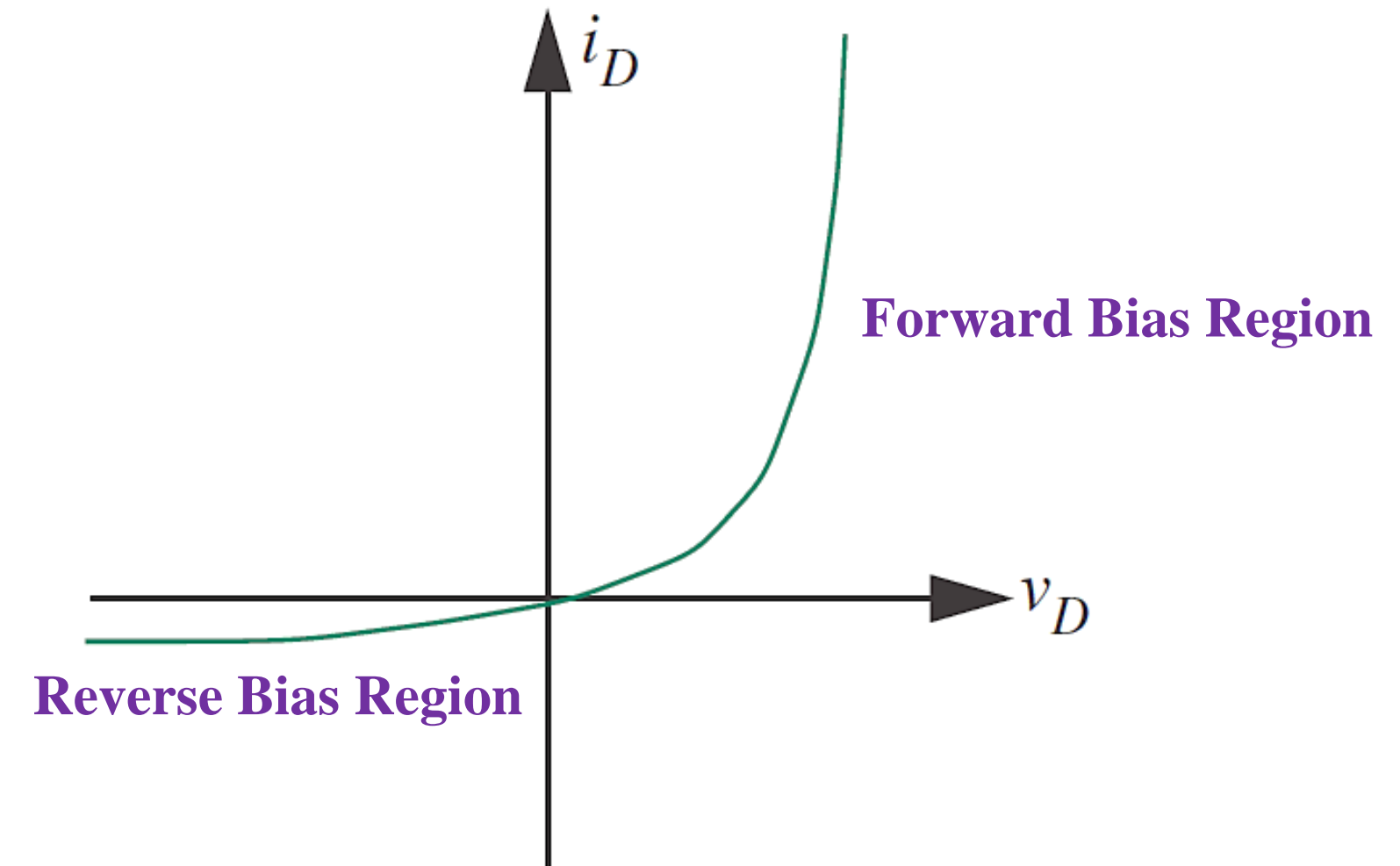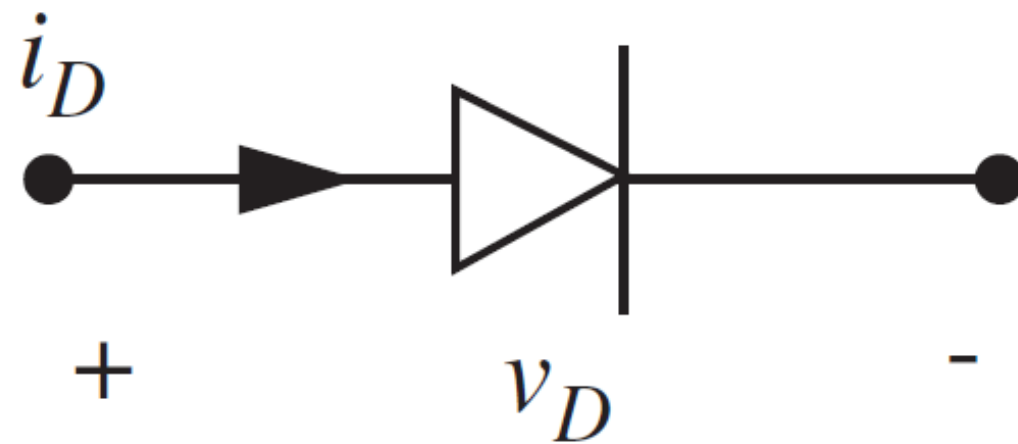

$$i_D = I_s (e^{v_D/v_T} - 1)$$

Saturation Current  $\approx 10^{-12}$


Thermal Voltage  $\approx 25\text{mV}$


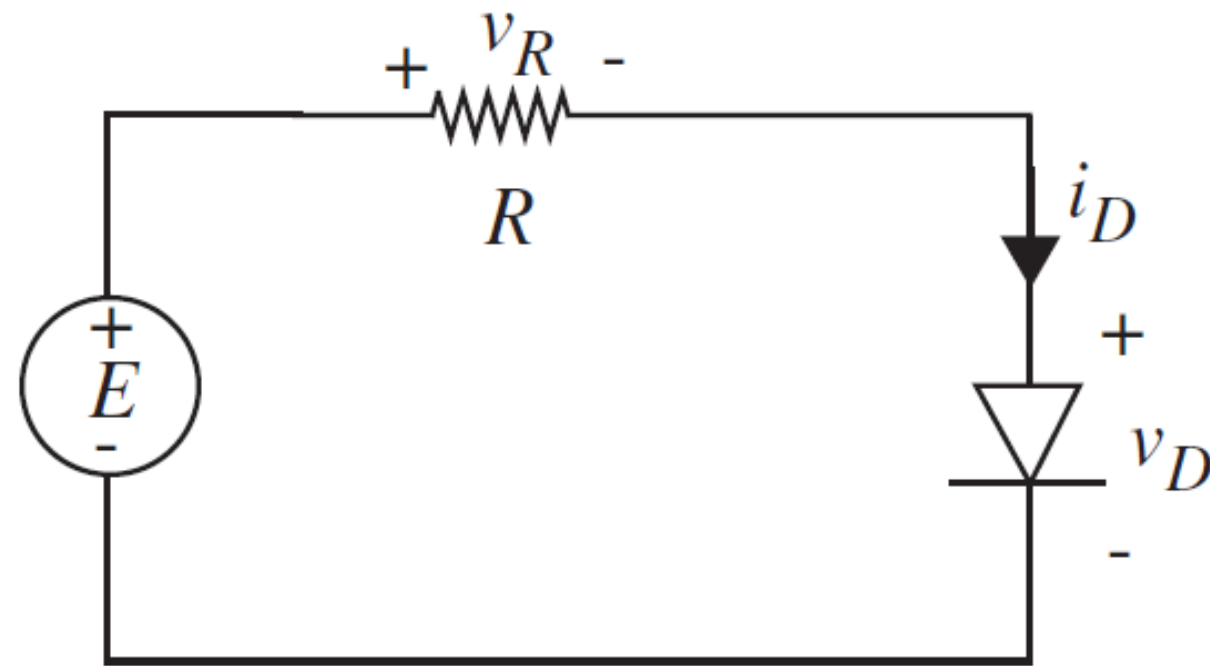
# Example


- Find the values of  $i_D$  and  $v_D$ .

By applying Kirchhoff's Voltage Law (KVL), we have:




$$-E + Ri_D + v_D = 0$$

$$i_D = I_s (e^{v_D/v_T} - 1)$$

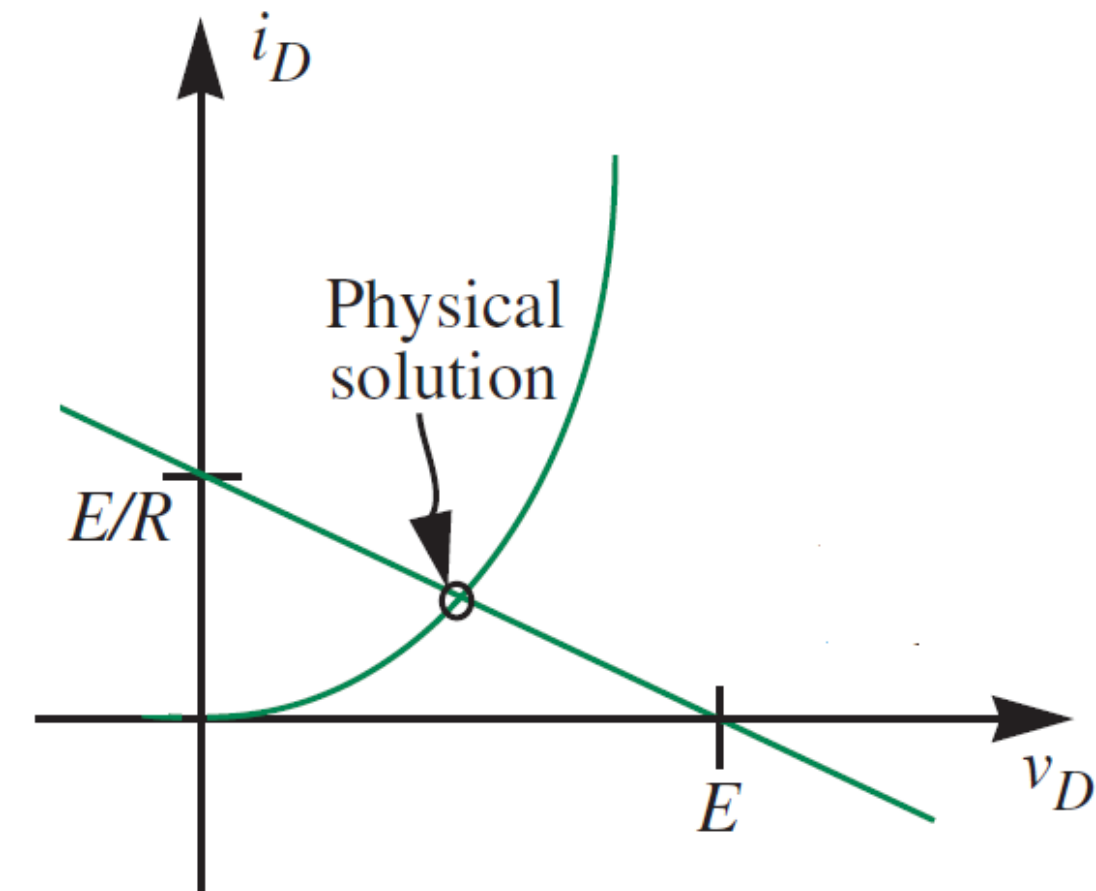


- ✓ The exact model complicates the analysis.
- ✓ Simpler models are needed.

## ➤ Ideal Model

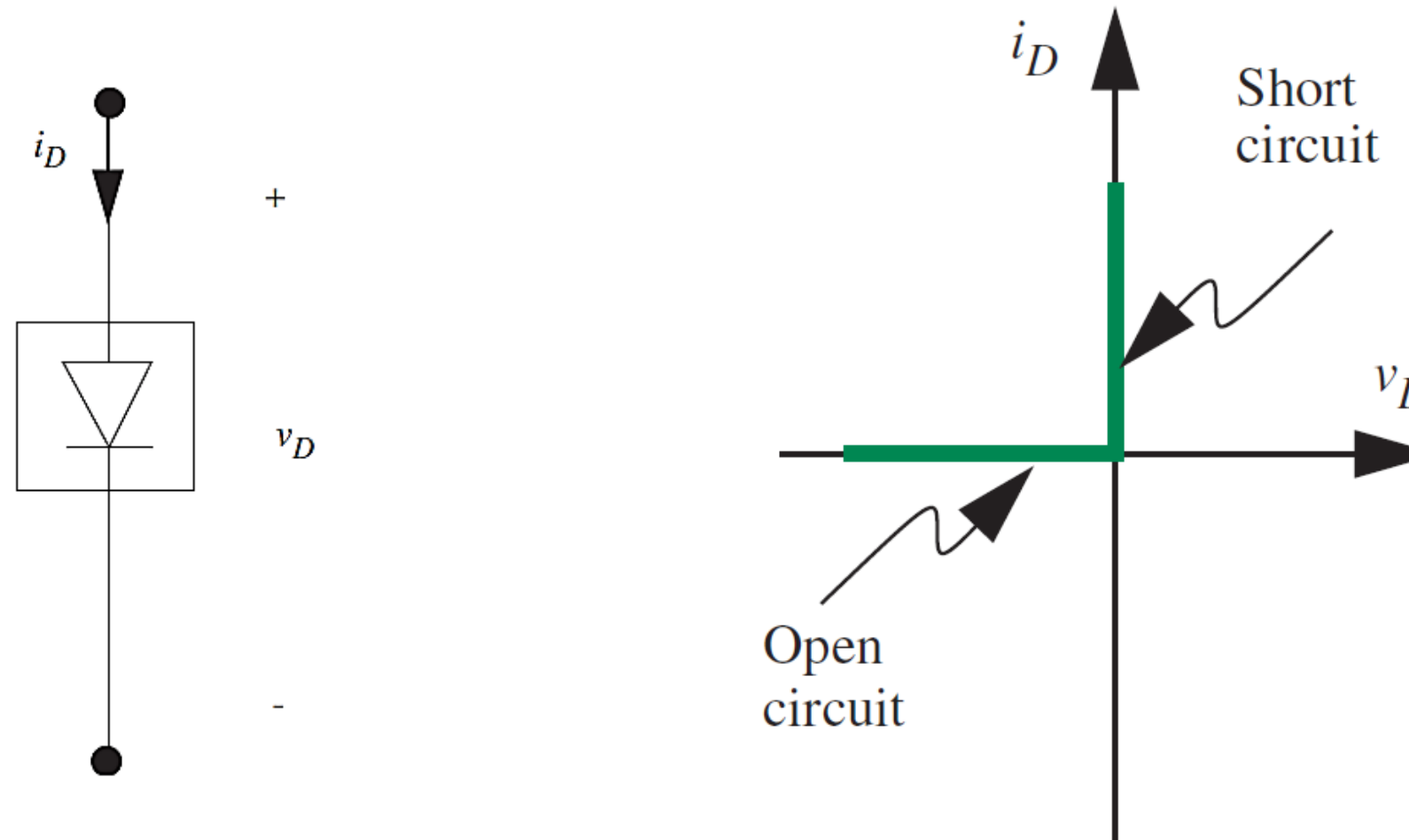

- ✓ The diode is always in one of the two following states:
- ✓ **On:** ( $v_D = 0, i_D > 0$ ) In this case, the diode behaves as a short circuit.
- ✓ **Off:** ( $i_D = 0, v_D < 0$ ) In this case, the diode behaves as an open circuit.

## ➤ Piecewise Linear

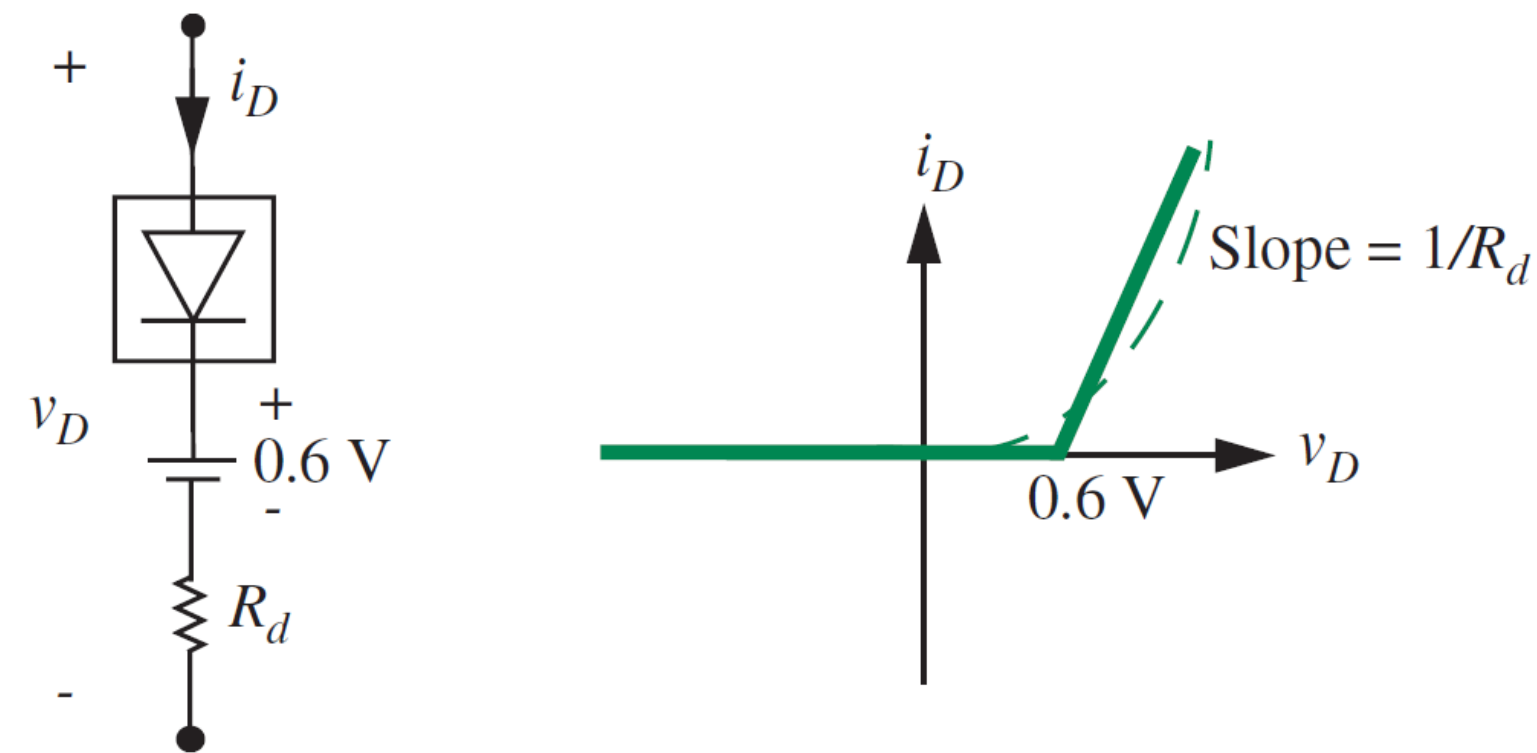

Threshold Voltage ( $v_{TH}$ )

- ✓ The diode is always in one of the two following states:
- ✓ **On:**  $v_D = R di_D + 0.6$ ,  $v_D > 0.6$ ,  $i_D > 0$
- ✓ **Off:**  $i_D = 0$ ,  $v_D < 0.6$

## ❖ Hypothetical Method

### 1. For each diode, assume it is either on or off.

- ✓ For each assumption, draw the corresponding circuit (there will be  $2^N$  possible states for N diodes).

### 2. Analyze one of the circuits:

- ✓ Select one circuit and perform the analysis based on the given assumptions.

### 3. Check the validity of assumptions:

- ✓ If the diode is assumed to be off, its voltage should be negative.
- ✓ If the diode is assumed to be on, its current should be positive.

### 4. Final verification:

- ✓ If all assumptions are correct, the analysis is complete.
- ✓ If any assumption is incorrect, revisit and check the assumption again (repeat step 2).

# Example 1

**Assume the Diode is Ideal, Find the Voltage  $v$**

**Assume the Diode is Off (Open Circuit)**


✓  $i_D = 0, v_D < 0$

✓  $v_D = 0.75V$  (The diode voltage is positive. **Contradiction!**)

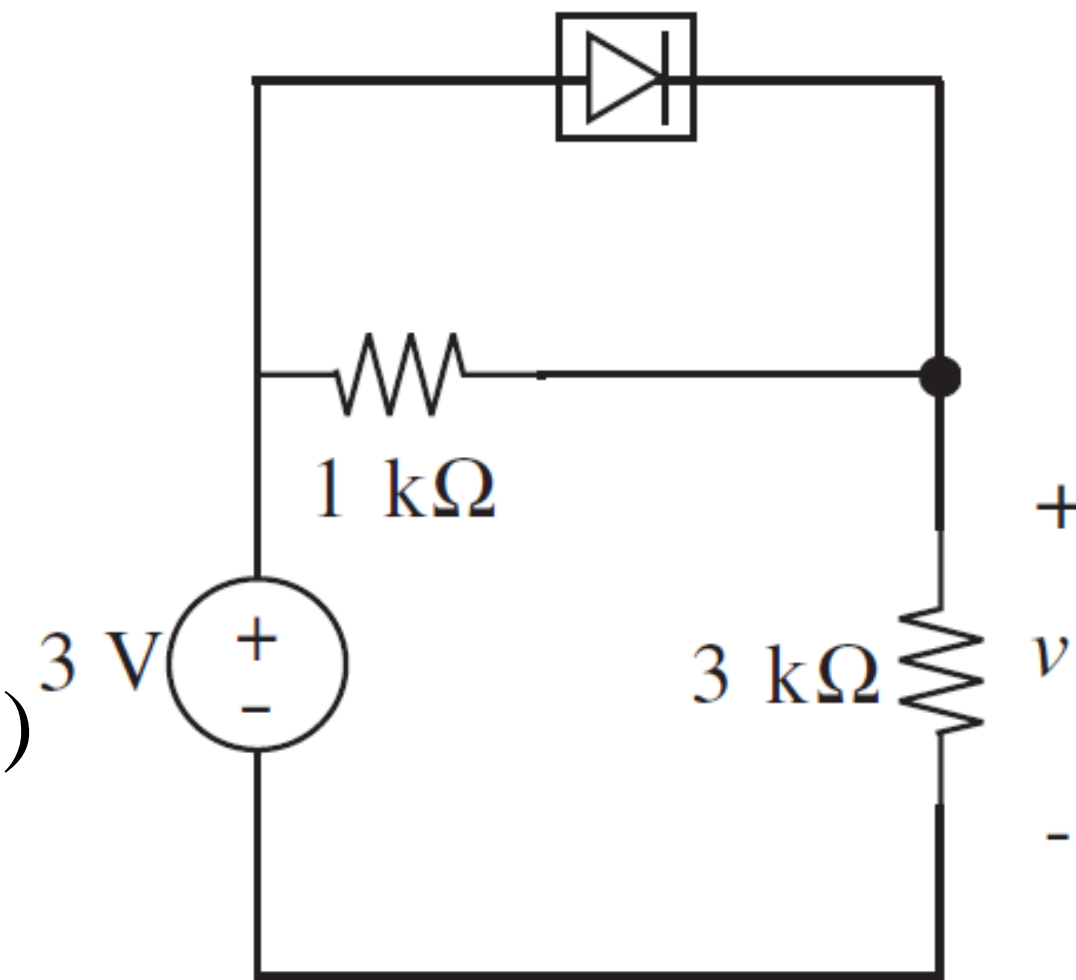**Assume the Diode is On (Short Circuit)**

✓  $v_D = 0, i_D > 0$

✓  $i_D = 1mA \rightarrow v = 3V$  (The diode current is positive. **Correct.**)



## Example 2

Assuming a piecewise-linear model, determine the voltage  $v$ .

✓  $R_d = 1, v_{TH} = 0.6$

Assume the diode is off (open circuit):


✓  $i_D = 0, v_D < 0.6$

✓  $v_D = 0.75V$  **(The diode voltage is positive. Contradiction!)**

Assume the diode is on (short circuit):


✓  $v_D = i_D + 0.6, i_D > 0, v_D > 0.6$

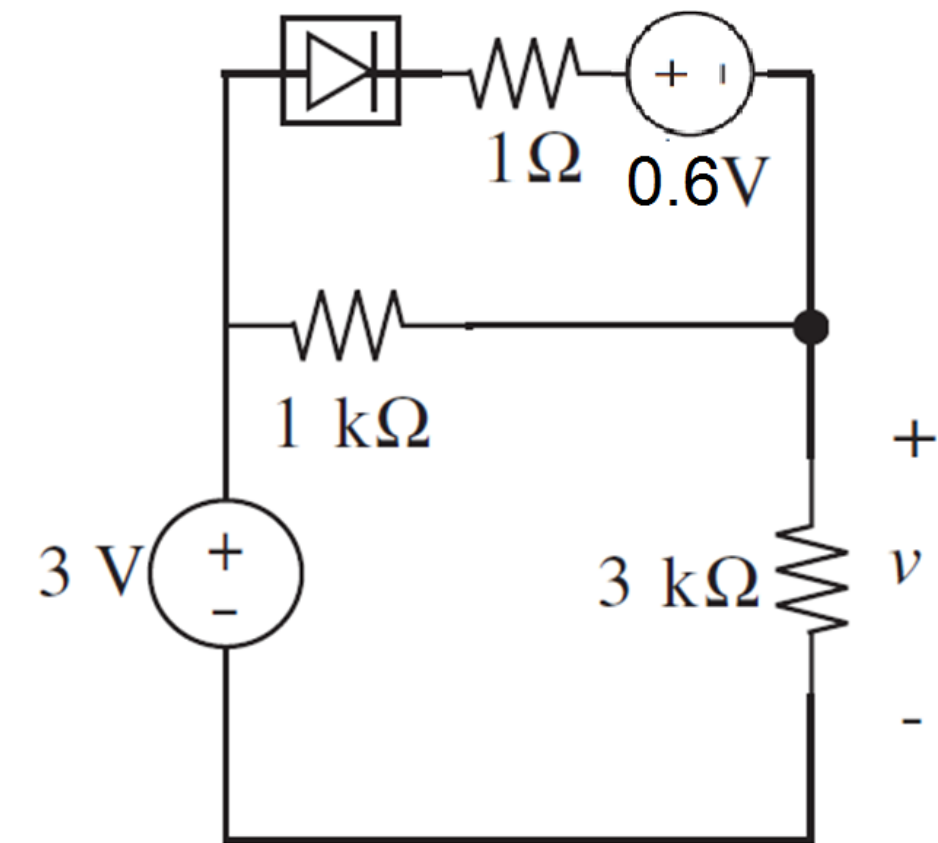✓  $i_D \approx 0.2mA \rightarrow v \approx 2.4V$  **(The diode current is positive. Correct.)**






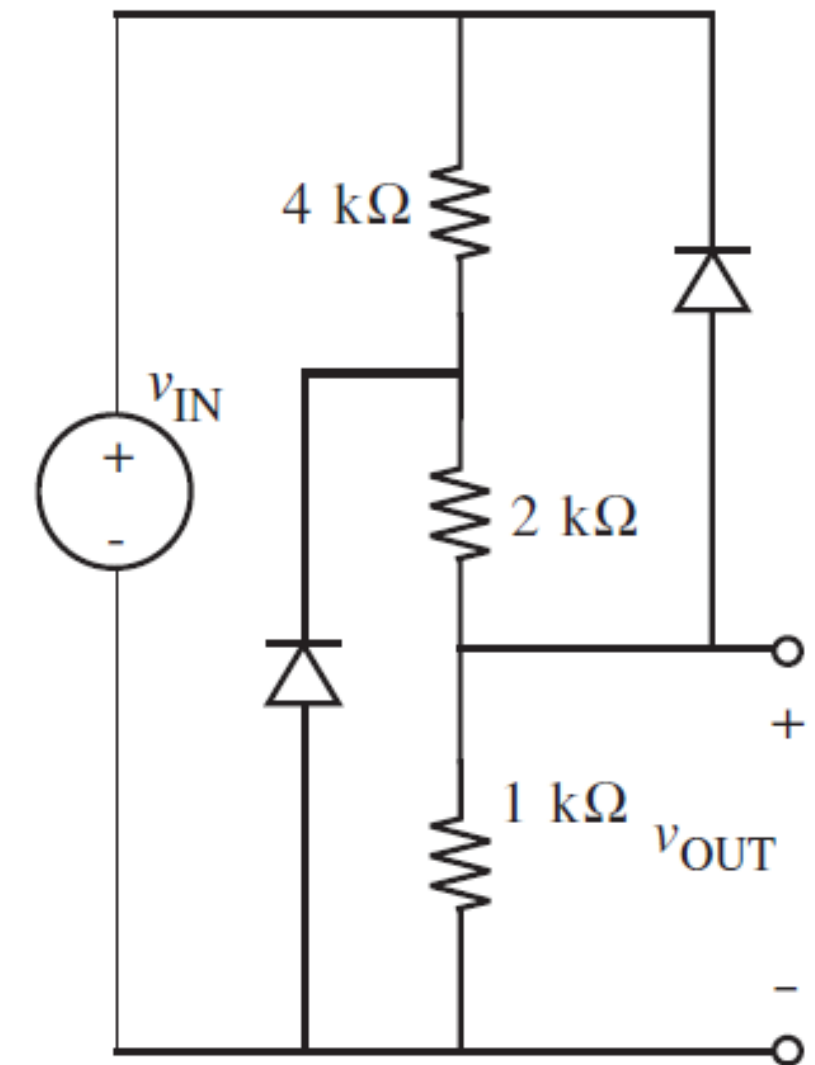
## Example 3

- Plot the output voltage  $v_{OUT}$  as a function of the input voltage  $v_{IN}$ .
- Four cases can be considered:
  - ✓  $D_1$  ON,  $D_2$  ON
  - ✓  $D_1$  ON,  $D_2$  OFF
  - ✓  $D_1$  OFF,  $D_2$  ON
  - ✓  $D_1$  OFF,  $D_2$  OFF
- Can you guess the correct case?
  - ✓ If  $v_{IN} > 0$
  - ✓ If  $v_{IN} < 0$



# Example 4





## ➤ Rectifier

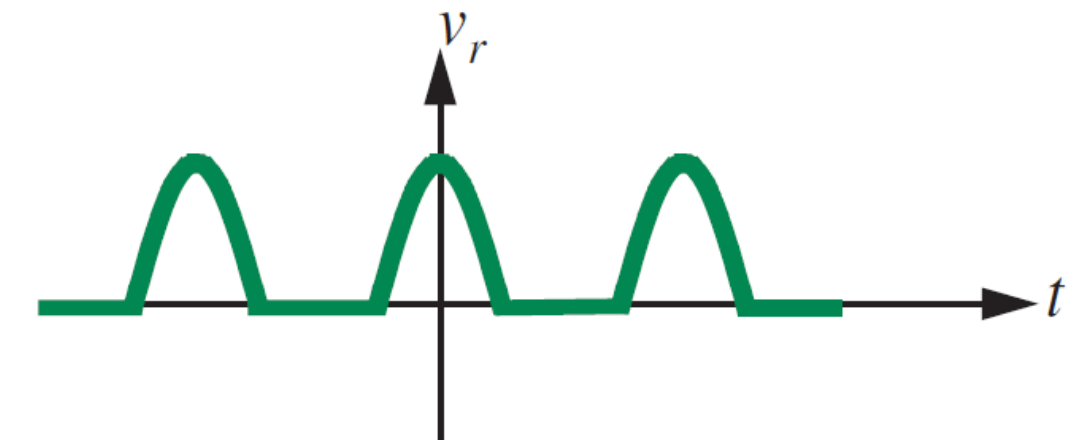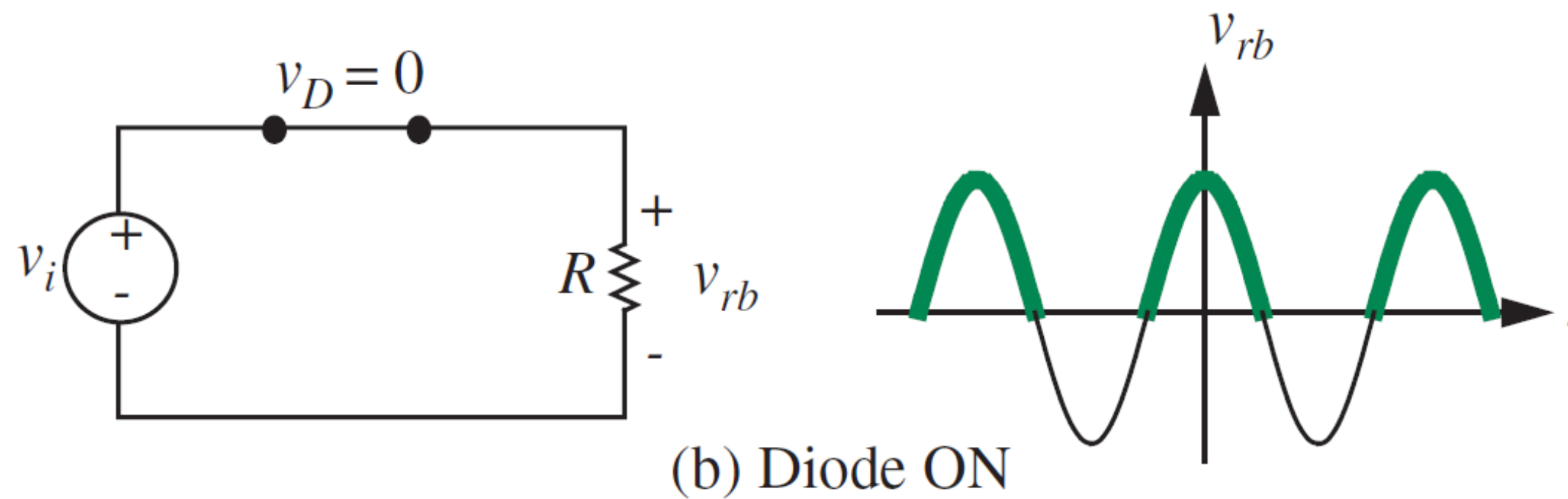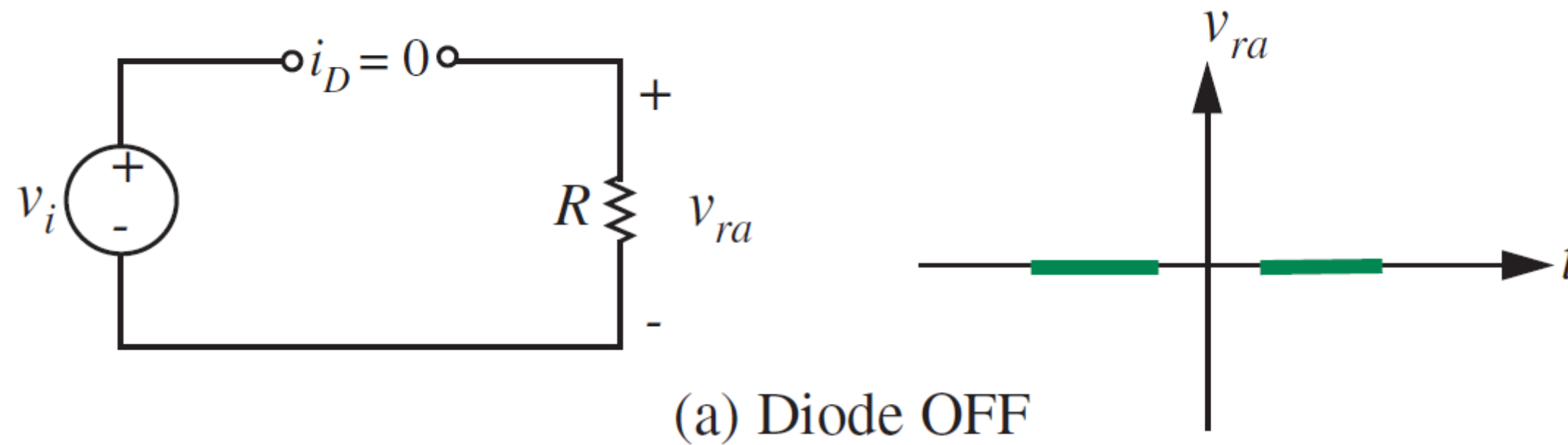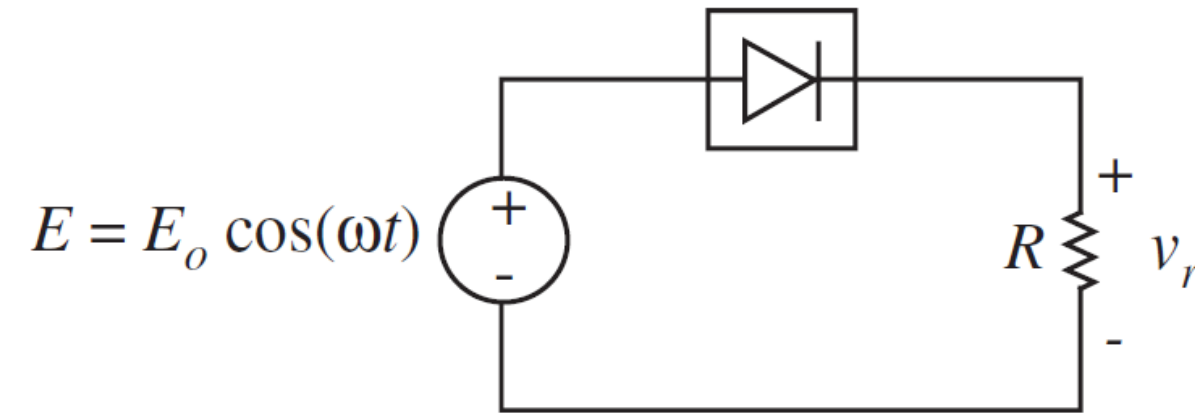





# Example 5

## ➤ Rectifier

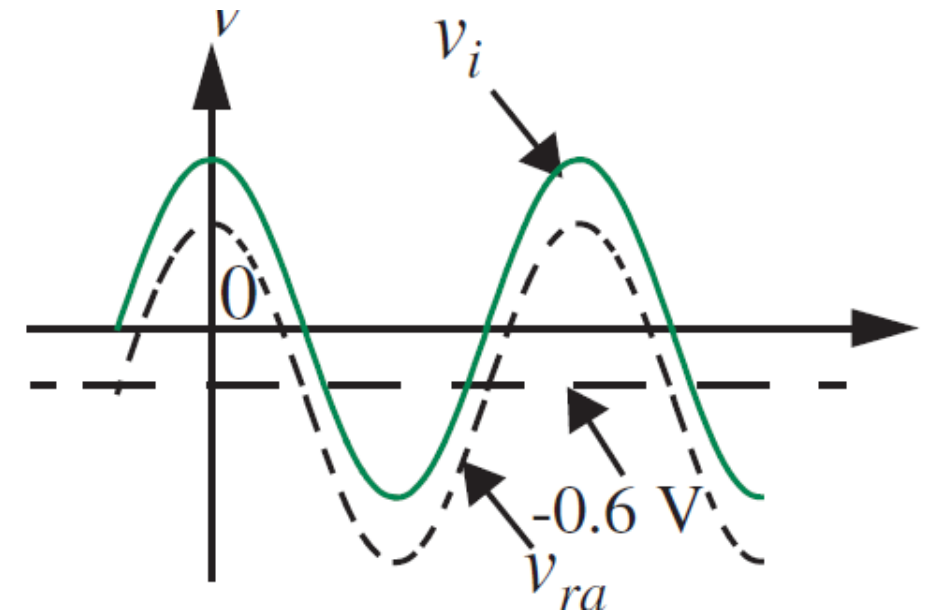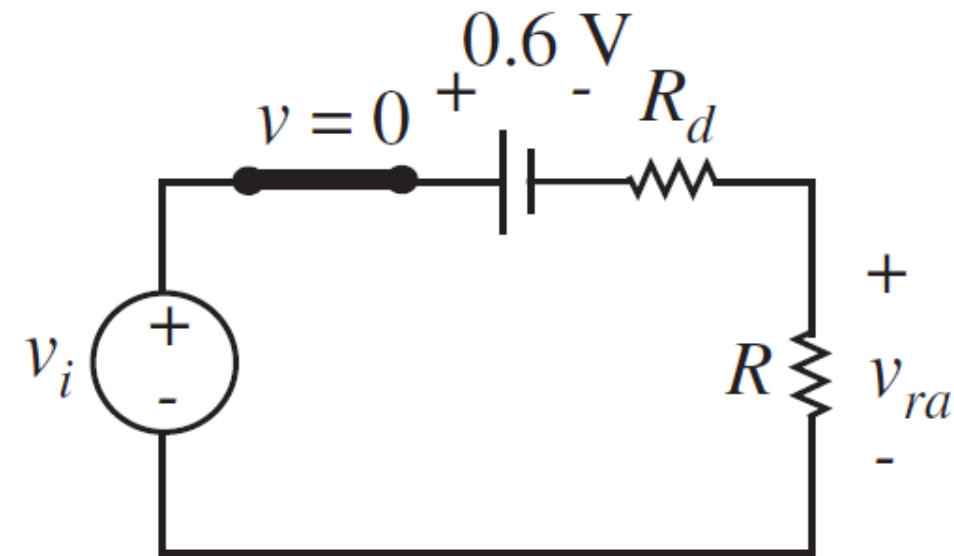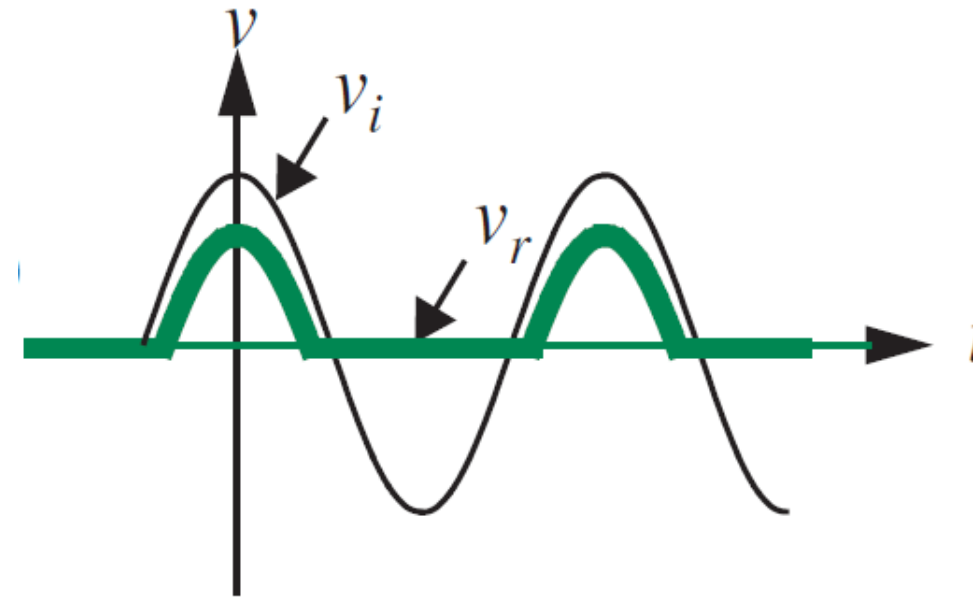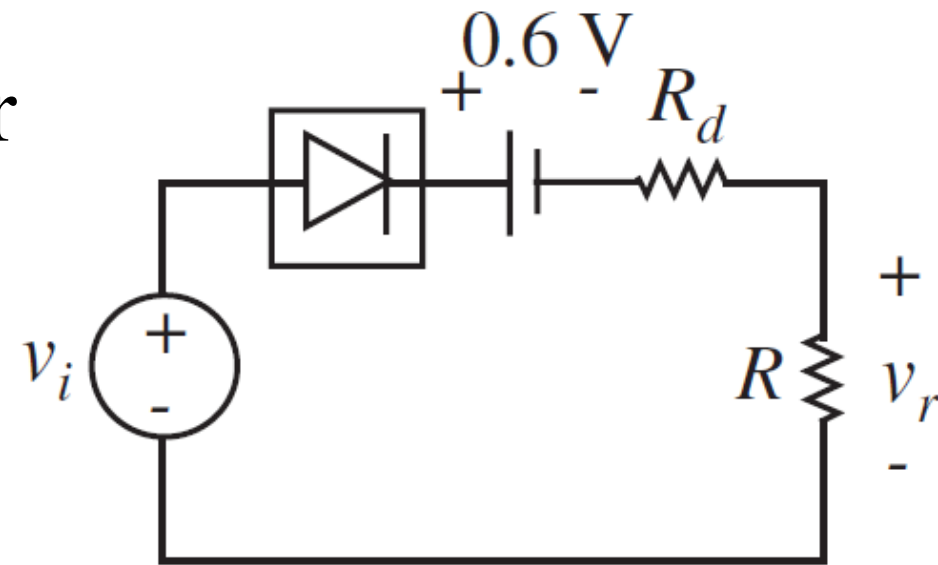

$$v_r = (v_i - 0.6) \frac{R}{R + R_d}$$

for  $v_i > 0.6$

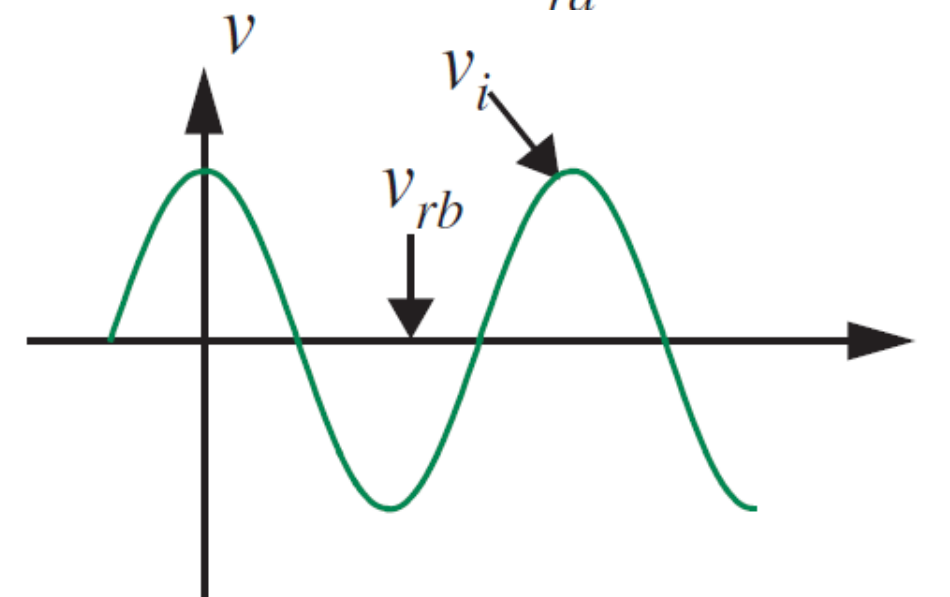
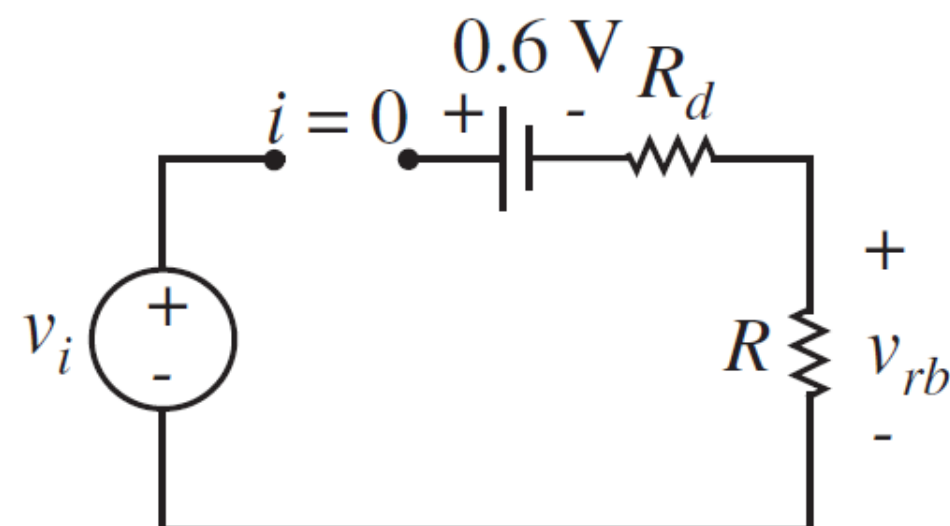


$$v_r = 0$$



for  $v_i < 0.6$

# Example 6

## ➤ Peak detector

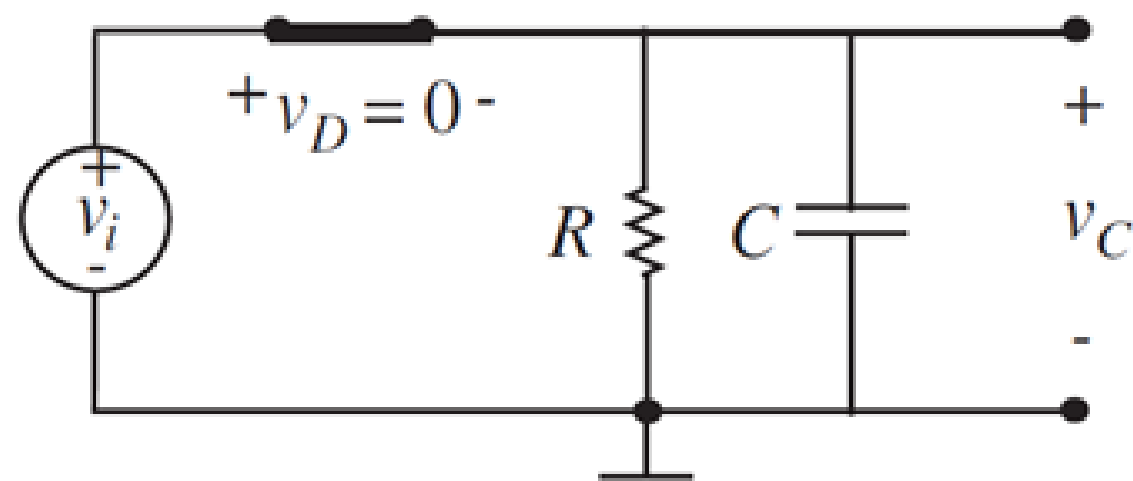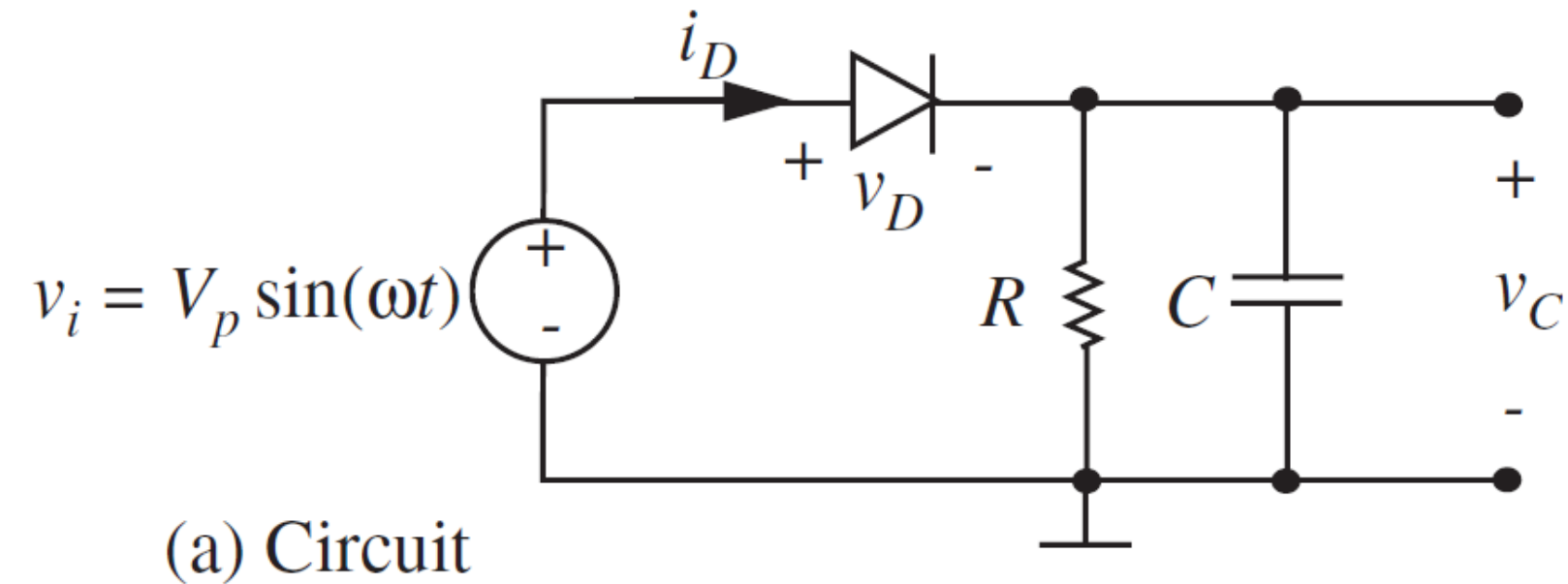

$$v_C = v_i$$

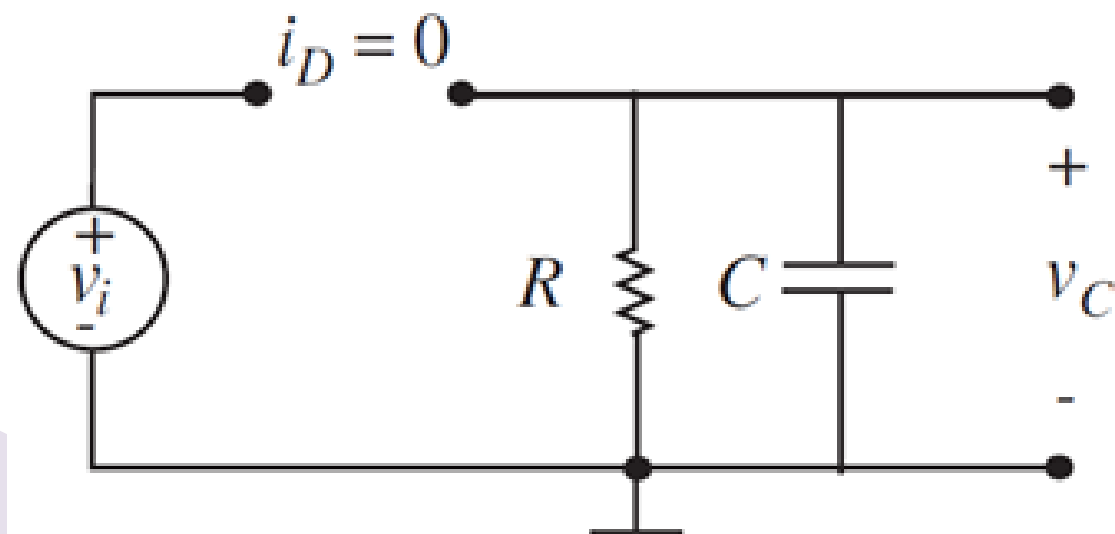
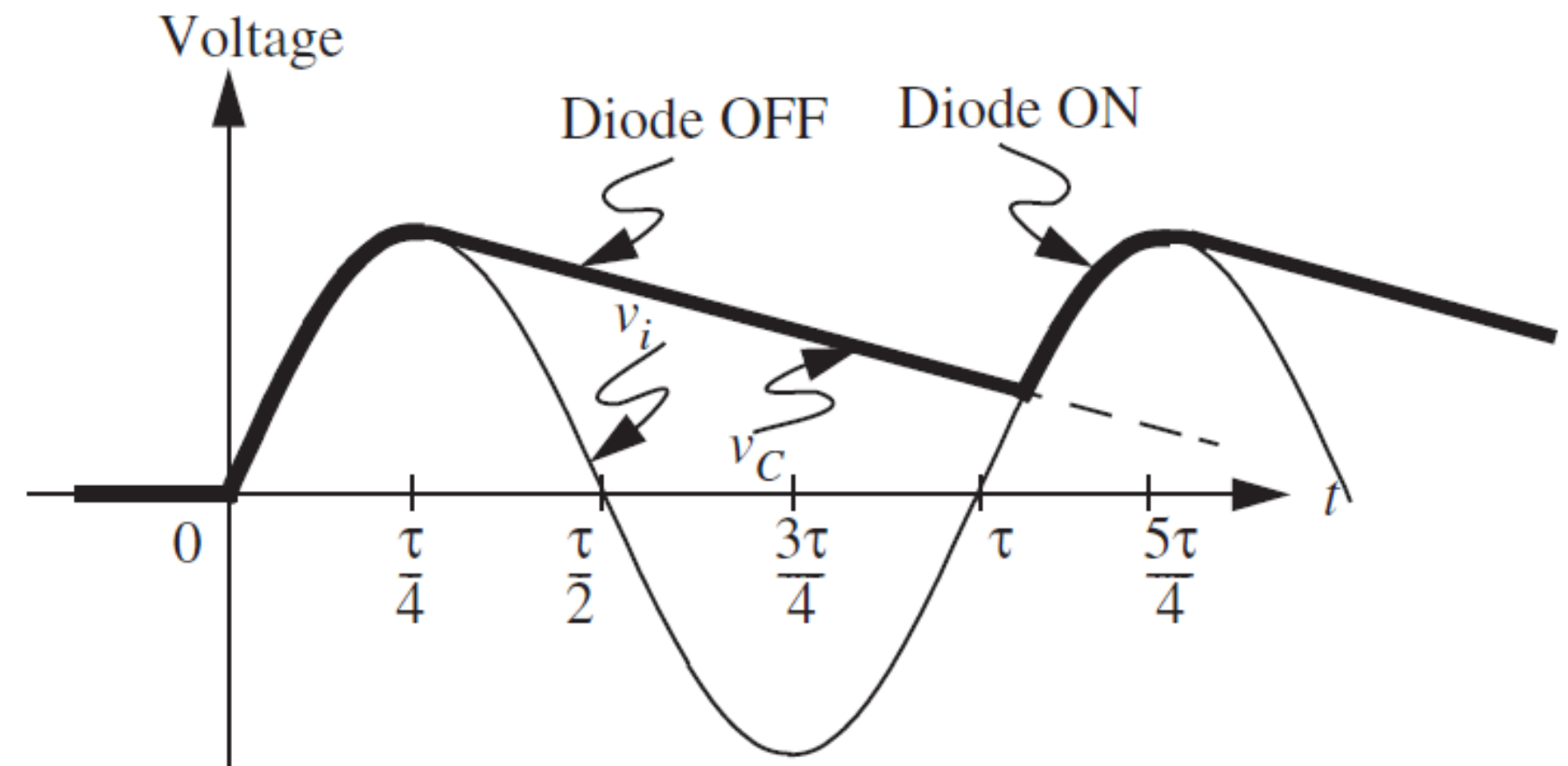


$$v_C = K e^{-t/RC}$$

$$v_C = V_p e^{-(t-\tau/4)/RC}$$

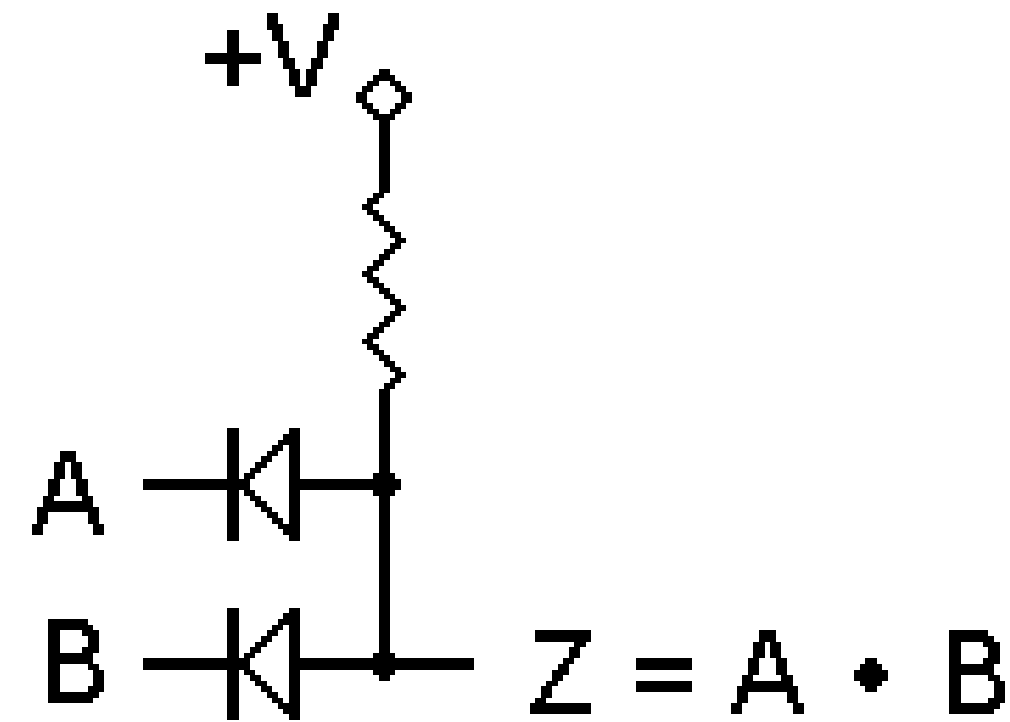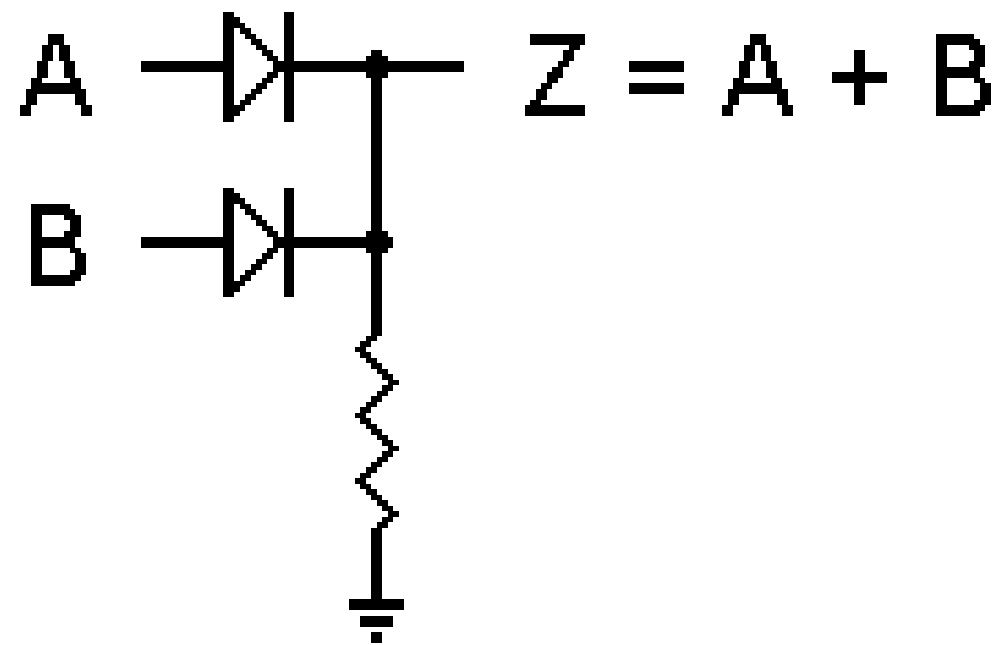
## Example 7

- Analyze the functionality of the following circuits.


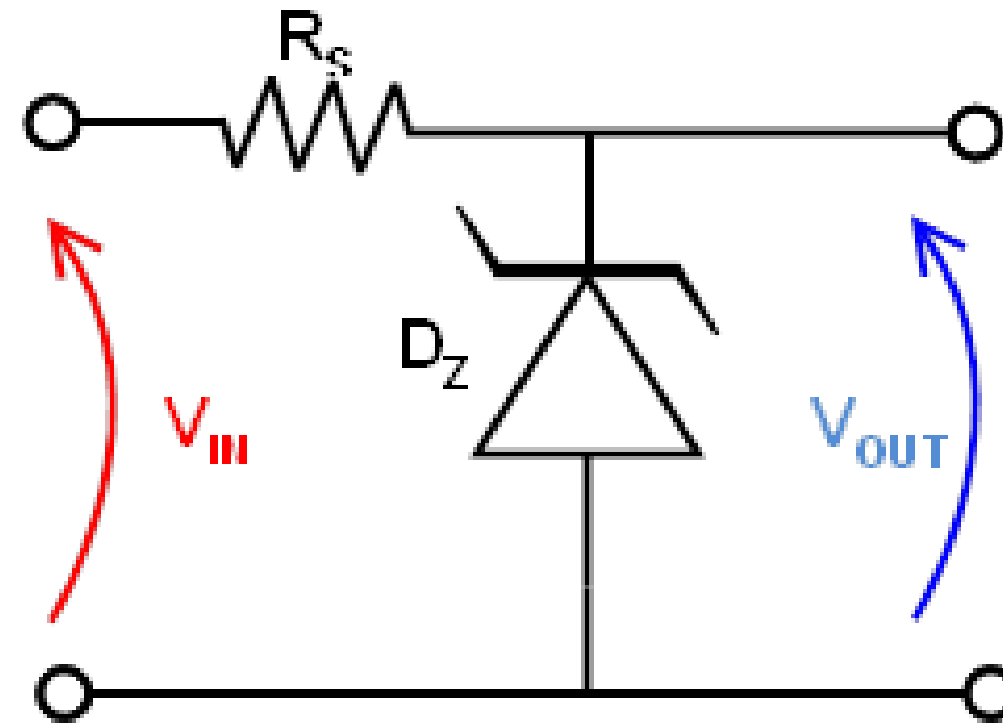
## Example 8

- In the circuit below, the threshold voltage of the Zener diode is -6 volts. Plot the output voltage  $v_{OUT}$  as a function of  $v_{IN}$ .





# Thanks

---